
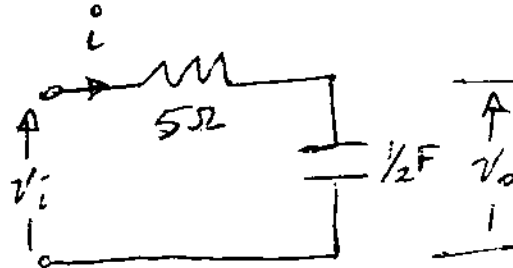


1. An RC-circuit is given below.

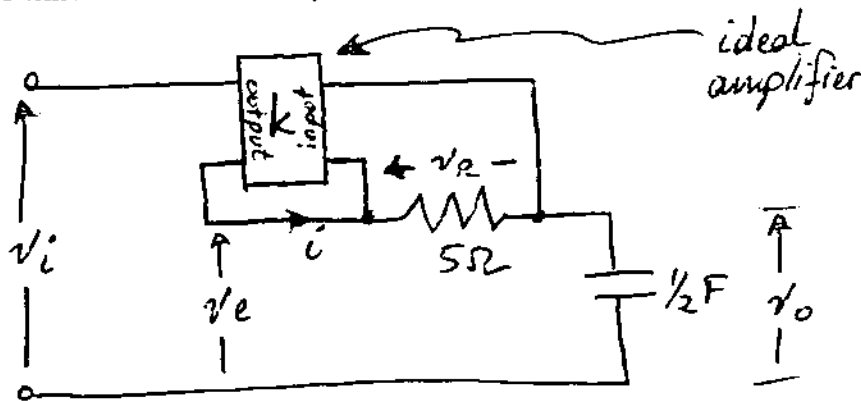

- (a) Calculate the time constant of this system. (5pts.)
- (b) Determine the 2% settling time for a unit-step input voltage. (5pts.)

To improve the time behavior of the system, a feedback controller, as shown below, is utilized.




- (c) Determine the feedback proportionality constant k to reduce the time constant to 1/5th of its original value. *Note: Draw the block diagram of the circuit, such that variables v_i , i , v_o and v_e are clearly shown to see the effects of the controller.* (15pts.)
 - (d) Find the sensitivity of the transfer function with respect to k for the k determined in part (1c) and for $\omega = 5$ rad/sec. (10pts.)
 - (e) Determine the steady-state error voltage, $v_e(\infty)$ when the input voltage, $v_i(t)$ is a unit step. (5pts.)
2. An electrical circuit with an input voltage, v_i and an output voltage, v_o has the following transfer function:

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 + 6s + 36}$$

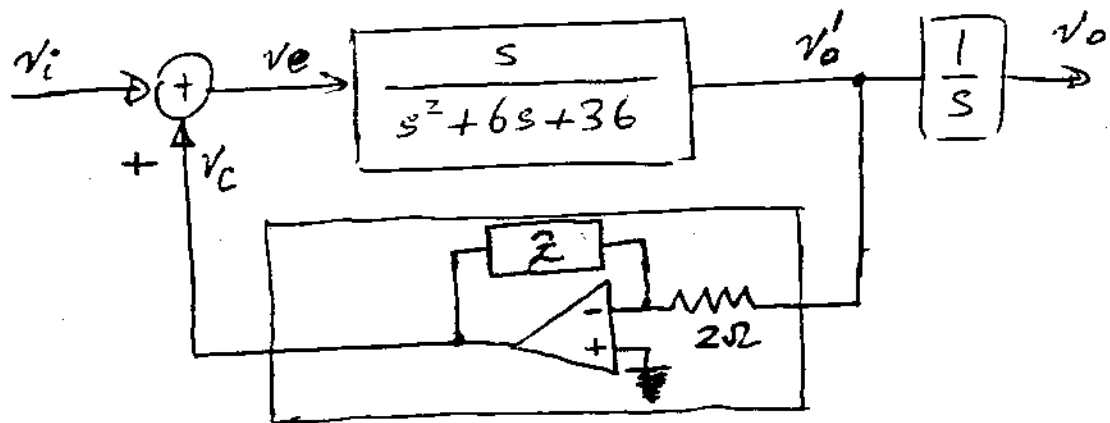- (a) Find the natural frequency and the damping constant of the system. (5pts)

To control the output voltage, the following feedback controller is implemented.



Here, Z is an unknown impedance.

- (b) Pick a Z , such that a proportional controller is implemented, and the damping constant is 0.8. (15pts)
Note: Draw the block diagram to see the effects of the controller.
- (c) Determine the steady-state error, $v_e(\infty)$ for unit-step and unit-ramp reference inputs. (10pts)
- (d) To improve the steady-state behavior, this time pick another Z , such that a proportional-integral controller is implemented, and the natural frequency and the maximum percent overshoot are 8 and 1.5165%, respectively. (20pts)
- (e) Determine the steady-state error for unit-step and unit-ramp reference inputs for the new case. (5pts)

3. A transfer function is given by

$$\frac{Y(s)}{U(s)} = \frac{10}{s} - \frac{1}{s^2 + 1} + \frac{2}{s^2 + 16} + \frac{5}{s + 3} - \frac{2}{s + 10} + \frac{1}{s + 100}$$

Determine the least-order approximation of the transfer function, such that the approximation error stays within 2% in 0.5 second for an impulse input. Do not try to simplify the approximated transfer function. (5pts)

COPYRIGHT © 1991
BY L. ACAR

#1 a) $T = 2.5 \text{ sec}$

b) $t_{s 2\%} = 10 \text{ sec}$

c) $k = 0.8$

d) $S_k \frac{v_o/v_i}{\omega} = 3.7139$
 $\omega = 5 \text{ rad/sec}$

e) $v_o(\infty) = 1$

#2 a) $\omega_n = 6$, $\zeta = 0.5$

b) $Z = 7.2 \Omega$

c) $v_o(\infty) = 1$ for unit step input

$v_o(\infty) = \infty$ for ramp input

d) $Z = 13.6 + \frac{56}{s}$ (Resistor & Capacitor)

e) $v_o(\infty) = 0.5625$ for unit step input

$v_o(\infty) = \infty$ for ramp input

#3 $\frac{Y(s)}{U(s)} \approx \frac{10}{s} - \frac{1}{s^2+1} + \frac{2}{s^2+16} + \frac{5}{s+3}$

