

Project 1: CE Amplifier

Project 1
Report

9/17/2013

Introduction:

The purpose of this project was to design a Common emitter amplifier circuit. The transistor had to be npn, not from the lab, and available from newark.com. The criteria to be met included that the circuit must be bias stable, must have AC gain stability and an emitter bypass capacitor, must have an undistorted output, must have suitable coupling capacitors that meet my assigned lower cut off frequency of 60Hz.

Experiment:

To begin the design, I looked through the available transistors on newark.com, and chose the 2N551 npn transistor for my amplifier. After comparing it with some other transistors it seemed to have values that would match most closely to my input voltage (see datasheet and Table 3). 5V were chosen for the ease of calculations.

Next, I chose $I_C = 1mA$ for simplicity of design

effect (Keep R_E high to match input impedance so no voltage gain lost)

For the AC analysis, (Figure 2) I calculated r_{ff} (calculation 8), g_m (calculation 9), and A_v (calculation 10). Next, I needed to find the values of the coupling capacitors and bypass capacitor. To calculate C_E , I rearranged the equation to calculate frequency (calculation 11), where f was my lower cutoff frequency of 60 Hz. Since C_E was to be the dominating capacitor, it was necessary to choose a frequency much lower than 60 Hz to ensure that the coupling capacitors would not interfere with C_E . I chose a frequency of 0.6 Hz for C_1 and 0.006 Hz for C_2 . This ensured values that were available in the lab, and that the capacitors would not dominate the circuit (calculations 12-13).

After building and testing the circuit, I measured the current and voltage values to compare (Table 1). Recalculating gave $\beta_{\text{transistor}} = 162.75438$, which was used along with other measured values for another set of calculations.

Next, the upper and lower cutoff frequencies were measured using the oscilloscope (figures 3 and 4).

The midband gain was in that range (figure 5). The gain was calculated to be $\frac{1.91V}{0.0244V} = 64.966$.

After getting these values, the parameters C_U , C_M , and C_{ff} were calculated to see how the calculated upper cutoff frequency compares to the measured upper cutoff frequency (Calculations 14-18). To do this, SPICE parameters were used to find C_{ff} , C_U , and C_M .^(Table 3) After calculating f_{ff} to be 3.5844 MHz, it was much larger than the measured 410 kHz. Since R_S was the only estimated value, it must be skewing the data.

somehow. Using an Excel spreadsheet, R_s was increased until the gain was lowered and the cutoff frequency was lowered to very close to my measured cutoff frequency. That value was 525 Ω . Using a 523- Ω resistor connected in series between the circuit and frequency generator, the upper and lower cutoff frequencies were measured again (Figure 6-7). My new upper cutoff frequency was 352 kHz, and the new lower cutoff frequency was 47.4 Hz. The voltage and current parameters were measured again to compare (Table 2). The gain was reduced to $1.94V_{out}/38.1mV = 50.9186$, which is still relatively good. β increased to 187,596, which is ok because the $2\beta_s$ calculated were within 1% of each other.

Next, the BJT SPICE parameters were calculated again for comparison (calculations 19-22). This increased C_M by 1,063.9 times.

Conclusion

It is possible to control both the gain and the midband with an amplifier circuit. I was able to use a chosen lower cutoff frequency and calculate the values of both bypass and coupling capacitors to cause this cutoff. Controlling the high end cutoff was trickier, but I was able to adjust R_s to an appropriate number that did not change my original value very much. When recalculating the C_H , C_U , and C_M parameters, I did not get the expected cutoff frequency. This is probably due to an error in calculation,

because the upper cutoff frequency increased. The fault was not in the circuit itself, because my measured values were very similar when comparing Tables 1 and 2. It would be interesting to see if there is a formula to find R_s given a cutoff frequency instead of trying to adjust it. Increasing R_s definitely helped, but there should be a better way to find that value apart from trial and error. R_s also adjusted the lower cutoff frequency as well. Internal resistance can be a big issue in cases like this.

Calculations

+5V

5V

Dc

1)


3)

4)

5)

7)

AC Analysis:

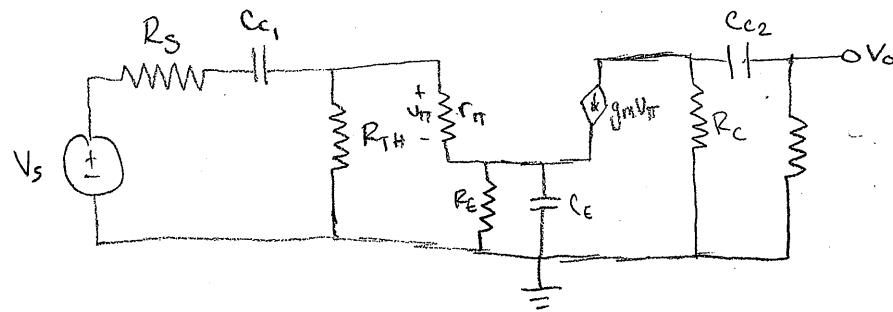

Capacitor Calculations:

• C_E

T_A
 T_B

$$II) C_E =$$

3722 Hz


ring less for

ω_1 and ω_2

Capacitor Calculations (cont.) :

C_{c1}

Chose $f_{C_1} = 0.6\text{Hz}$

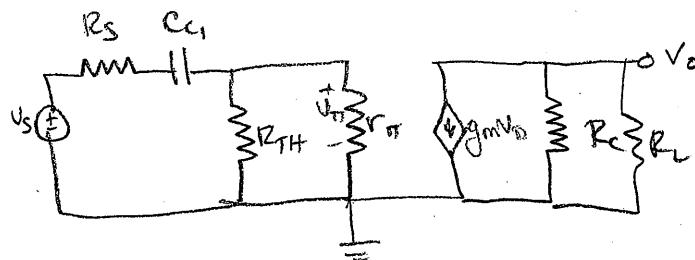


$$T_{S_1} = (R_s + R_{TH}/(r_{pi}))C_{c1}$$

12) $C_{c1} = \boxed{\quad} = 169\mu\text{F}$

C_{c2}

13) $C_{c2} = \boxed{\quad}$

$$\approx C_2(K_C K_L)$$

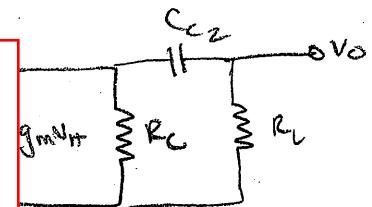

C_{π}, C_L, C_M using SPICE Parameters

14) C_L

15) C_L

16) C_M

17)

μF

$$\equiv$$

$$t_p = (C_{\pi}/1C_M)(R_{\pi} + R_S + R_{\pi}) = 4.44021 \times 10^{-8} s$$

$$18) f_H = \frac{1}{2\pi t_p} = 3.5844 \text{ MHz}$$

• Recalcula



Figures and Tables

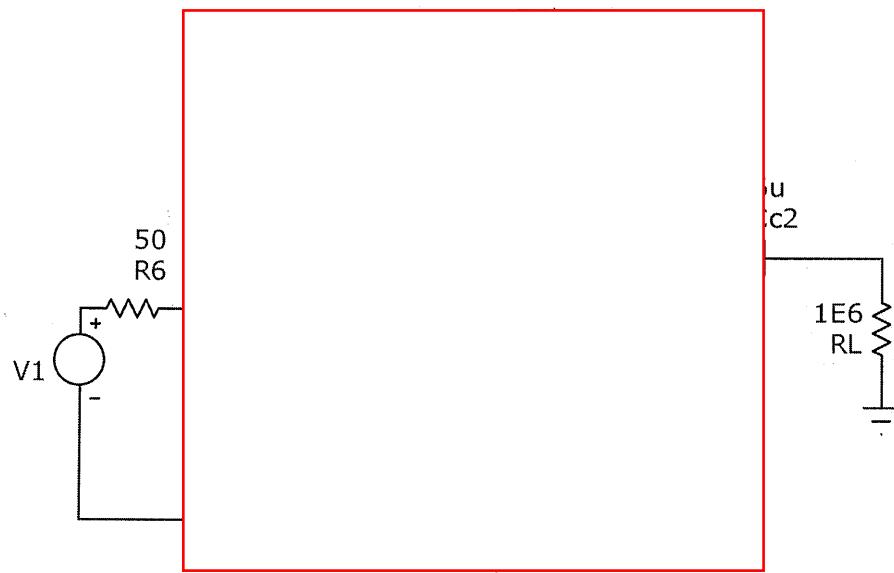


Figure 1: DC Common Emitter Circuit

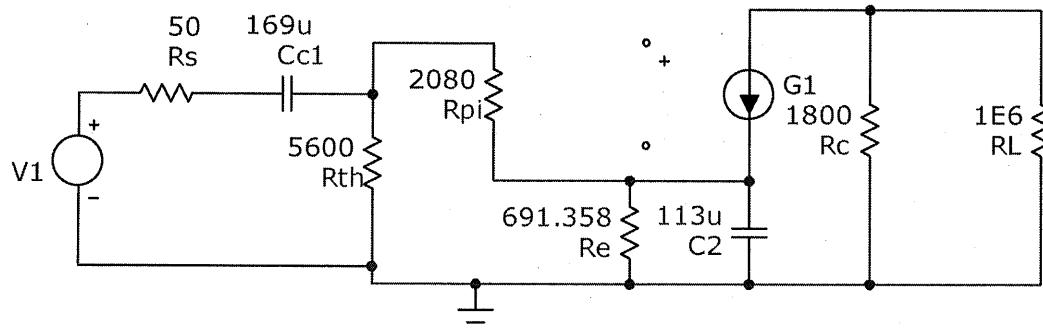


Figure 2: AC equivalent

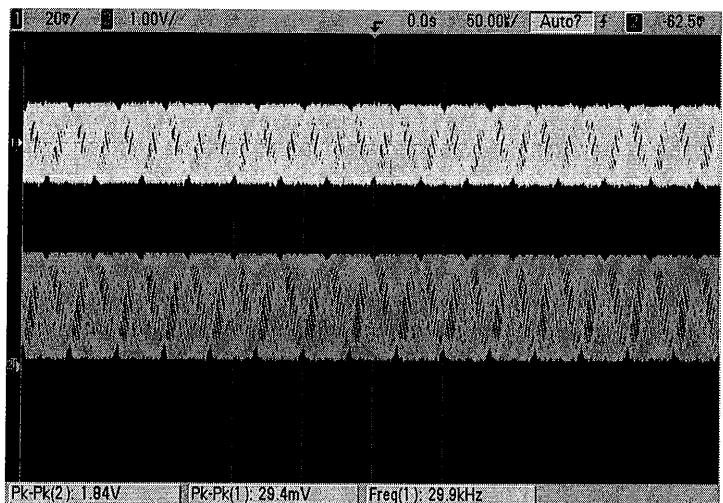


Figure 5: Midband Gain region


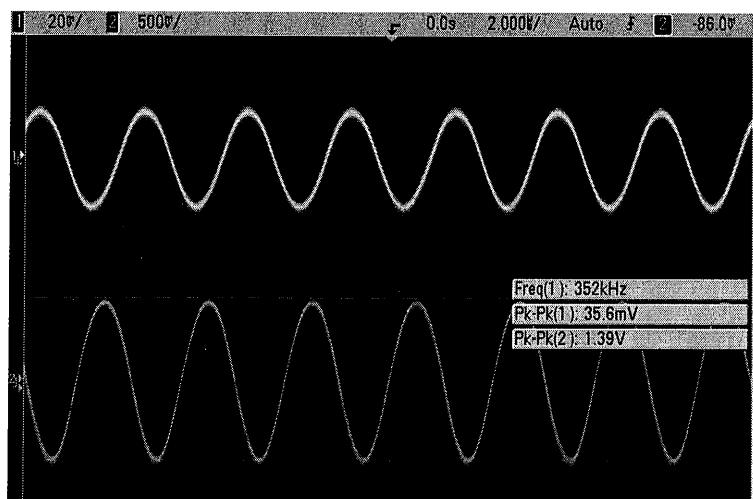


Figure 6: Upper cutoff frequency after changing Rs

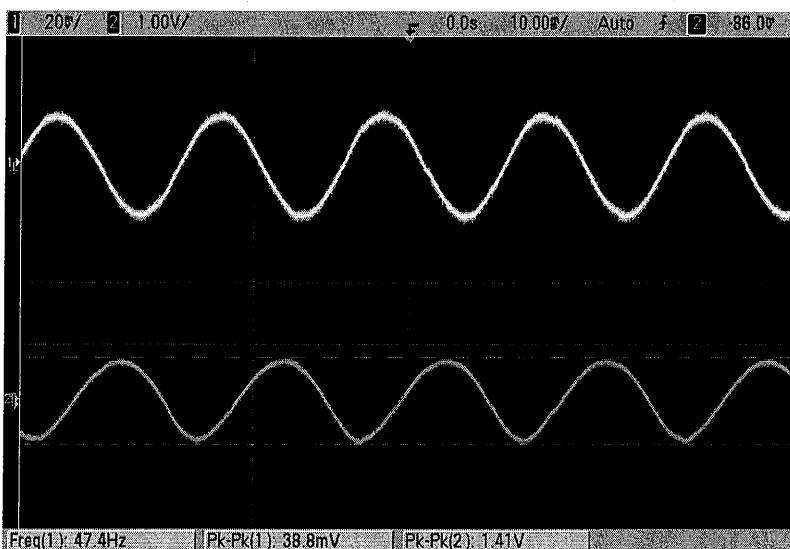

*** Power Discrete Bipolar Electrical Parameter ***

 ** Power Amplifier Transistor

 ** Product: 2N5551 / TO-92

```

.MODEL 2N5551 npn
+ IS      = 2.04174E-14    BF      = 122.7        NF      = 1
+ BR      = 17.075          NR      = 1            ISE     = 5.7544E-13
+ NE      = 2                ISC     = 2.29087E-11  NC      = 1.5
+ VAF     = 176.831         VAR     = 35.3         IKF     = 0.144627
+ IKR     = 0.0158489       RB      = 125          RBM     = 8.092
+ IRB    = 1.12202E-7       RE      = 0.14         RC      = 1.8
+ CJE     = 2.450889E-11   VJE     = 0.7175263    MJE     = 0.3413777
+ FC      = 0.5              CJC     = 5.03462E-12  VJC     = 0.5
+ MJC    = 0.3226407       XTB     = 1.2776        EG      = 1.2222
+ XTI     = 3                TF      = 1.73E-11

```

* Creation : Sep.-24-2004

 * Fairchild Semiconductor

Table 3: Fairchild 2N5551 SPICE model




April 2006

2N5551- MMBT5551 NPN General Purpose Amplifier

Features

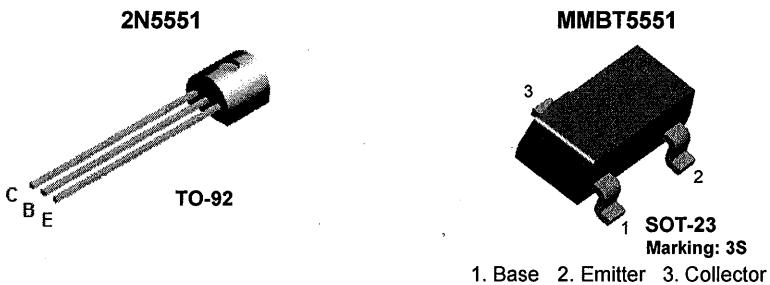- This device is designed for general purpose high voltage amplifiers and gas discharge display drivers.
- Suffix "C" means Center Collector in 2N5551 (1. Emitter 2. Collector 3. Base)
- Suffix "-Y" means h_{FE} 180~240 in 2N5551 (Test condition : $I_C = 10mA$, $V_{CE} = 5.0V$)



Absolute Maximum Ratings * $T_a = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Value	Units
V_{CEO}	Collector-Emitter Voltage	160	V
V_{CBO}	Collector-Base Voltage	180	V
V_{EBO}	Emitter-Base Voltage	6.0	V
I_C	Collector current - Continuous	600	mA
T_J, T_{stg}	Junction and Storage Temperature	-55 ~ +150	°C

* These ratings are limiting values above which the serviceability of any semiconductor device may be impaired.

NOTES:

- These ratings are based on a maximum junction temperature of 150 degrees C.
- These are steady state limits. The factory should be consulted on applications involving pulsed or low duty cycle operations.

Thermal Characteristics $T_a = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Max		Units
		2N5551	*MMBT5551	
P_D	Total Device Dissipation Derate above 25°C	625 5.0	350 2.8	mW mW/°C
$R_{\theta JA}$	Thermal Resistance, Junction to Case	83.3		°C/W
$R_{\theta JA}$	Thermal Resistance, Junction to Ambient	200	357	°C/W

* Device mounted on FR-4 PCB 1.6" x 1.6" x 0.06."

Typical Performance Characteristics

Figure 1. Typical Pulsed Current Gain vs Collector Current

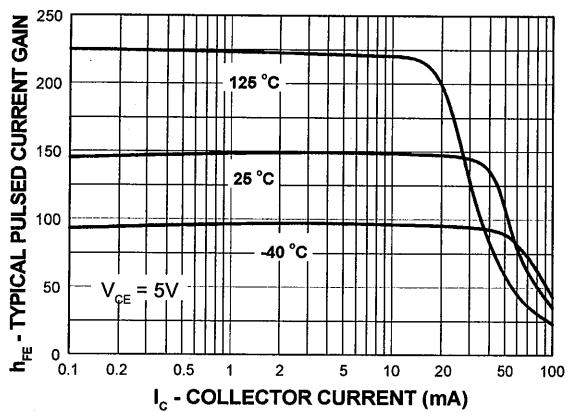


Figure 2. Collector-Emitter Saturation Voltage vs Collector Current

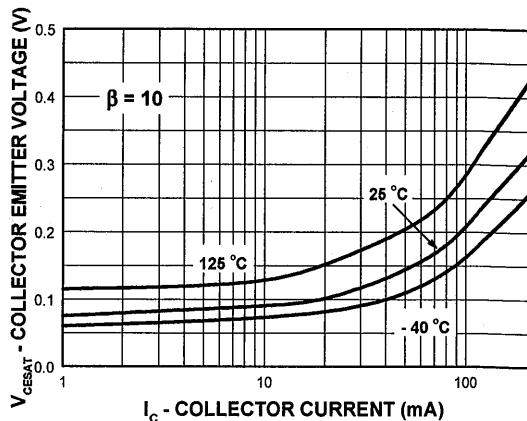


Figure 3. Base-Emitter Saturation Voltage vs Collector Current

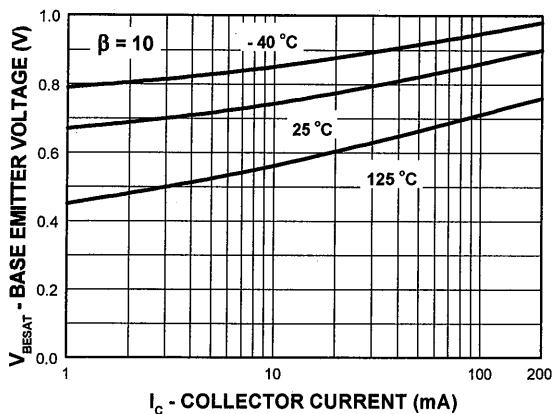


Figure 4. Base-Emitter On Voltage vs Collector Current

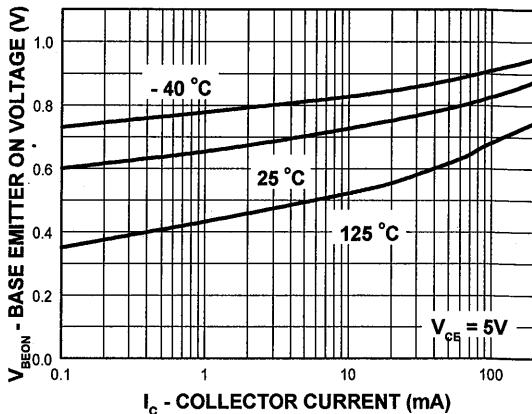


Figure 5. Collector Cutoff Current vs Ambient Temperature


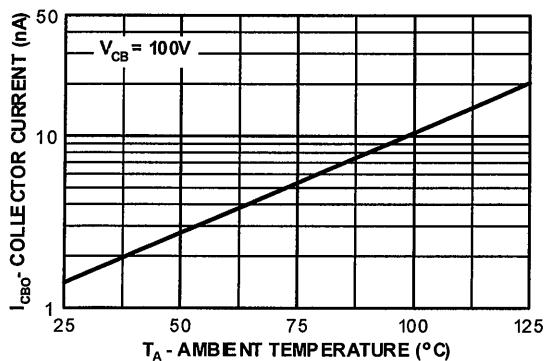


Figure 6. Input and Output Capacitance vs Reverse Voltage

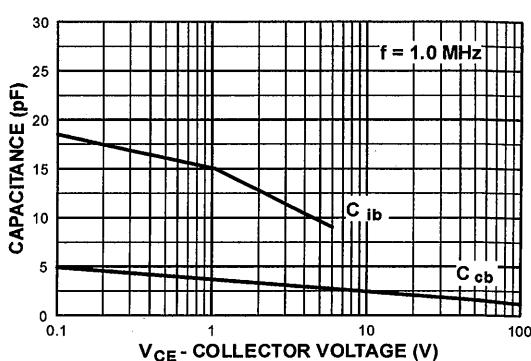

TRADEMARKS

The following are registered and unregistered trademarks Fairchild Semiconductor owns or is authorized to use and is not intended to be an exhaustive list of all such trademarks.

ACEx™	FAST®	ISOPLANAR™	PowerEdge™	SuperFET™
ActiveArray™	FASTR™	LittleFET™	PowerSaver™	SuperSOT™-3
Bottomless™	FPS™	MICROCOUPLER™	PowerTrench®	SuperSOT™-6
Build it Now™	FRFET™	MicroFET™	QFET®	SuperSOT™-8
CoolFET™	GlobalOptoisolator™	MicroPak™	QS™	SyncFET™
CROSSVOLT™	GTO™	MICROWIRE™	QT Optoelectronics™	TCM™
DOME™	HiSeC™	MSX™	Quiet Series™	TinyLogic®
EcoSPARK™	I ² C™	MSXPro™	RapidConfigure™	TINYOPTO™
E ² CMOS™	i-Lo™	OCX™	RapidConnect™	TruTranslation™
EnSigna™	ImpliedDisconnect™	OCXPro™	μSerDes™	UHC™
FACT™	IntelliMAX™	OPTOLOGIC®	ScalarPump™	UltraFET®
FACT Quiet Series™		OPTOPLANAR™	SILENT SWITCHER®	UniFET™
Across the board. Around the world.™		PACMAN™	SMART START™	VCX™
The Power Franchise®		POP™	SPM™	Wire™
Programmable Active Droop™		Power247™	Stealth™	

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS. THESE SPECIFICATIONS DO NOT EXPAND THE TERMS OF FAIRCHILD'S WORLDWIDE TERMS AND CONDITIONS SPECIFICALLY THE WARRANTY THEREIN, WHICH COVERS THESE PRODUCTS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

PRODUCT STATUS DEFINITIONS

Definition of Terms

Datasheet Identification	Product Status	Definition
Advance Information	Formative or In Design	This datasheet contains the design specifications for product development. Specifications may change in any manner without notice.
Preliminary	First Production	This datasheet contains preliminary data, and supplementary data will be published at a later date. Fairchild Semiconductor reserves the right to make changes at any time without notice in order to improve design.
No Identification Needed	Full Production	This datasheet contains final specifications. Fairchild Semiconductor reserves the right to make changes at any time without notice in order to improve design.
Obsolete	Not In Production	This datasheet contains specifications on a product that has been discontinued by Fairchild semiconductor. The datasheet is printed for reference information only.

Rev. I19