

### Project 3: Schmitt Trigger

The purpose of this test was to determine the upper and lower hysteresis voltages of the Schmitt trigger using an LM741 Op-Amp to produce a unique

In order to determine the upper and lower hysteresis voltages, a zero crossing test was first performed to determine the upper and lower hysteresis voltages of the detection circuit was used (Figure 1), and the upper and lower hysteresis voltages were determined to be  $V_H = 11.9$  and  $V_L = -10.9$  (Figure 2).

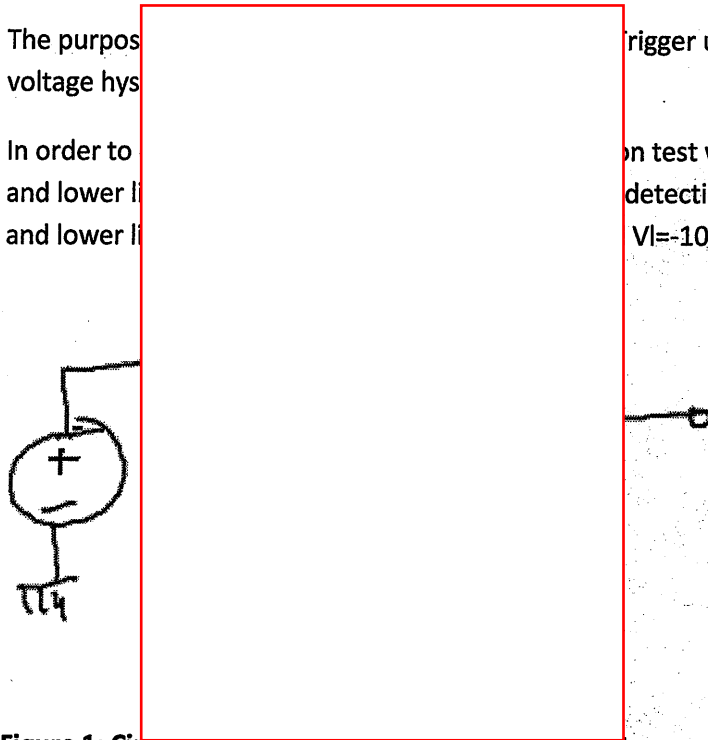


Figure 1: Circuit used for zero crossing detection test


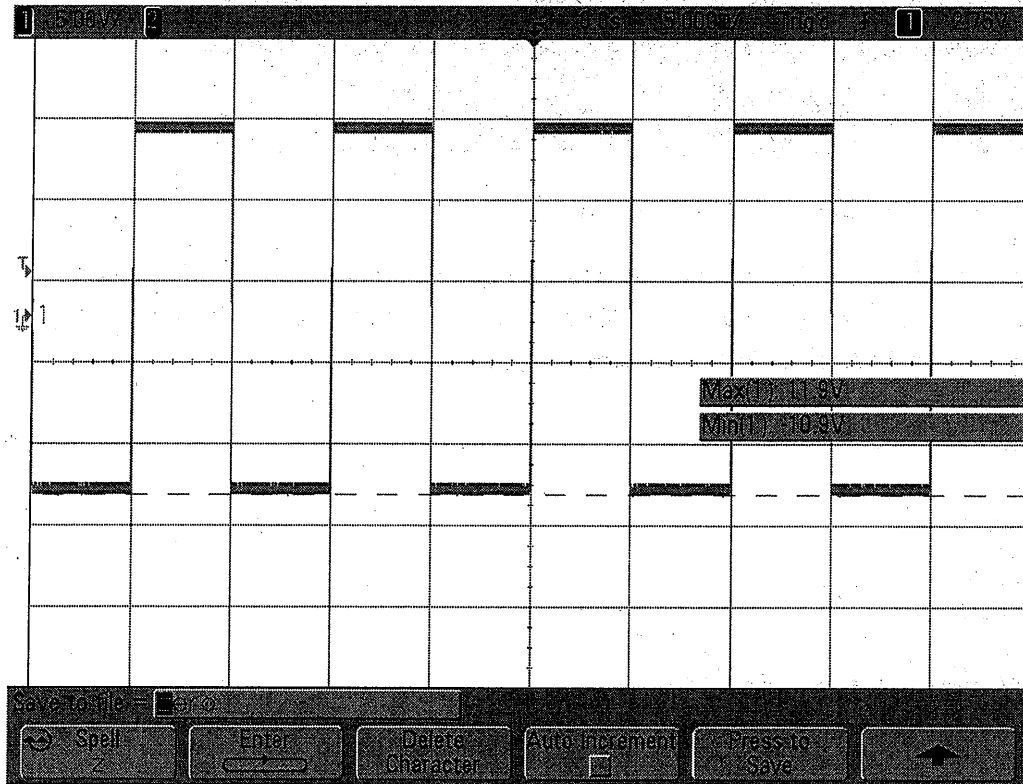


Figure 2:  $V_H$  and  $V_L$  from zero crossing test

Next, the parameters for the circuit (Figure 3) were calculated using the assigned parameters (See Calculations page). The circuit was then built and tested. The measured  $V_{th}$  and  $V_{tl}$  were  $-1.511\text{ V}$  and  $4.5337\text{ V}$  respectively, which were fairly close to the calculated values.  $V_{ref}$  had to be lowered to  $1.8\text{ V}$  in order to get this hysteresis, which was a drop of  $0.7\text{ V}$ . This hysteresis can be seen in figure 4.

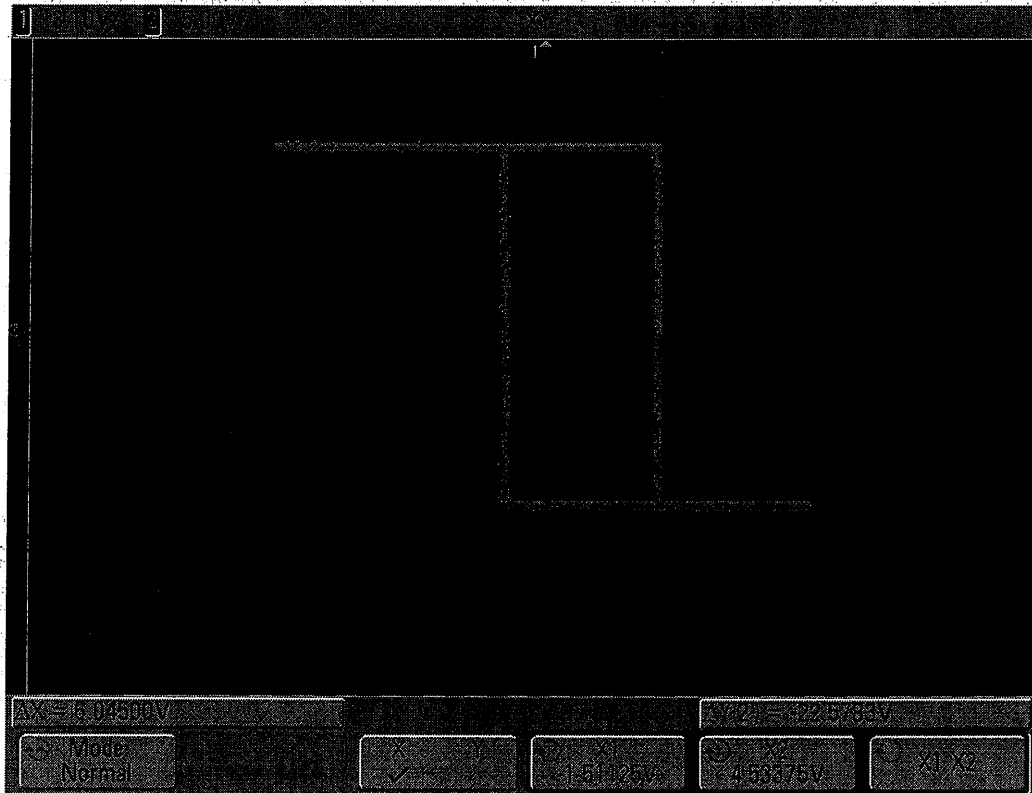

**Figure 4: voltage hysteresis of operating Schmitt Trigger**

The circuit (Figures 5 and 6) was simulated using Micro-CAP.

When the circuit was simulated in PICE, the expected hysteresis should look like the square wave in figure 6 was simulated, but PICE were unable to simulate the circuit correctly.

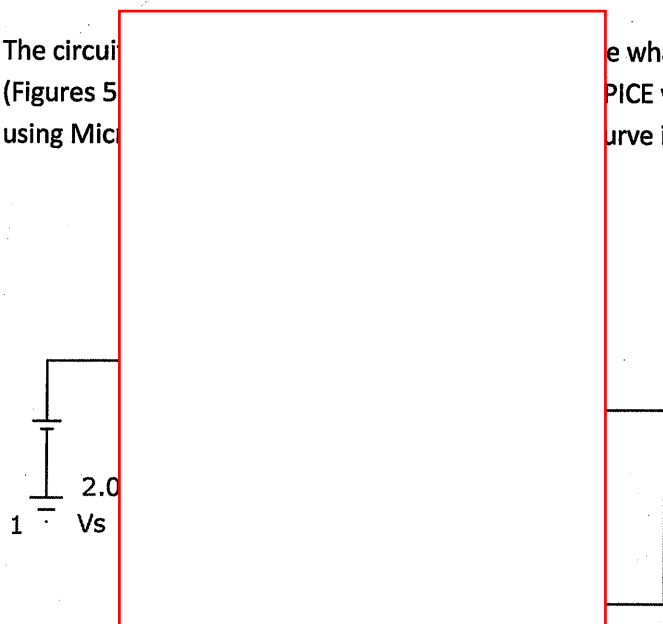


Figure 5: Circuit used to simulate Hysteresis


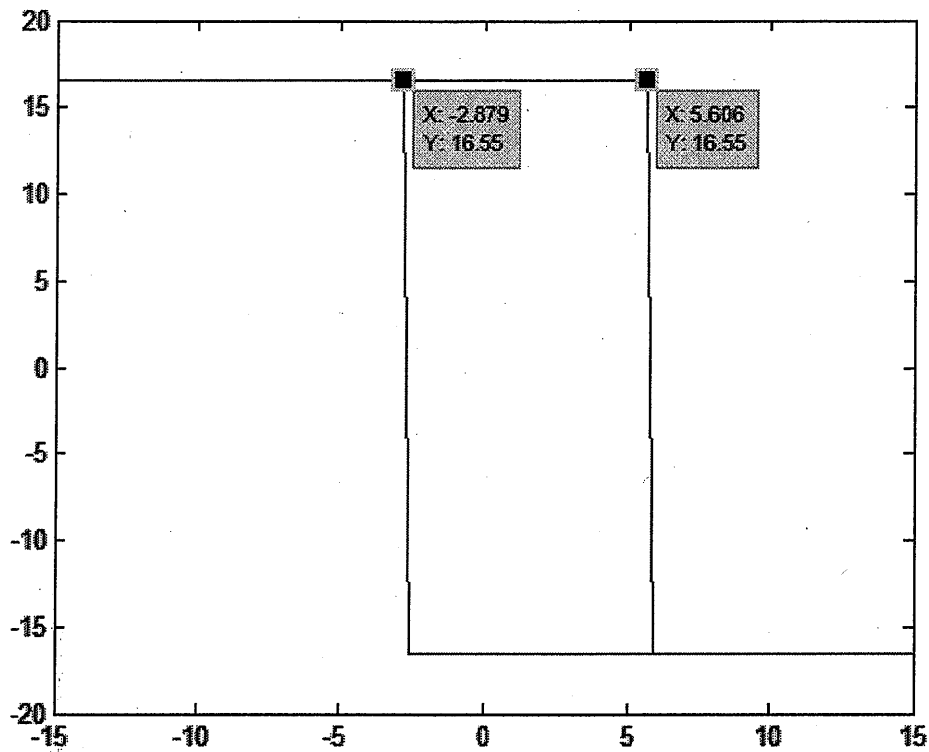


Figure 6: Simulated Hysteresis loop

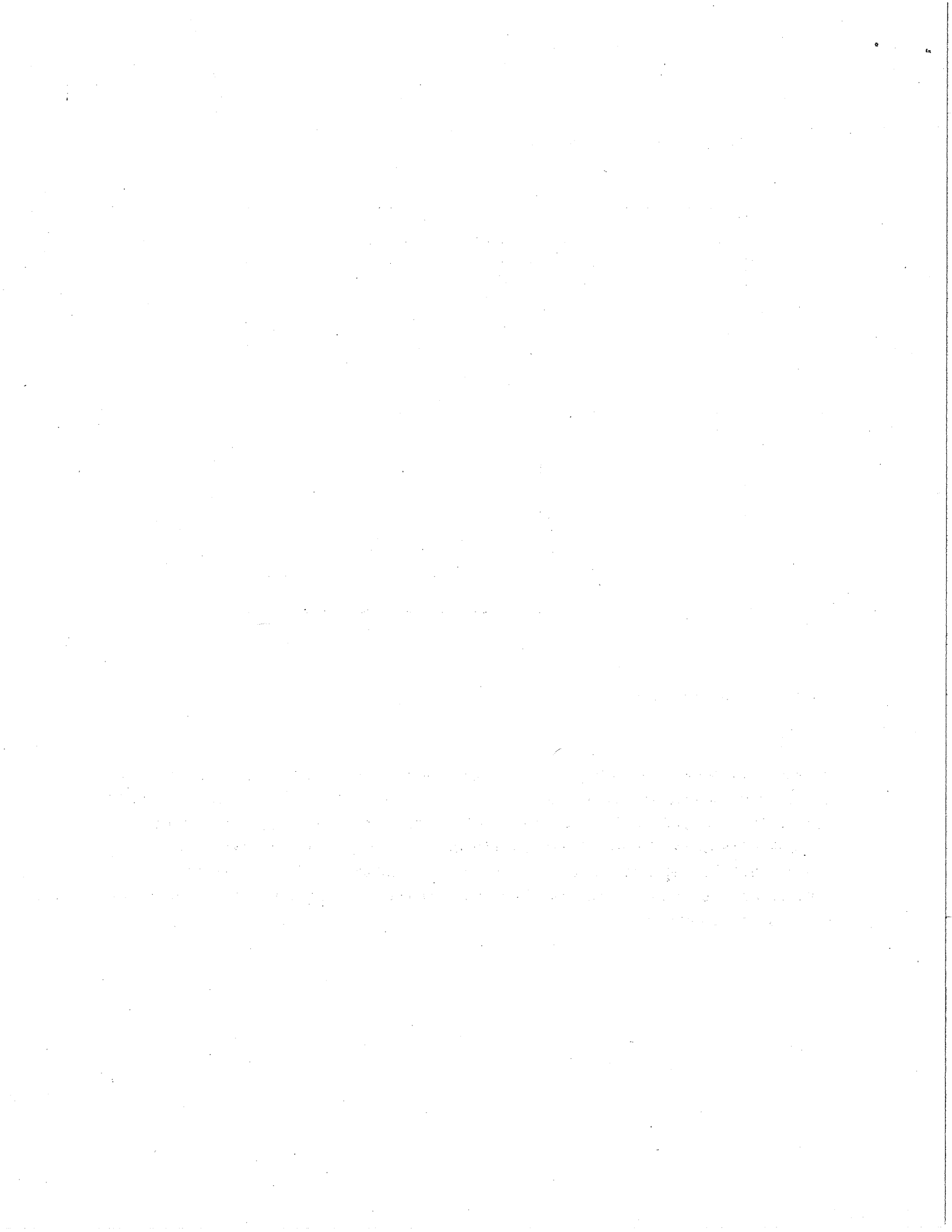**Conclusion:**

After doing this experiment, a Schmitt Trigger was correctly designed based on the given parameters. A zero crossing test was used to determine  $V_h$  and  $V_l$ , and these parameters were then used to design the circuit. When tested, this circuit worked as expected. The trickiest part of this experiment was the simulation. The software has some issues simulating the Hysteresis loop with the correct voltage parameters. The Schmitt trigger is a way to control the output voltage in a range by adjusting the input voltage. This project was a good example of a situation where the simulation does not at all reflect what happens to the actual circuit.



# Calculations Page

$V^+ =$

$V_{ref}$


$V_{ref}$

$V_i$

$V_i$

0

+

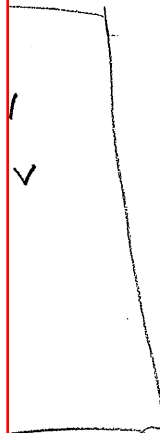

1.8k $\Omega$

0.035V

$$V_{TH} = V_s$$

$$V_{TL} = V$$

