


Project 5: D/A and A/D Converters

The purpose of resistors, op-am

First, the number Calculations). The calculated(Calcul actuality, $3R/2$ were used. The voltage levels in




ee
istors
the

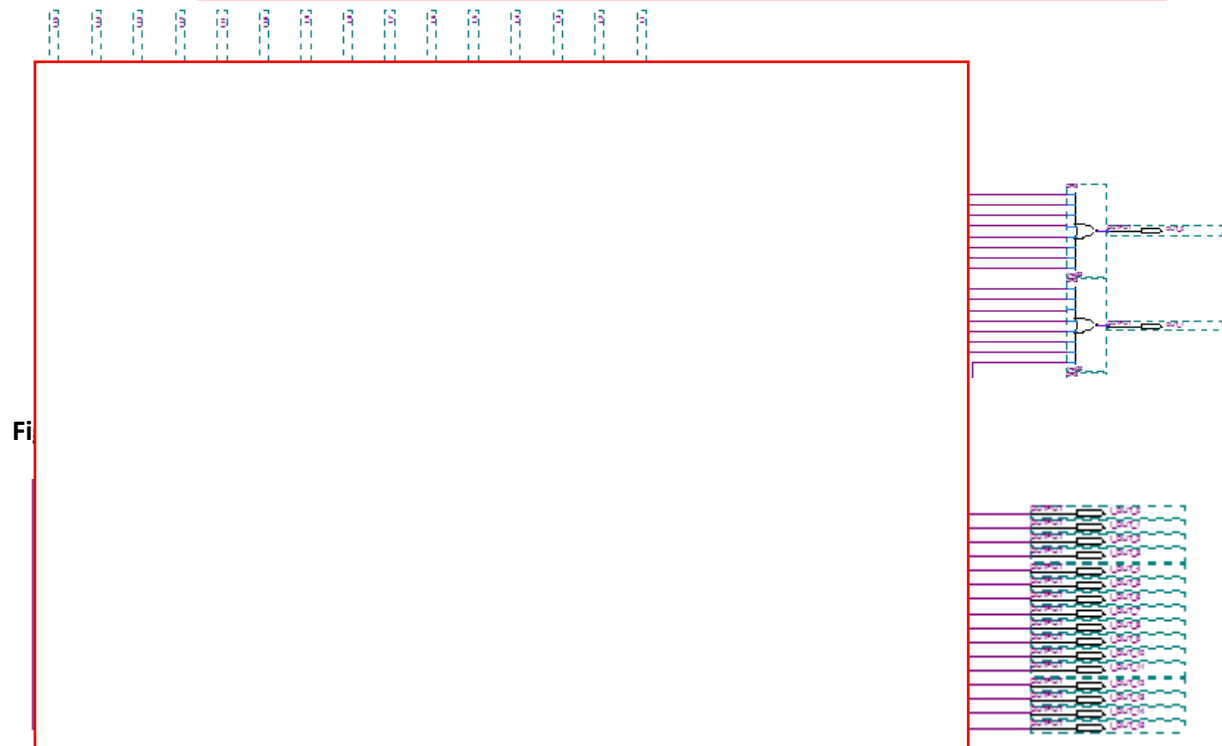

Fi

Figure 3: voltage outputs

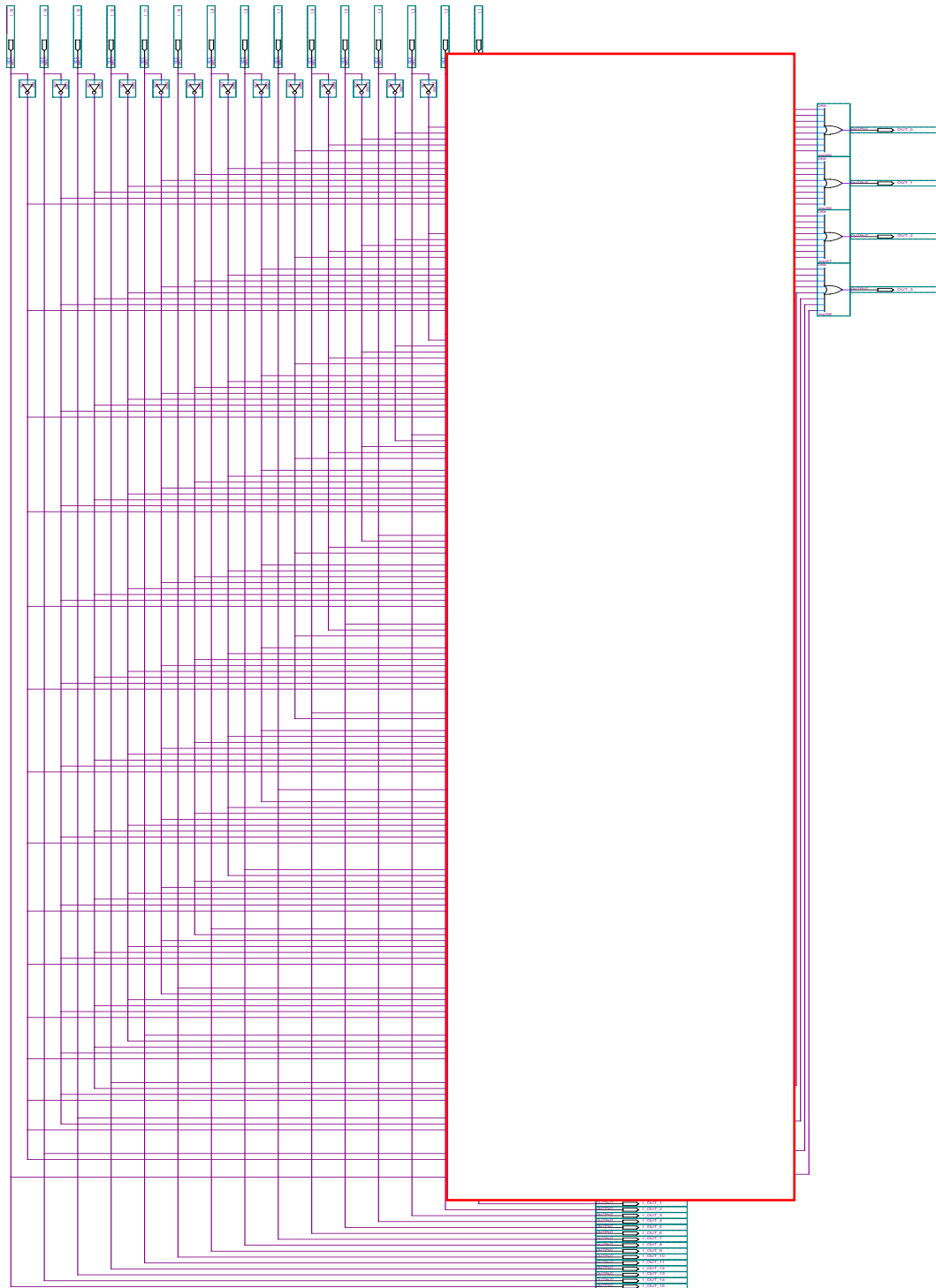

After building the circuit, the voltage of each level was measured in order to compare to the calculated levels (table 2 and figures 5-6). Then, the priority encoder was downloaded to the Altera board, and the

outputs of the circuit were connected to the expansion header on the Altera board. The pin assignments were made, and as the voltage increased, the 4 logic levels increased in order.

Logic level	Trial 1 (V)	Trial 2 (V)
0 0 0 0	0	0
0 0 0 1	0.17758	0.1718
0 0 1 0	0.49732	0.48038
0 0 1 1	0.78455	0.82613
0 1 0 0	1.13348	1.16044
0 1 0 1	1.4524	1.4051
0 1 1 0	1.7228	1.7277
0 1 1 1	2.0955	2.1036
1 0 0 0	2.3584	2.4575
1 0 0 1	2.7118	2.6591
1 0 1 0	2.9829	2.9771
1 0 1 1	3.3469	3.282
1 1 0 0	3.6028	3.6346
1 1 0 1	3.9735	3.9271
1 1 1 0	4.2247	4.268
1 1 1 1	4.5616	4.6434

Table 2: minimum voltage required for each logic level

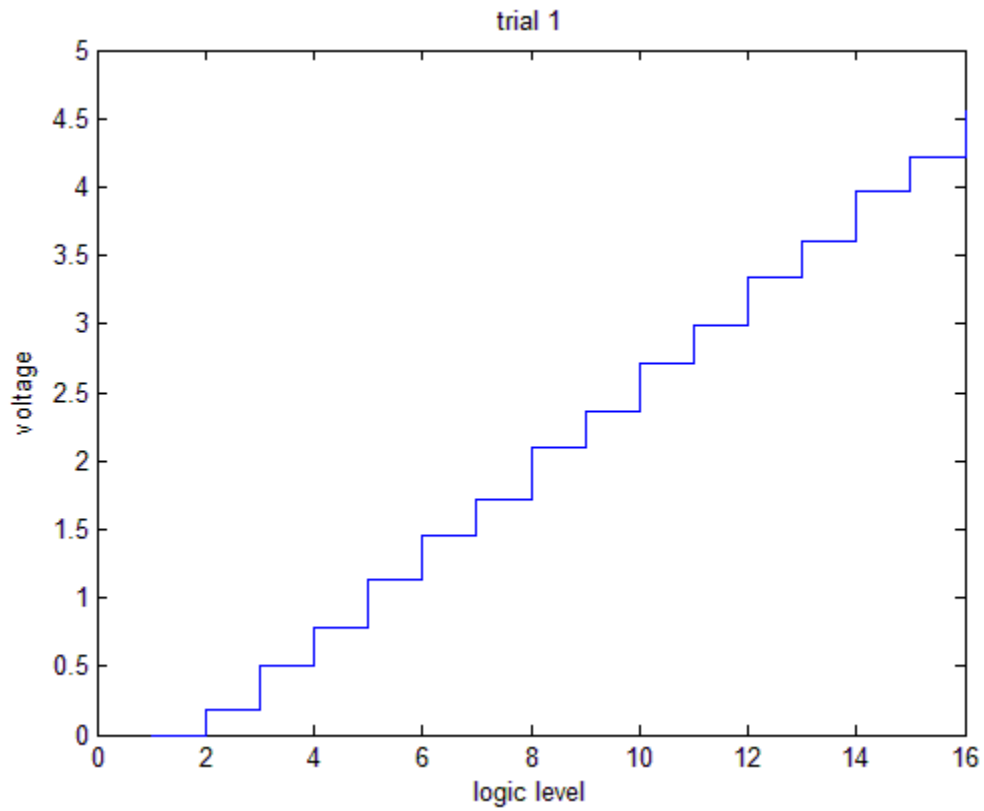


Figure 5: plot of voltage increase


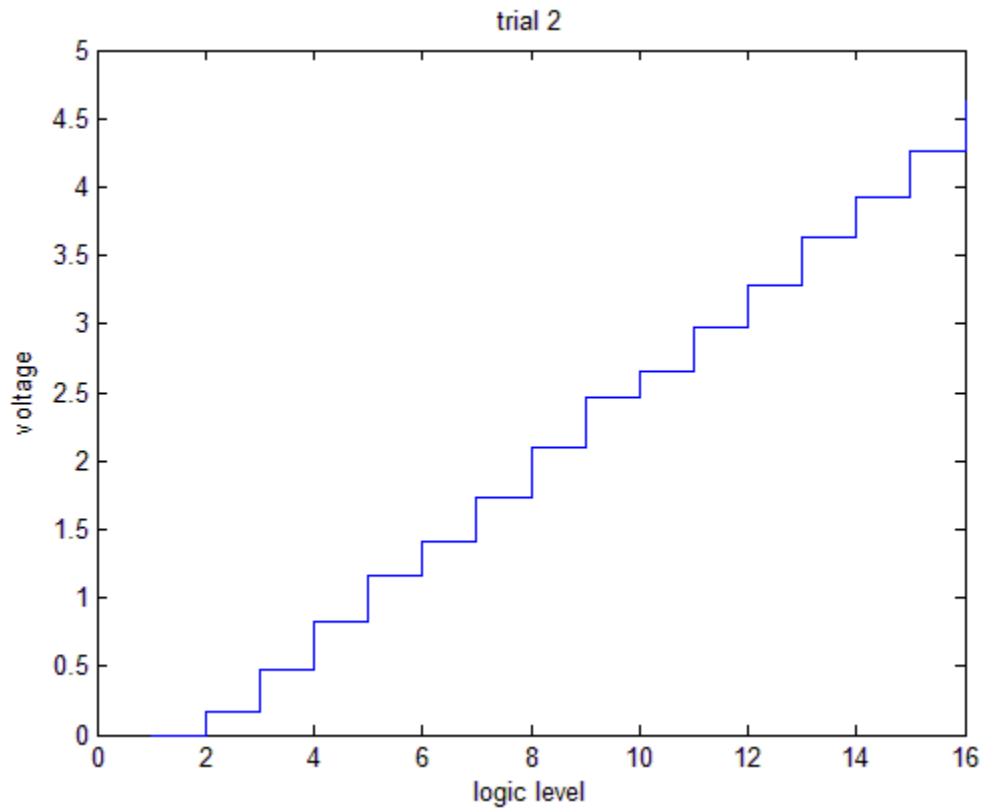


Figure 6: plot of voltage increase trial 2


Conclusion

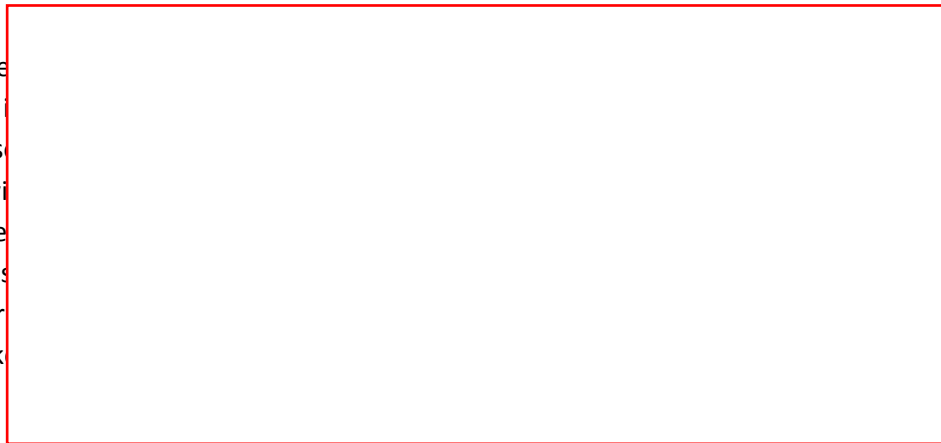This experiment re
reference voltage
analog voltage is s
the comparator wi
smallest voltage le
voltage levels are s
resistors are deter
the circuit, it work



that
s the
The
number of
building

Calculations

 


converter

$1k\Omega$

$$1.5k\Omega = 1k + 500\Omega$$

500Ω

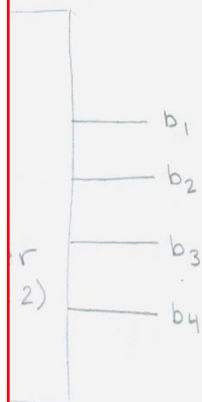

①

$$V_{15} = \frac{29V_{ref}}{16} = 4.53125V$$

$$V_{14} = \frac{27V_{ref}}{16} = 4.21875V$$

$$V_{13} = \frac{25V_{ref}}{16} = 3.90625V$$

$$V_{12} = \frac{23V_{ref}}{16} = 3.59375V$$

$$V_{11} = \frac{21V_{ref}}{16} = 3.28125V$$

$$V_{10} = \frac{19V_{ref}}{16} = 2.96875V$$

$$V_9 = \frac{17V_{ref}}{16} = 2.65625V$$

$$V_8 = \frac{15V_{ref}}{16} = 2.34375V$$

$$V_7 = \frac{13V_{ref}}{16} = 2.03125V$$

$$V_6 = \frac{11V_{ref}}{16} = 1.71875V$$

$$V_5 = \frac{9V_{ref}}{16} = 1.40625V$$

$$V_4 = \frac{V_{ref}}{16R} (3R + R/2) = \frac{7V_{ref}}{16} = 1.09375V$$

$$V_3 = \frac{V_{ref}}{16R} (2R + R/2) = \frac{5V_{ref}}{32} = 0.78125V$$

$$V_2 = \frac{V_{ref}}{16R} (R + R/2) = \frac{3V_{ref}}{32} = 0.46875V$$

$$V_1 = \frac{V_{ref}}{16R} \left(\frac{R}{2}\right) = \frac{V_{ref}}{32} = 0.15625V$$

$$\rightarrow V_{ref} = 5V$$