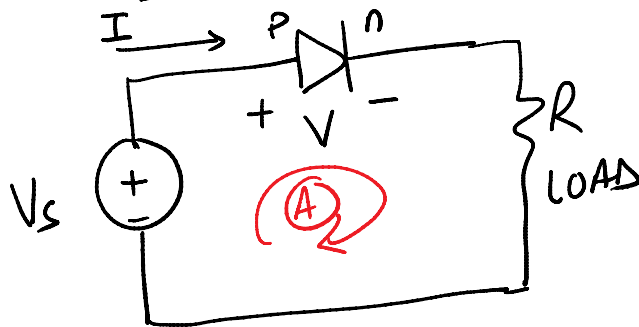


# LECTURE -18

## BASIC DIODE CIRCUIT



TURN ON VOLTAGE  
 $= V_{to}$   
REVERSE SATURATION  
CURRENT  $= -I_0$

KVL LOOP (A)

$$-V_s + V + IR = 0$$


$$V = V_s - IR \quad \text{--- (1)}$$

LOAD LINE EQUATION

$$I = I_0 (e^{qV/KT} - 1) \quad \text{--- (2)}$$

SOLVE (1) AND (2) TO FIND THE OPERATING POINT  $V, I?$

→ Q-POINT

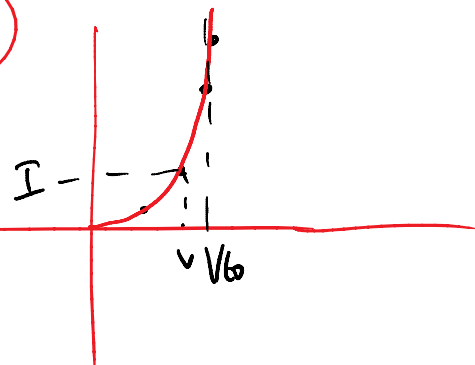

①


FB  $\rightarrow$   $V_S$  IS POSITIVE

IF OPERATING POINT  $V$  AND  $I$   
ARE AWAY FROM THE KNEE OF THE  
CURVE

$$V \approx V_{t0} \Rightarrow V = V_{t0}$$


FROM LOAD LINE EQUATION

$$I = \frac{1}{R} (V_S - V_{t0})$$

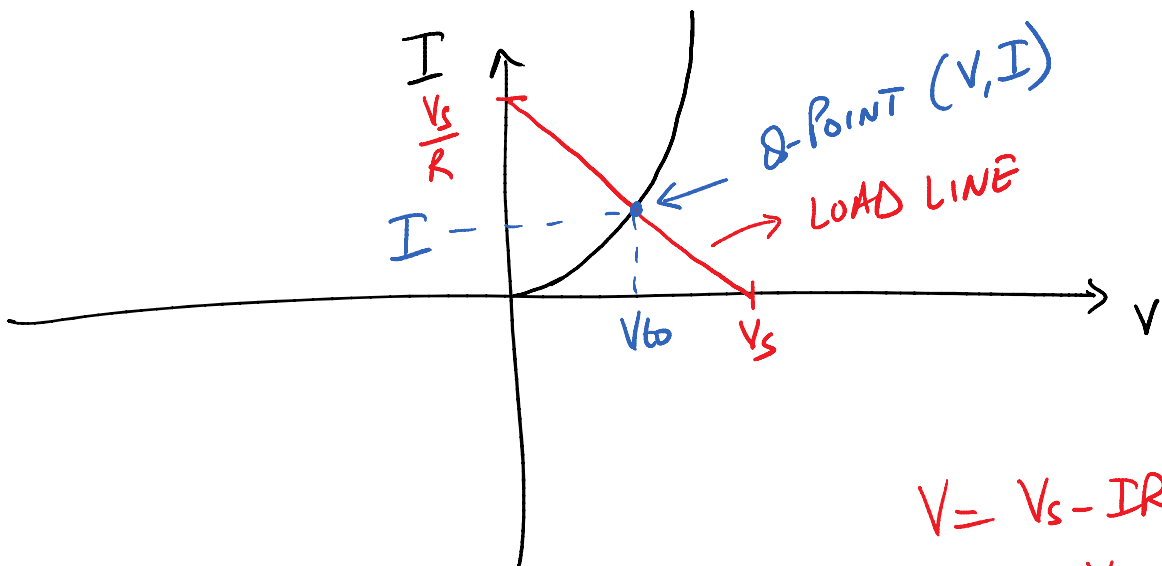


$$V = V_S - IR$$
$$I = 0 \quad V = V_S$$
$$V = 0 \quad I = \frac{V_S}{R}$$

Friday, January 25, 2013  
11:15 AM

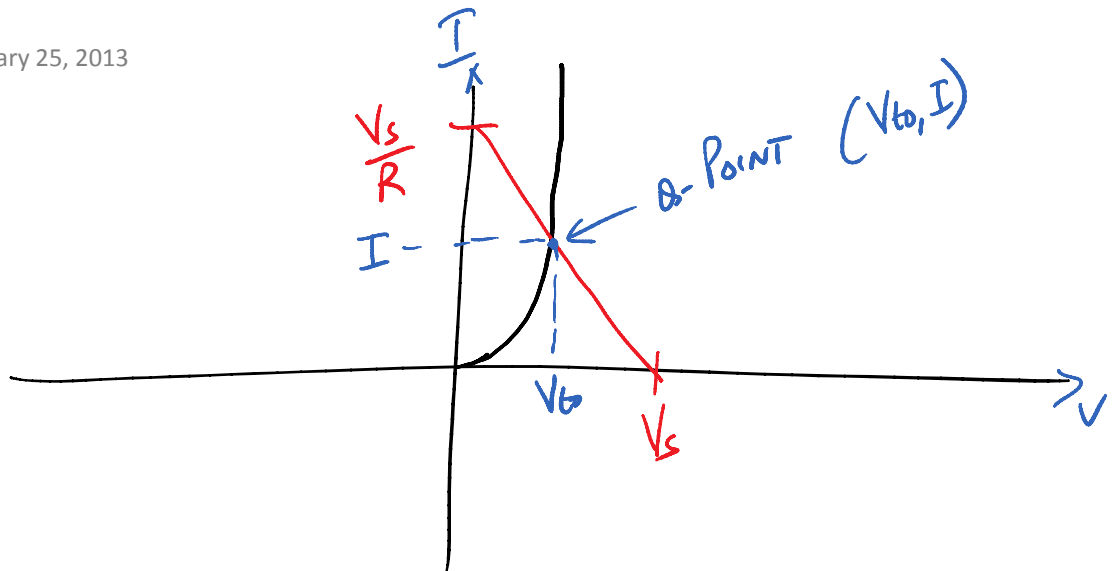


②

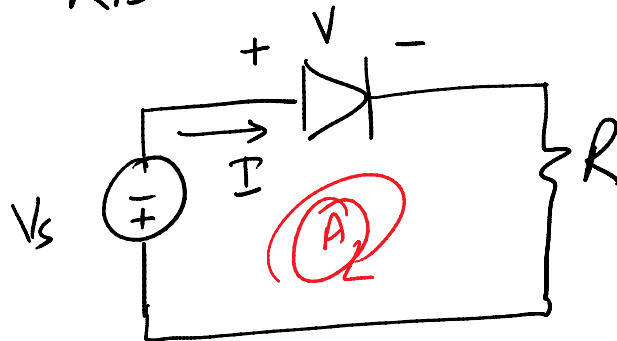RB CASE  $\rightarrow$   $V_s$  IS NEGATIVE



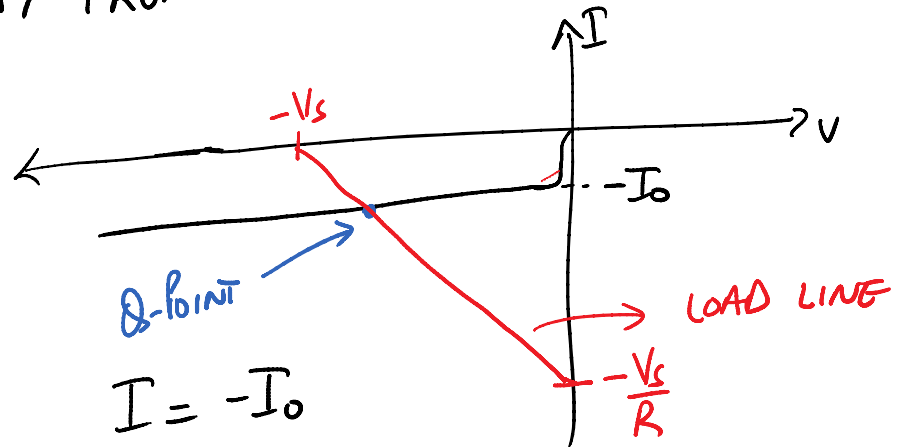IF THE ~~ARE~~ OPERATING POINT  $V$  AND  $I$  ARE AWAY FROM THE KNEE OF THE CURVE



KVL LOOP (A)

$$V_s + V + IR = 0$$

$$V = -V_s - IR$$

$\rightarrow$  LOAD LINE EQUATION

$V=0$


$V_s = -IR$

$\Rightarrow I = -\frac{V_s}{R}$

$I=0$

$V = -V_s$

Friday, January 25, 2013  
11:19 AM

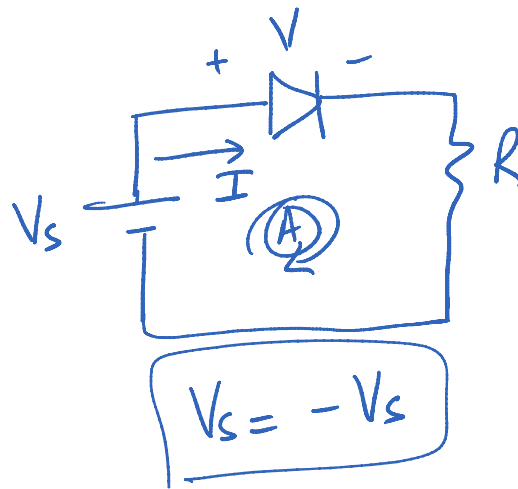

$$I = -I_0$$

$$-V_s + V + IR = 0$$

$$V_s = V + IR$$

$$V = 0$$

$$V_s = IR$$

$$\Rightarrow I = \frac{V_s}{R}$$


$$V_s = -V_s$$

$$= -\frac{V_s}{R}$$

$$I = 0$$

$$V = V_s = -V_s$$

RB → BUT WITH BREAKDOWN! → 2 CASES!

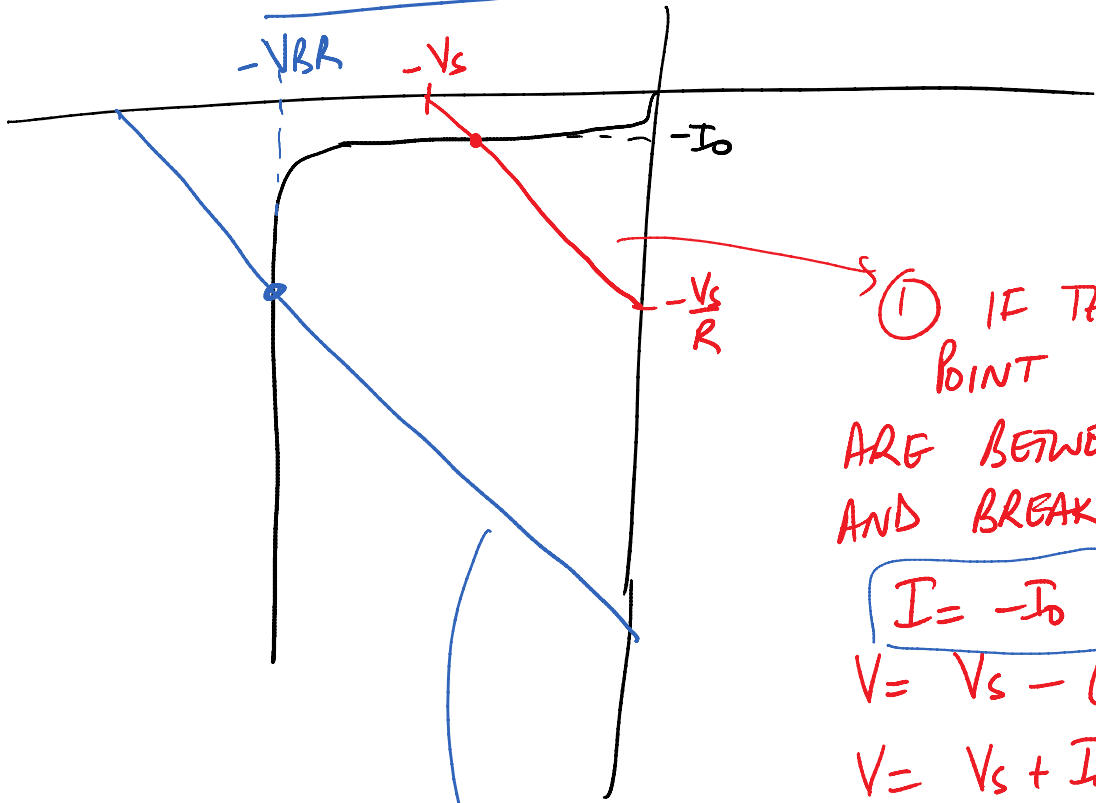

① IF THE OPERATING POINT V AND I ARE BETWEEN THE KNEE AND BREAKDOWN

$$I = -I_0$$

$$V = V_s - (-I_0 R)$$

$$V = V_s + I_0 R$$

↳ NEGATIVE

② IF OPERATING V AND I ARE IN THE BREAKDOWN REGION

$$V = -V_{BR}$$

$$I = \frac{1}{R} (V_s - (-V_{BR}))$$