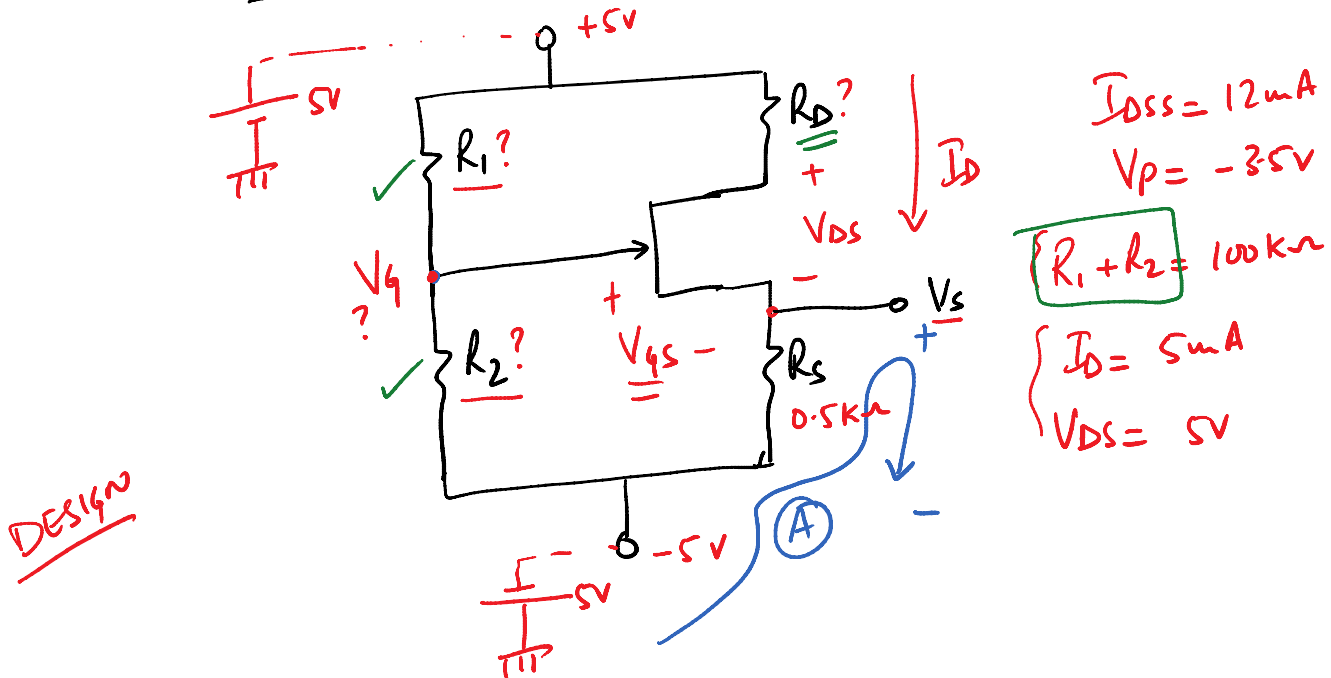


# LECTURE - 35

## VOLTAGE DIVIDER BIASING CIRCUIT



ASSUME TRANSISTOR IS IN SAT.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$5\text{mA} = 12\text{mA} \left(1 - \frac{V_{GS}}{-3.5}\right)^2$$

$$V_{GS} = -1.24\text{V}$$

KVL LOOP (A)


$$5 - I_D R_S + V_S = 0$$

$$V_S = (5\text{mA})(0.5\text{k}\Omega) - 5 = -2.5\text{V}$$

$$V_{GS} = V_G - V_S$$

$$V_G = V_{GS} + V_S = -1.24 - 2.5 = -3.74\text{V}$$

Tuesday, March 12, 2013  
1:13 PM

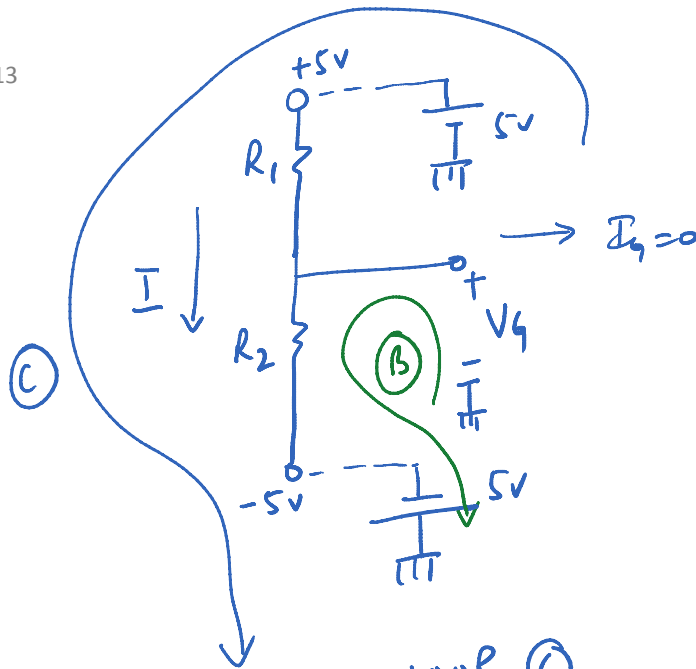

KVL LOOP (C)

$$-5 + I(R_1 + R_2) - 5 = 0$$

$$I = \frac{10}{R_1 + R_2}$$

KVL LOOP (B)

$$5 - IR_2 + V_q = 0$$

$$V_q = IR_2 - 5$$

$$V_q = \left( \frac{10}{R_1 + R_2} \right) R_2 - 5$$

$$-3.74 = \frac{10}{100K} R_2 - 5 \Rightarrow R_2 = \underline{\underline{12.6K\Omega}}$$

$$R_1 = \underline{\underline{87.4K\Omega}}$$

KVL D-S LOOP

$$-5 + I_D R_D + V_{DS} + I_D R_S - 5 = 0$$


$$R_D = \frac{10 - V_{DS} - I_D R_S}{I_D} = \frac{10 - 5 - (5\mu)(10.5K)}{5\mu}$$

$$I_D$$
$$R_D = \underline{\underline{0.5 \text{ k}\Omega}}$$


sm

$$V_{DS(SAT)} = V_{GS} - V_P = -1.24 - (-3.5) = 2.26 \text{ V}$$

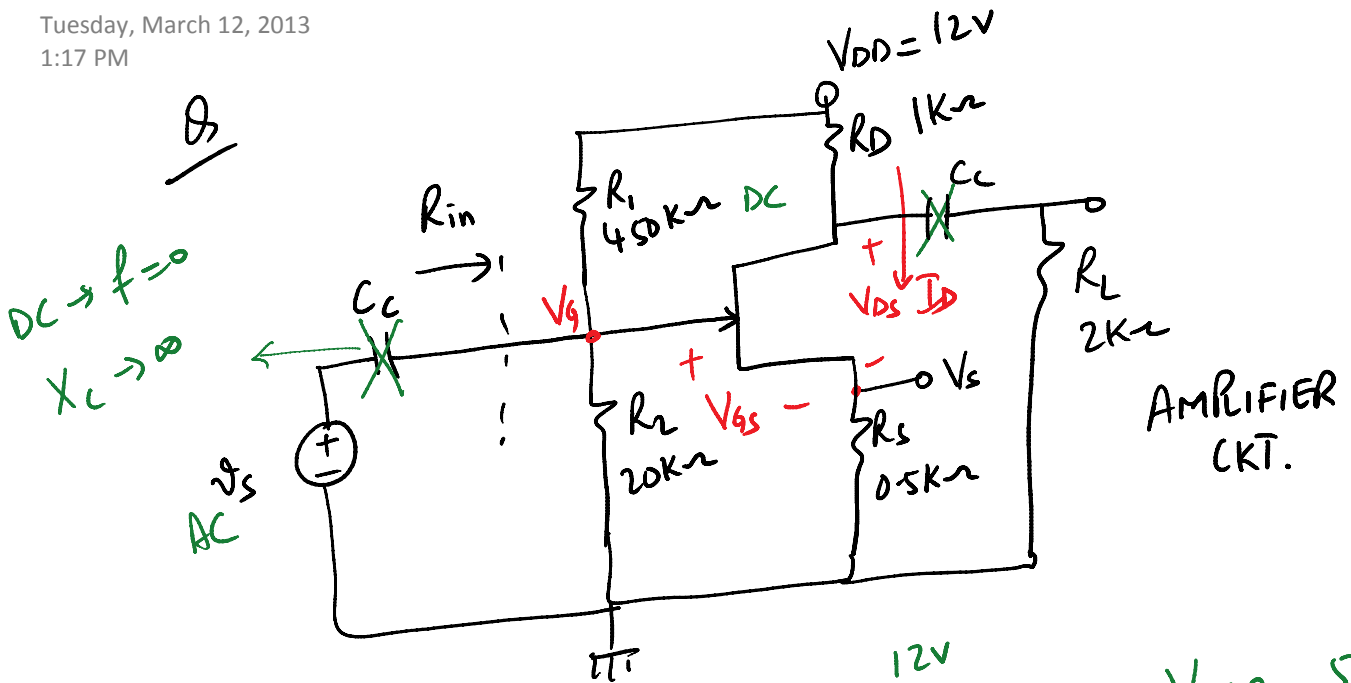$V_{DS} = V_{DS(SAT)} \therefore \text{TR. IS IN SAT.}$



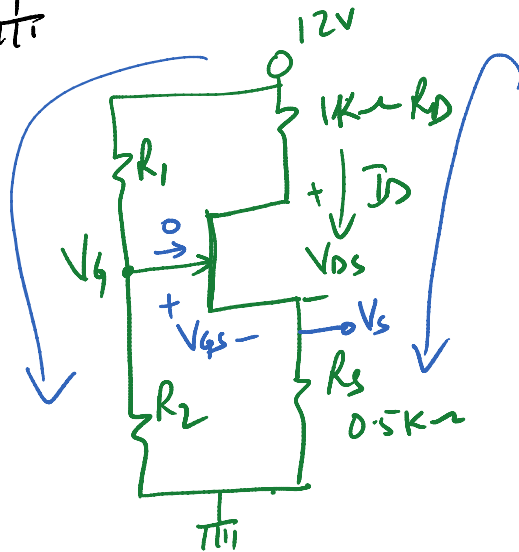$\frac{\partial}{\partial}$   
DC  $\rightarrow f=0$   
 $X_C \rightarrow \infty$



$V_{DSQ} = 5V$   
 $I_{DQ} = 10\mu A$   
 $V_P?$

KVL DC LOOP

$$V_{DD} = I_{DQ} R_D + V_{DS} + I_{DQ} R_S$$

$$I_{DQ} = \frac{V_{DD} - V_{DS}}{R_D + R_S} = \frac{12 - 5}{1K + 0.5K} = 4.67\mu A$$

$$\rightarrow V_S = I_{DQ} R_S = (4.67\mu A)(0.5K) = 2.33V$$

$$\rightarrow V_G = V_{DD} \left( \frac{R_2}{R_1 + R_2} \right) = \frac{12(20K)}{450K + 20K} = 0.511V$$

$$\therefore V_C = 0.511 - 2.33 = \underline{\underline{-1.82V}}$$

$$V_{GS} = V_G - V_S = 0.511 - 2.33 = \underline{\underline{-1.82V}}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$4.65\text{mA} = 10\text{mA} \left(1 - \frac{(-1.82)}{V_P}\right)^2$$

$$V_P = -5.75V$$