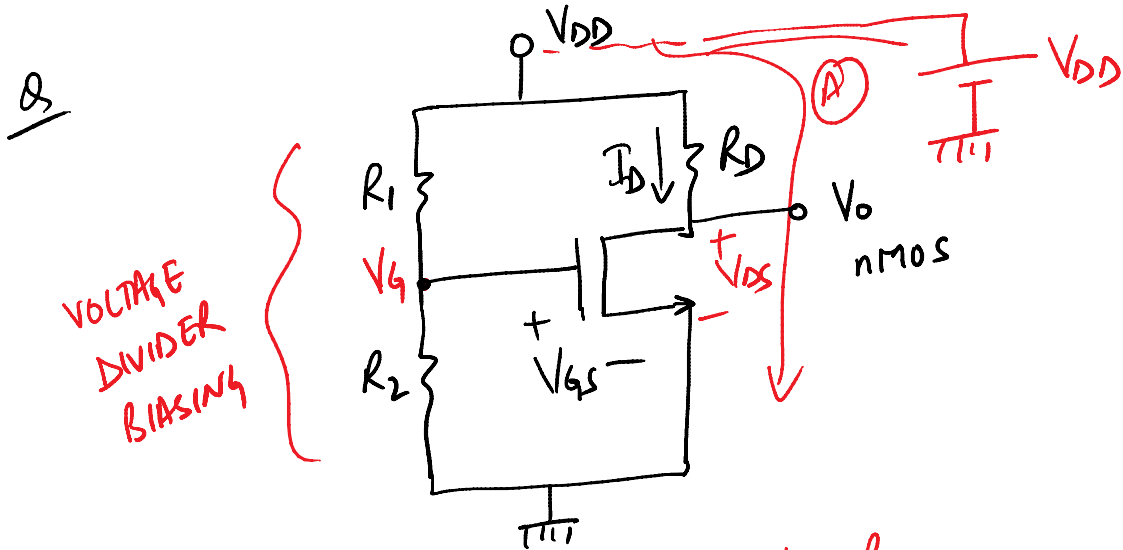


# LECTURE - 38



$$V_G = V_{GS} = \frac{V_{DD} R_2}{R_1 + R_2}$$

IF  $V_{GS} > V_{TN}$  AND WE ARE IN SAT. REG.  
 $V_{DS} > V_{DS(SAT)} = V_{GS} - V_{TN}$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

KVL LOOP A

$$V_{DS} = V_{DD} - I_D R_D \quad [LL \text{ EQUATION}]$$

$P_T \rightarrow$  POWER DISSIPATED IN THE TRANSISTOR

$$P_T = V_{DS} I_D$$

$$R_1 = 30k\Omega \quad R_2 = 20k\Omega \quad R_D = 20k\Omega \quad V_{DD} = 5V$$
$$V_{TN} = 1V \quad K_n = 0.1 \text{ mA/V}^2$$

$$V_G = V_{GS} = \left( \frac{20k}{20k + 30k} \right) 5 = 2V$$

ASSUMING TR. IS IN SAT.

$(Q\text{-Point})$   $(V_{DS}, I_D)$

$$\begin{cases} I_D = K_n (V_{GS} - V_{TN})^2 = (0.1 \text{ mA/V}^2) (2 - 1)^2 = \underline{\underline{0.1 \text{ mA}}} \\ V_{DS} = 5 - (0.1 \text{ mA}) (20k) = \underline{\underline{3V}} \end{cases}$$

$$P_T = V_{DS} I_D = (0.1) (3) = \underline{\underline{0.3 \text{ mW}}}$$


$$V_{DS(SAT)} = V_{GS} - V_{TN} = 2 - 1 = 1V$$

$$V_{DS} > V_{DS(SAT)} \quad \therefore \text{TR. IS IN SAT.}$$

\* FOR TURN-ON  $V_{GS} > V_{TN}$

\* FOR SAT.  $V_{DS} > V_{DS(SAT)}$

PMOS

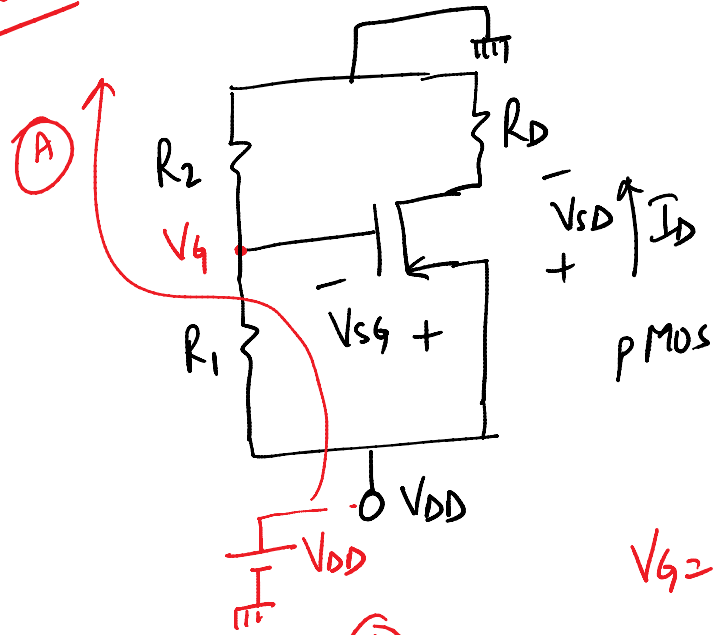

KVL LOOP (A)

$$V_g = \frac{V_{DD} R_2}{R_1 + R_2}$$

$$-V_{DD} + V_{sg} + V_g = 0$$

$$V_{sg} = V_{DD} - V_g$$

ENHANCEMENT MODE

PMOS  $V_{TP} < 0$   $V_{sg} \rightarrow$  POSITIVE  
 $V_{gs} \rightarrow$  NEGATIVE

TO TURN ON

$$V_{gs} < V_{TP}$$

IF IN SAT.

$$I_D = K_p (V_{sg} + V_{TP})^2$$

$$V_{sd} = V_{DD} - I_D R_D \quad \{\text{KVL EQUATION}\}$$

$$\text{SAT.} \quad V_{sd} > V_{sd}(\text{SAT}) = V_{sg} + V_{TP}$$

Ex

$$R_1 = R_2 = 50k\Omega \quad V_{DD} = 5V \quad R_D = 7.5k\Omega$$
$$V_{TP} = -0.8V \quad K_P = 0.2mA/V^2$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{50k}{50k + 50k} \right) 5 = 2.5V$$

$$V_{SG} = V_{DD} - V_G = 5 - 2.5 = 2.5V$$

ASSUME TR. IS IN SAT.

$$I_D = K_P (V_{SG} + V_{TP})^2 = (0.2m)(2.5 - 0.8)^2$$
$$= 0.578mA$$

$$V_{SD} = V_{DD} - I_D R_D = 5 - (0.578m)(7.5k)$$
$$= \underline{0.665V}$$

$$V_{SD(SAT)} = V_{SG} + V_{TP} = 2.5 - 0.8 = \underline{1.7V}$$

$$V_{SD} < V_{SD(SAT)} \rightarrow \underline{\therefore TR. IS NOT IN SAT.!$$

$$I_D = K_P [2 (V_{SG} + V_{TP}) V_{SD} - V_{SD}^2] \quad \text{TRIODE}$$

$$\begin{matrix} \curvearrowright \\ V_{SD} = \frac{V_{DD} - I_D R_D} \end{matrix}$$

$$\therefore I_D = K_P [2 (V_{SG} + V_{TP}) (V_{DD} - I_D R_D) - (V_{DD} - I_D R_D)^2]$$

$$I_D = (0.2 \text{m}) [2 (2.5 - 0.8) (5 - I_D (7.5 \text{k})) - (5 - I_D (7.5 \text{k}))^2]$$

QUADRATIC EQ.


SOLVE FOR  $I_D$

TWO VALUES OF  $I_D$  WHICH WILL GIVE TWO  
VALUES OF  $V_{SD}$

CHOOSE THE VALUE OF  $I_D$  THAT LEADS TO A  
VALUE OF  $V_{SD}$ , WHICH WILL MAKE THE  
TRANSISTOR IN TRIODE REGION

$I_D = 0.515 \text{ mA}$
$V_{SD} = 1.14 \text{ V}$

Q

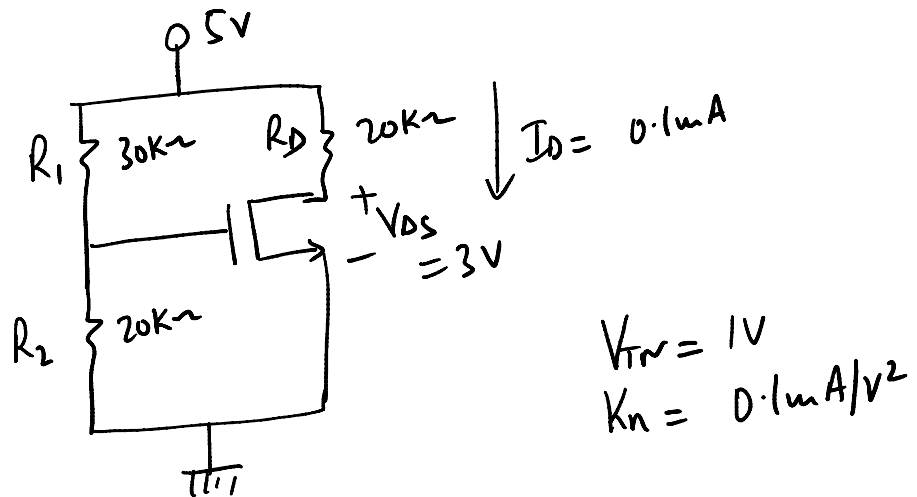

$$V_{DS} = V_{DD} - I_D R_D \rightarrow \text{LL EQUATION}$$

$$= 5 - I_D (20K)$$

$$I_D = \frac{5}{20K} - \frac{V_{DS}}{20K}$$

FIND THE TRANSITION POINT?

AT TRANSITION POINT

$$V_{DS} = V_{DS(CAT)} = V_{GS} - V_{TN} = V_{DD} - I_D R_D$$

$$I_D = \frac{K_n (V_{GS} - V_{TN})^2}{2}$$

$$V_{GS} - V_{TN} = V_{DD} - (K_n) R_D (V_{GS} - V_{TN})^2$$

$$K_n R_D (V_{GS} - V_{TN})^2 + (V_{GS} - V_{TN}) - 5 = 0$$

QUADRATIC EQUATION

SOLVE FOR  $V_{GS} - V_{TN}$

$$V_{GS} - V_{TN} = 1.35 = V_{DS}$$

$$\therefore V_{GS} = 2.35 \text{ V}$$

$$I_D = (0.1 \text{ mA}) (2.35 - 1)^2 = 0.182 \text{ mA}$$

For  $V_{GS} < 2.35 \text{ V}$  TR IS IN SAT.

$V_{GS} > 2.35 \text{ V}$  TR IS IN TRIODE REGION

As  $V_{GS} \uparrow$   $I_D \uparrow$   $V_{DS} \downarrow$