


LECTURE - 39

OPERATIONAL AMPLIFIERS

[OP-AMP]

COMPLEX DEVICE → MODELED AS A VCVS

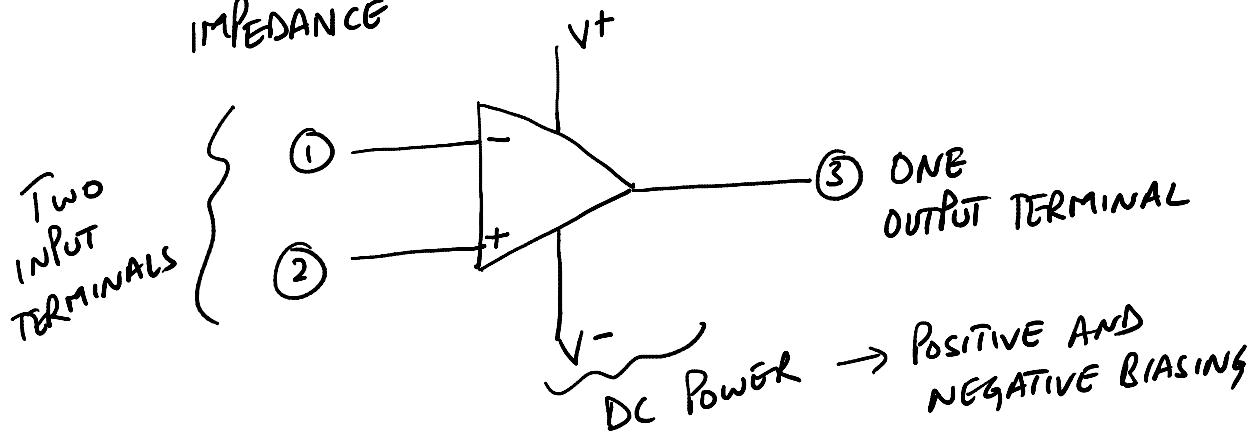HIGH GAIN, HIGH INPUT IMPEDANCE, LOW OUTPUT IMPEDANCE




BIAS → ACTIVE REGION FOR AMPLIFICATION!

- TERMINAL → INVERTING TERMINAL


+ TERMINAL → NON-INVERTING TERMINAL

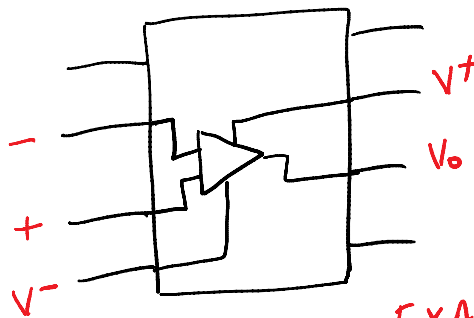20-30 TRANSISTORS FORM AN OP-AMP AS A I.C




EXAMPLE IC FOR 1 OP-AMP

EQUIVALENT CIRCUIT

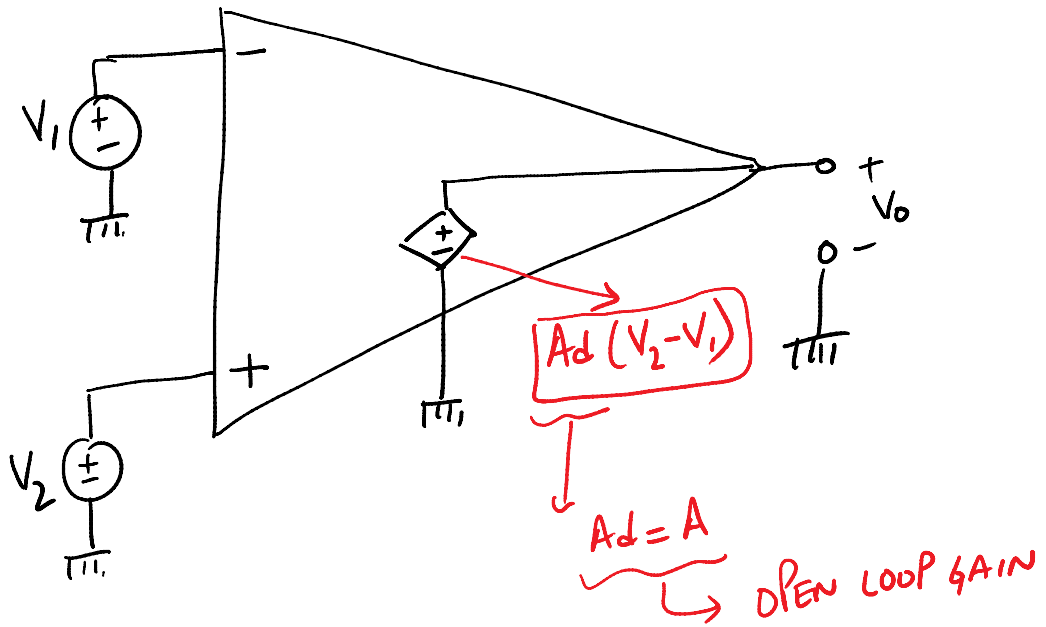

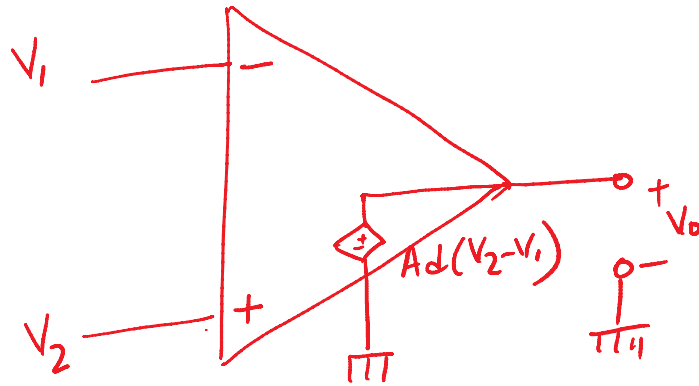
IDEAL OP-AMP \rightarrow SENSES THE DIFFERENCE BETWEEN TWO INPUT SIGNALS AND AMPLIFIES THE DIFFERENCE TO PROVIDE AN OUTPUT



IDEAL

- ① RESISTANCE BETWEEN $-$ + TERMINAL IS $\infty \Omega$ (R_{in}) \leftarrow INPUT IMPEDANCE
- ② $A_d \rightarrow$ OPEN LOOP GAIN IS VERY LARGE
IDEALLY $\infty \rightarrow$ PRACTICALLY $\rightarrow 200,000 - 300,000$
- ③ IF $V_1 = V_2$ O/P = 0
IF $V_1 = V_2 \neq 0 \rightarrow$ COMMON MODE INPUT
IDEAL COMMON MODE OUTPUT = 0
COMMON MODE REJECTION RATIO!
(CMRR)

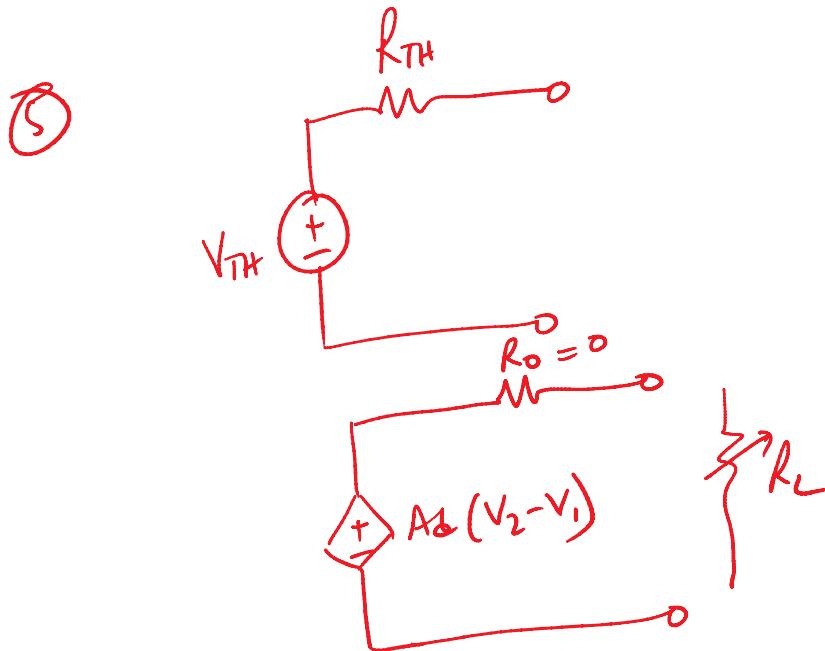
④ V^+ AND V^- (DIRECTLY COUPLED, NO COUPLING CAPACITORS NEEDED)
 DC INPUT SIGNALS ALLOWED \rightarrow DC OUTPUT



$R_o \rightarrow$ OUTPUT RESISTANCE $= 0 \approx 0$
 DIRECTLY CONNECTED TO THE DEPENDENT
 VOLTAGE SOURCE \rightarrow O/P VOLTAGE IS INDEPENDANT
 OF LOAD!

PRACTICAL

$$V_d = V_2 - V_1$$


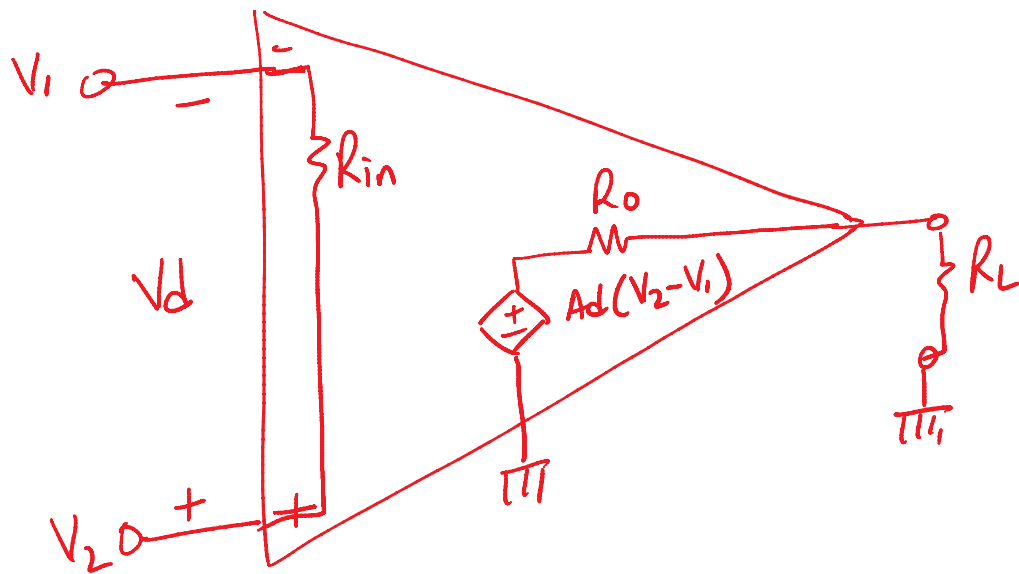


$$A_d \geq 10,000$$

$$R_{in} \geq 100\text{ k}\Omega$$


$$R_{out} \leq 100\ \Omega$$

Friday, March 22, 2013
11:06 AM

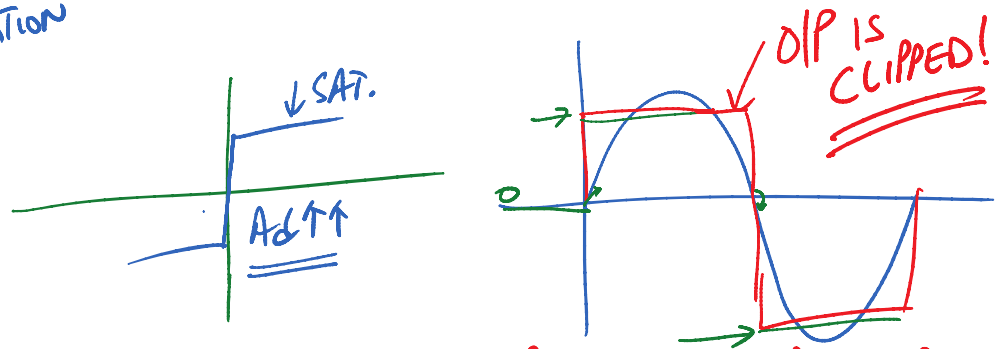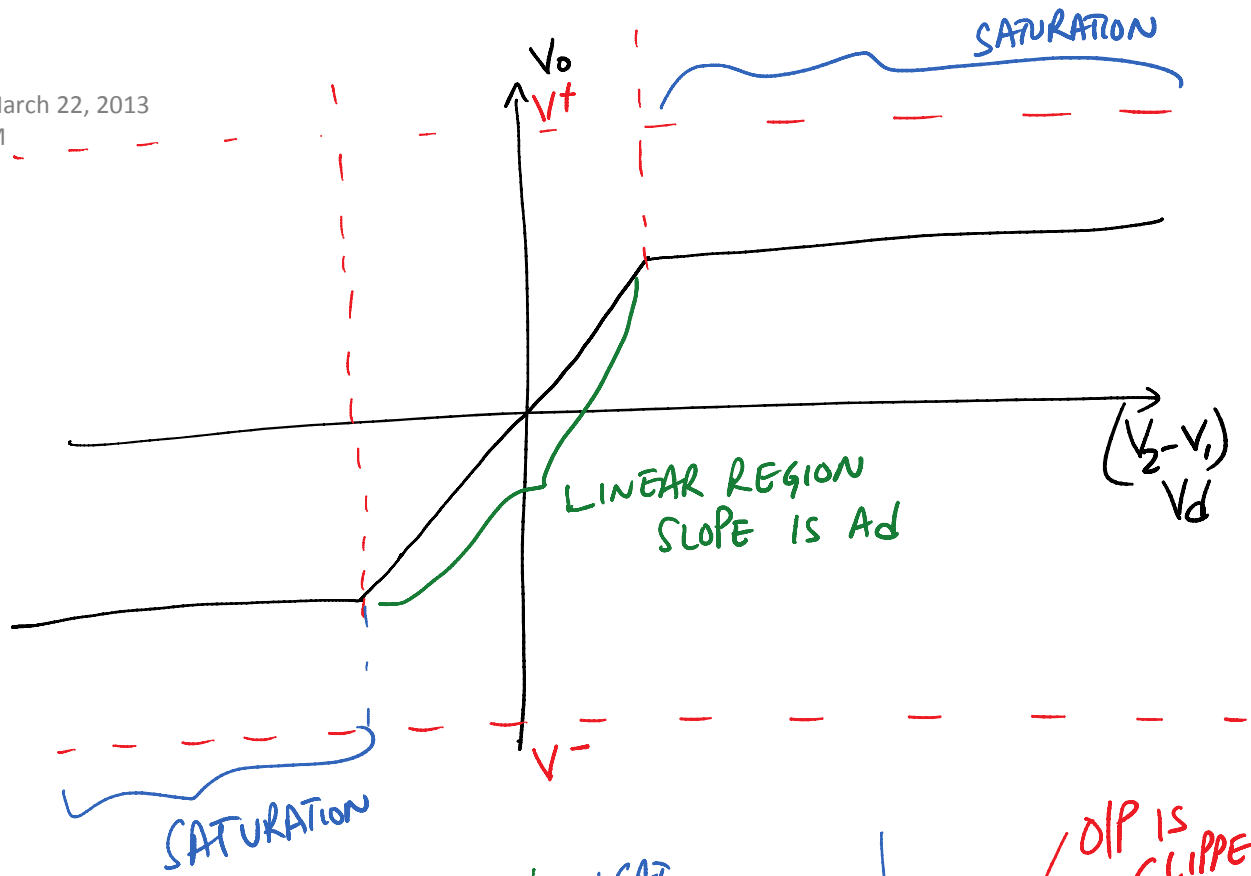

* APPLICATION OF USING THE OP-AMP IN OPEN LOOP
→ ZERO CROSSING DETECTOR

OUTPUT CURRENTS

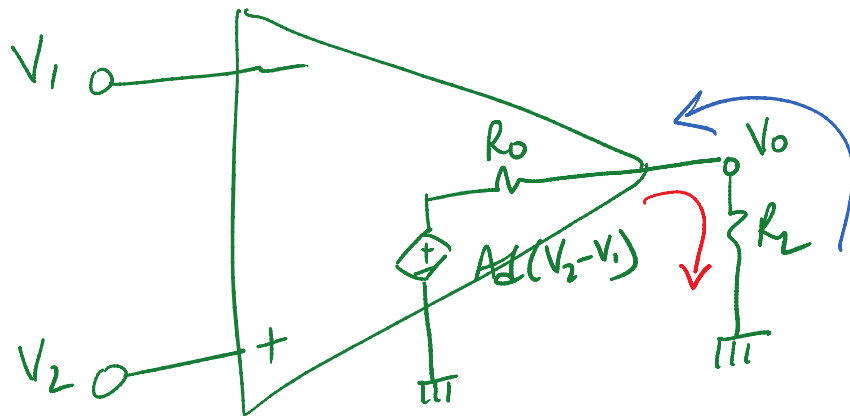

IF $V_o > 0 \rightarrow$ LOAD CURRENT IS SUPPLIED BY OP-AMP

IF $V_o < 0 \rightarrow$ OP-AMP SINKS THE LOAD CURRENT

TYPICAL VALUES = $\pm 20\text{mA}$