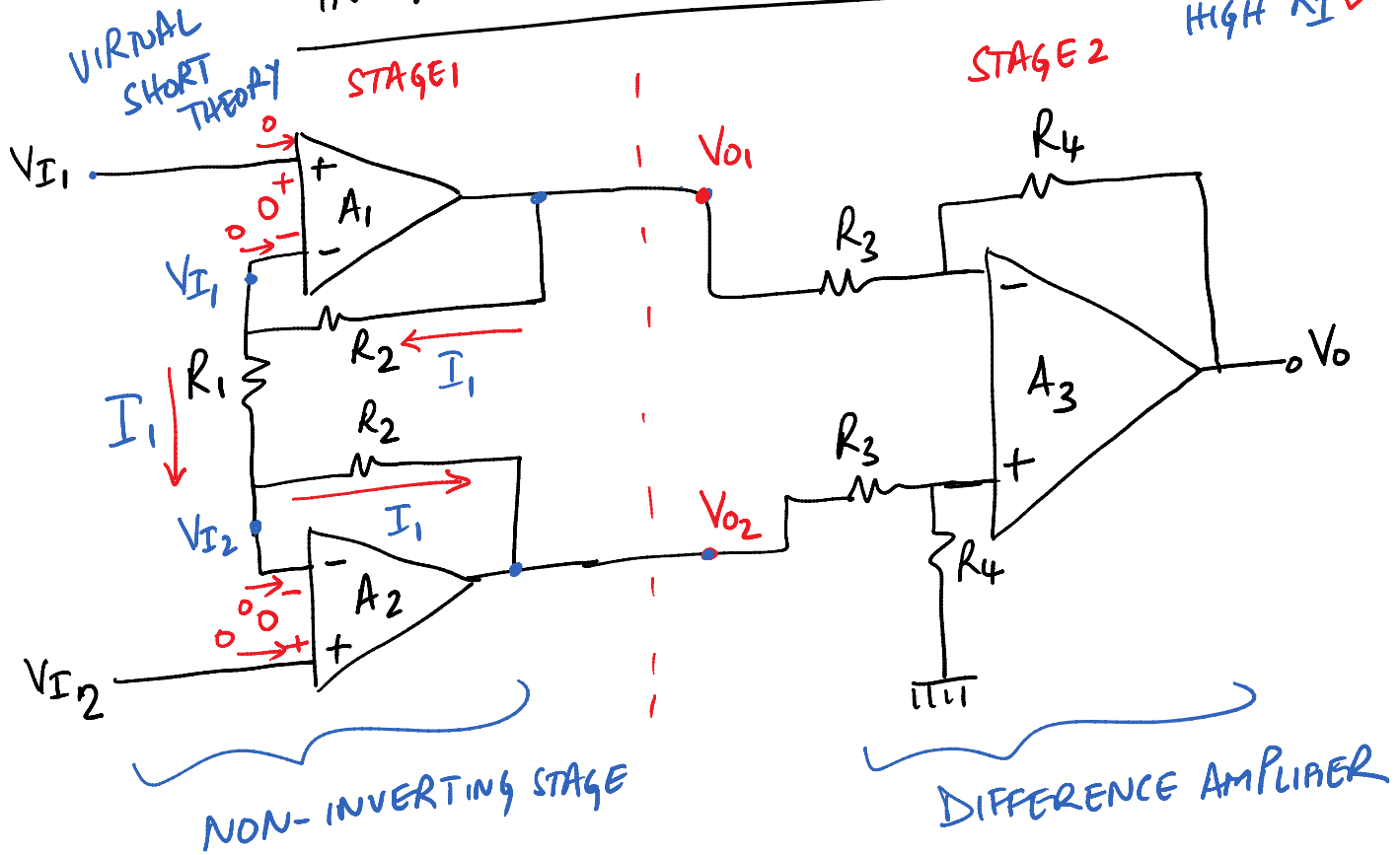


# LECTURE - 42

## DIFFERENCE AMPLIFIER

↳ NOT POSSIBLE TO GET HIGH GAIN AND HIGH  $R_I$

## INSTRUMENTATION AMPLIFIER → HIGH GAIN AND HIGH $R_I$ ✓



$$I_1 = \frac{V_{I1} - V_{I2}}{R_1}$$

$$I_1 = \frac{V_{O1} - V_{O2}}{2R_2 + R_1}$$

$$V_{O1} - V_{O2} = \frac{2R_2 + R_1}{n} (V_{I1} - V_{I2})$$


$$\frac{V_{o1} - V_{o2}}{R_1} = \frac{2R_2 + R_1}{R_1} (V_{I1} - V_{I2})$$

$$V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1})$$

$$\therefore V_o = \frac{R_4}{R_3} \left( \frac{2R_2 + R_1}{R_1} \right) (V_{I2} - V_{I1})$$

\* SINCE INPUT STAGE IS NON INVERTING  
 $R_I = \infty$

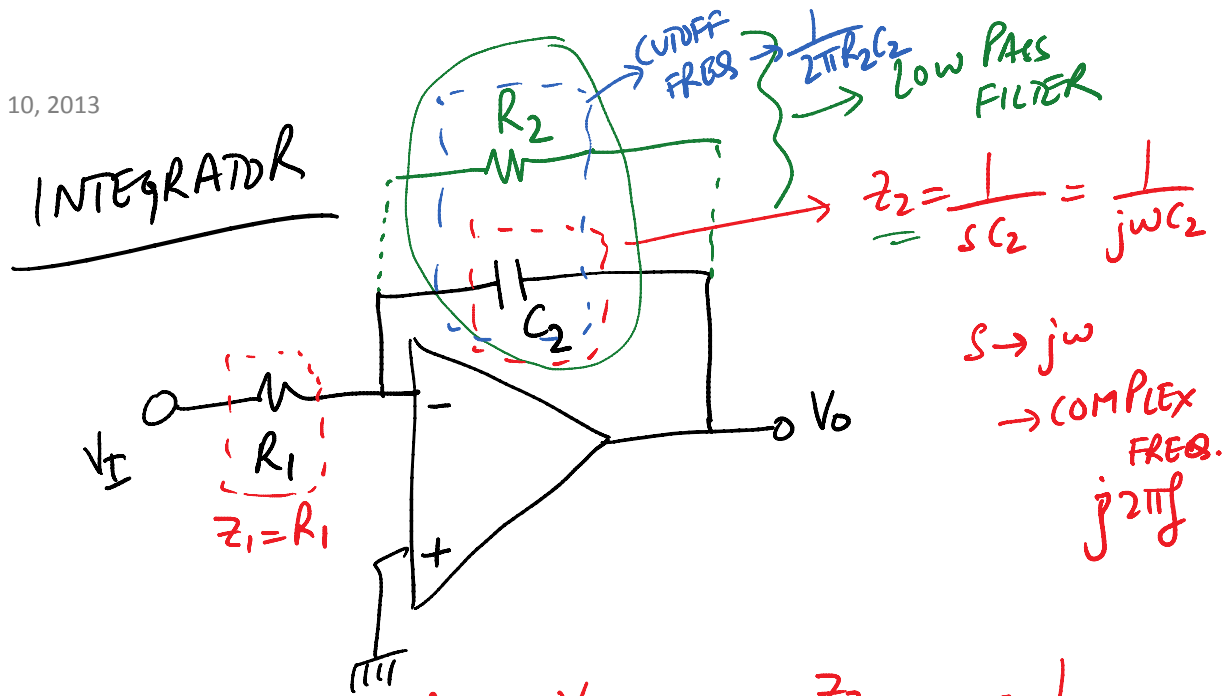\*  $V_o$  DEPENDS ON  $R_1 \rightarrow$  GAIN IS VARIED  
USING ONLY  $R_1$




$$A_v = \frac{V_o}{V_I} = -\frac{z_2}{z_1} = -\frac{1}{s R_1 C_2}$$


$V_c \rightarrow$  VOLTAGE ACROSS CAPACITOR AT  $t=0$

$$\rightarrow V_o = -\frac{1}{s R_1 C_2} V_I$$


$$\frac{d}{dt} \rightarrow s \rightarrow \frac{1}{s} = \int$$
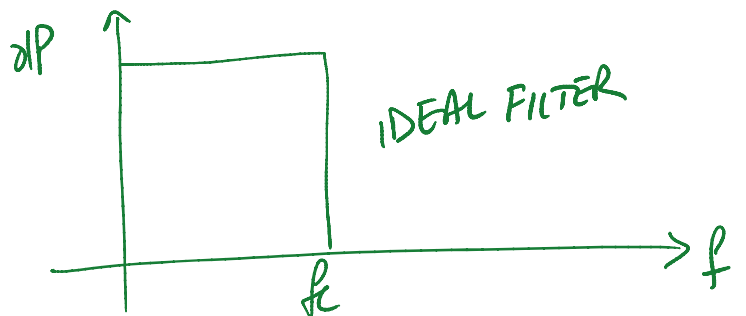
$$V_o = V_c - \frac{1}{R_1 C_2} \int_0^t V_I(t) dt$$



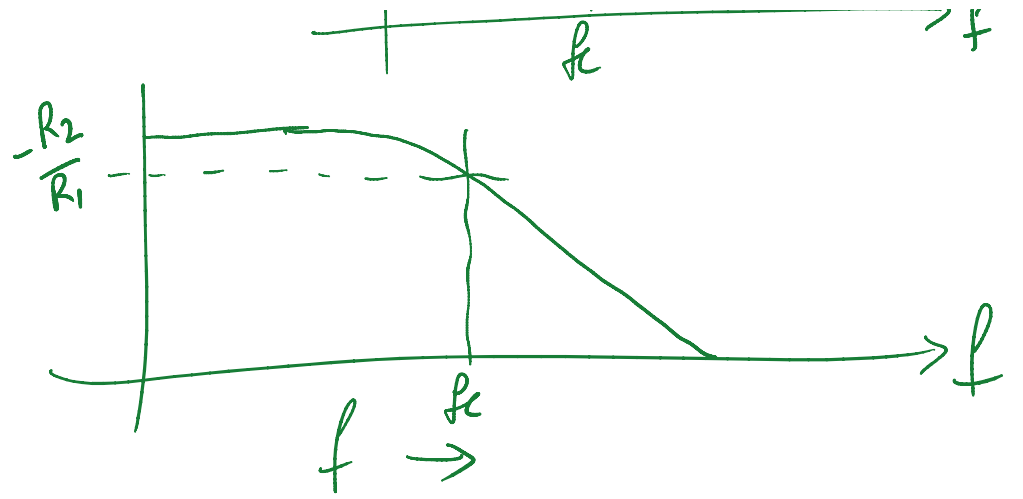


# DIFFERENTIATOR

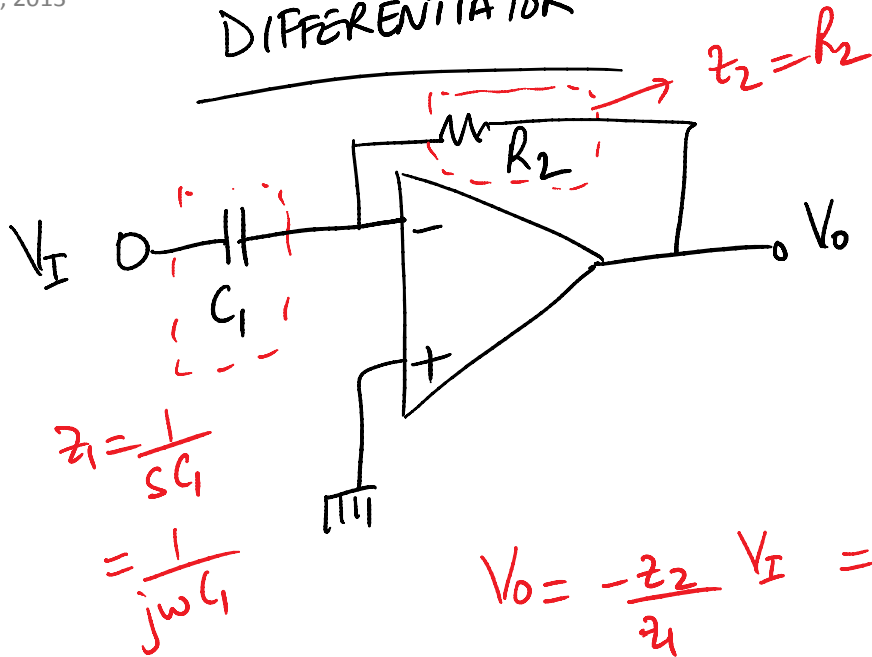


$\frac{d}{dt} \rightarrow s$



$V_O(t) = -R_2C_1 \frac{d}{dt} V_I(t)$

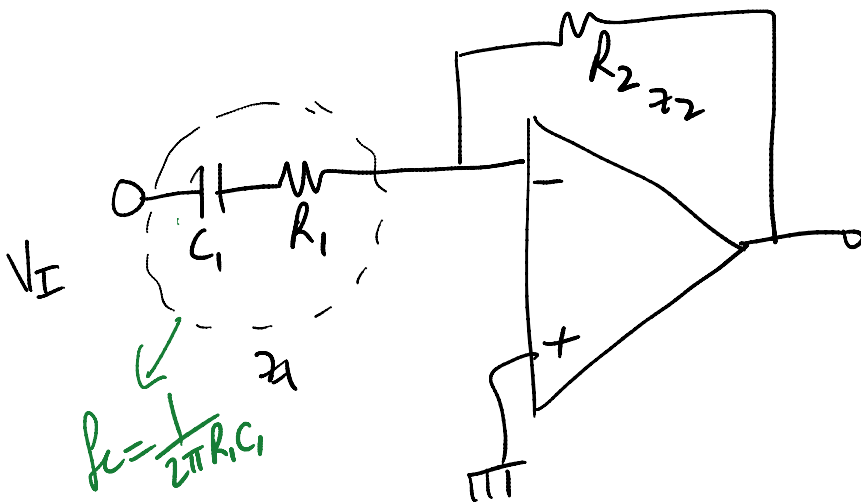


HIGH PASS FILTER

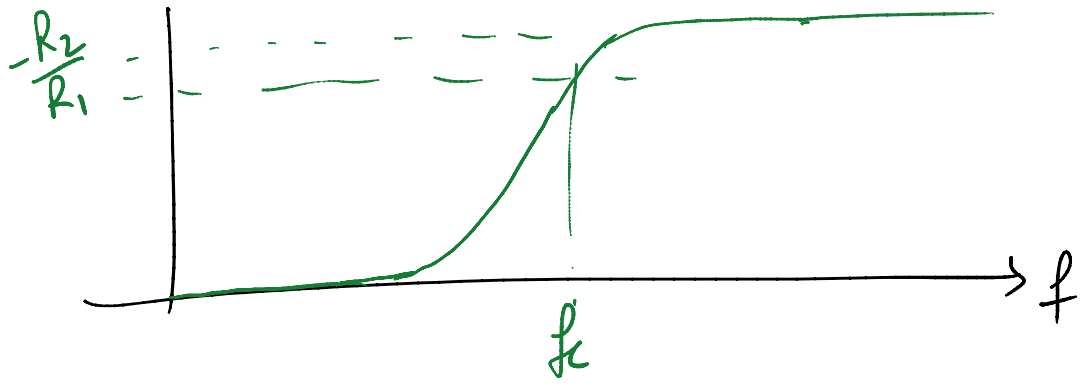

Wednesday, April 10, 2013  
11:14 AM

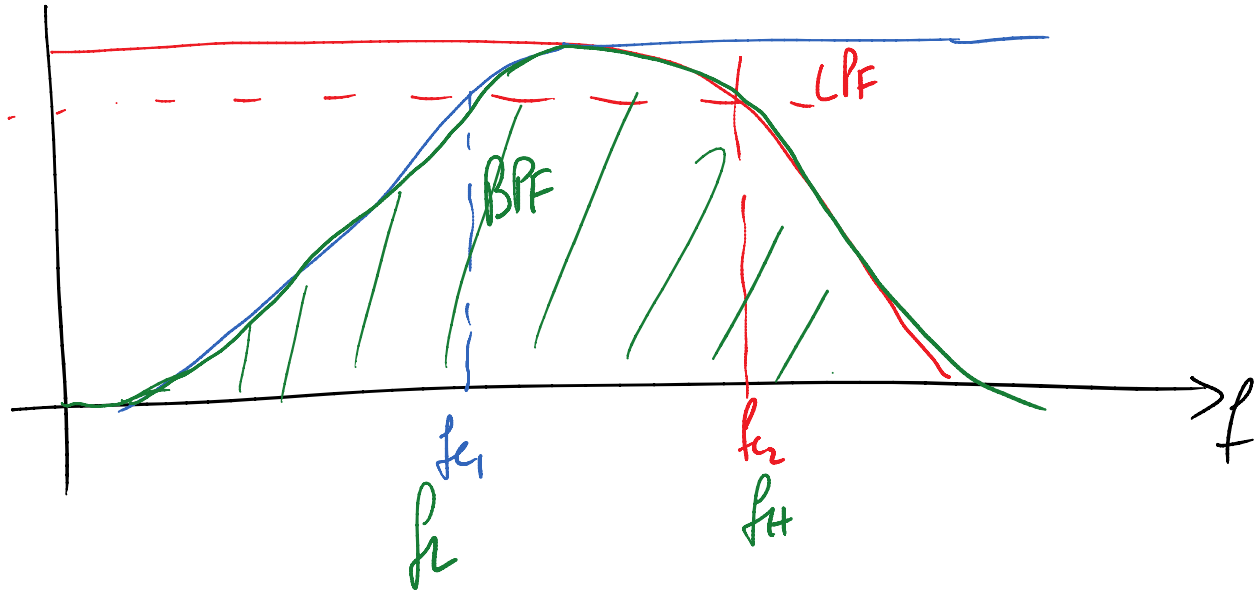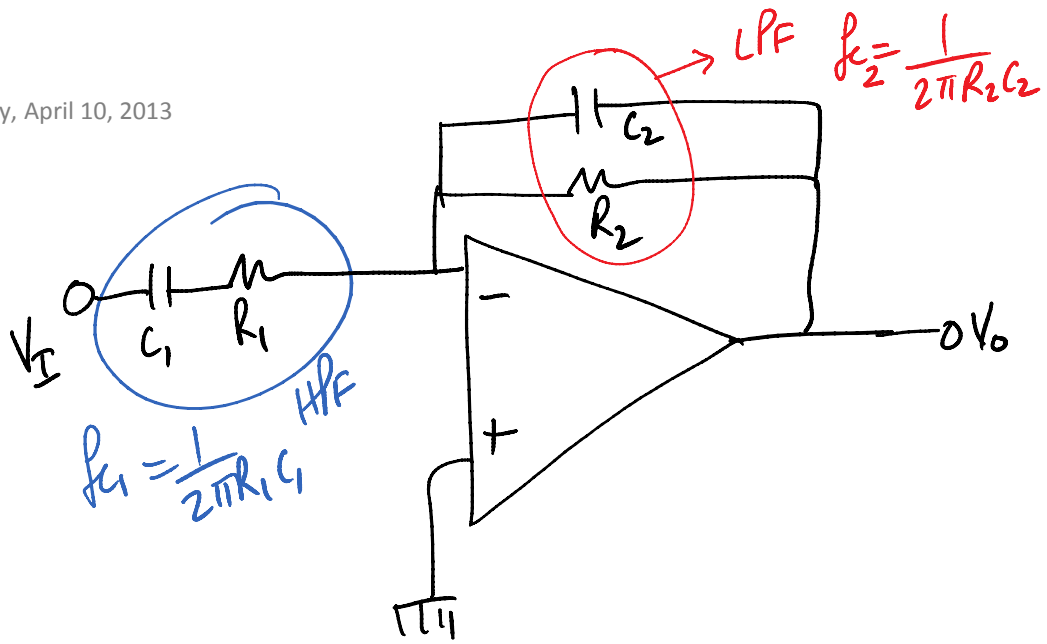

# HALF WAVE RECTIFIER OP-AMP CIRCUIT

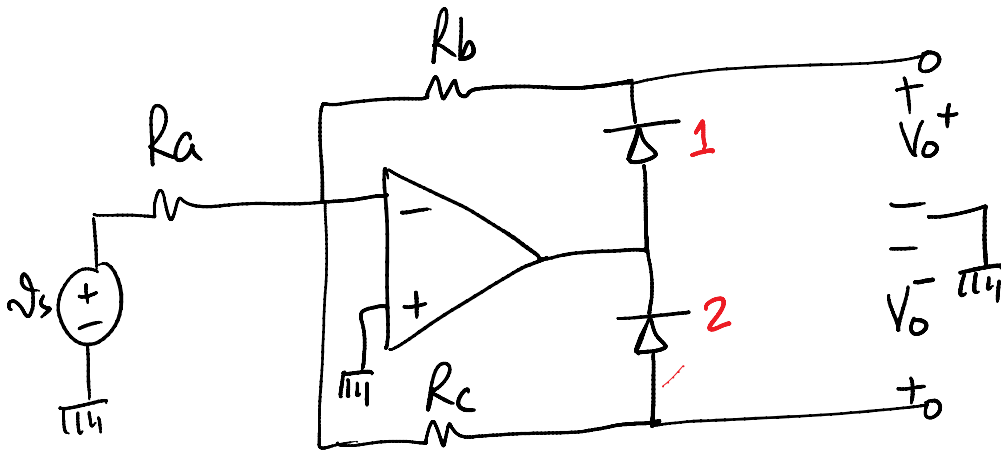

$v_s > 0$  DIODE 2 IS ON DIODE 1 IS OFF  
CURRENT FLOWS THROUGH  $R_c$   
(NEGATIVE)

$$\therefore V_o^- = -\frac{R_c}{R_a} v_s$$

$$V_o^+ = 0$$


$v_s < 0$  DIODE 1 IS ON, DIODE 2 IS OFF  
CURRENT FLOWS THROUGH  $R_b$

$$\therefore V_o^+ = \frac{R_b}{R_a} v_s \text{ (POSITIVE)}$$

$$V_o^- = 0$$



# VOLTAGE TO CURRENT OP-AMP CIRCUIT

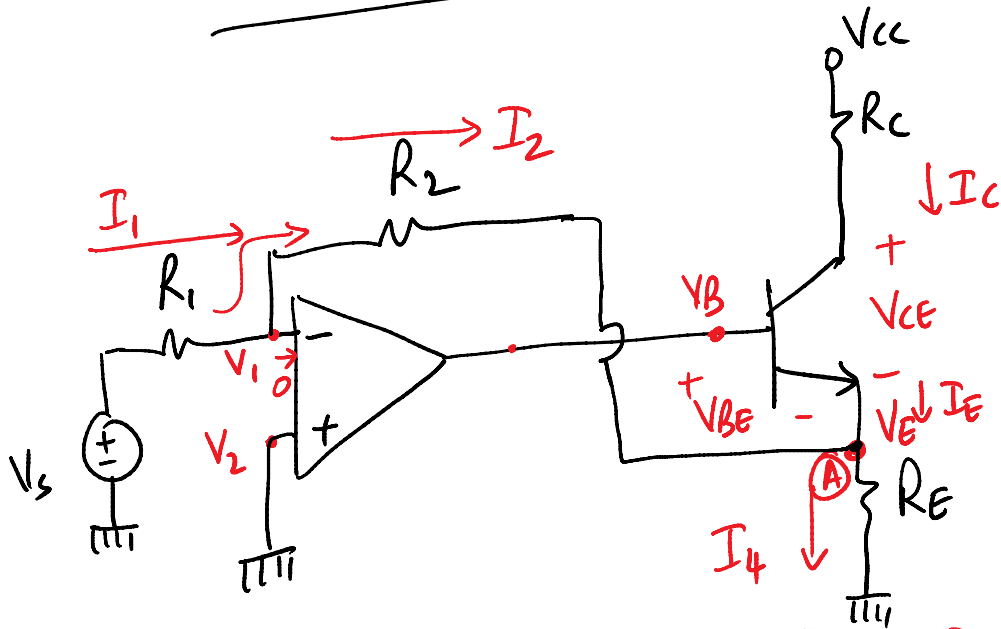

\* SINCE INPUT VOLTAGE IS GIVEN TO THE NEGATIVE TERMINAL  $\therefore V_s < 0$  (REQUIREMENT) FOR PROPER BIASING OF TRANSISTOR

$V_2 = 0$  VIRTUAL GROUND THEORY  $V_1 = 0$

$$I_1 = \frac{V_s}{R_1}$$

$$I_2 = \frac{0 - V_E}{R_2}$$

$$I_1 = I_2$$

$$\frac{V_s}{R_1} = -\frac{V_E}{R_2}$$

$$V_E = -V_s \frac{R_2}{R_1}$$

KVL BE LOOP

$$-V_B + V_{BE(ON)} + V_E = 0$$

← OUTPUT OF OP-AMP

$$V_B = V_{BE(ON)} + V_E$$

$$I_4 = \frac{V_E}{R_E}$$

KCL NODE (A)

$$I_E + I_2 = I_4$$

$$I_E = I_4 - I_2$$

ASSUMING OPERATION IN ACTIVE REGION

O/P CURRENT! →  $I_C = \alpha I_E$

KVL CE LOOP

$$\underline{\underline{V_{CE} = V_{CC} - I_C R_C - V_E}}$$