

Lecture 14: Current, Resistance, Ohm's Law

- Current is motion of charges
- Charge carriers in metals are electrons
- Current is created by a potential difference due to an electric field


Electric field is zero inside conductor **in static equilibrium**.

Now: charges move!

Conservation of current

Current is the same at all points in a current-carrying wire.

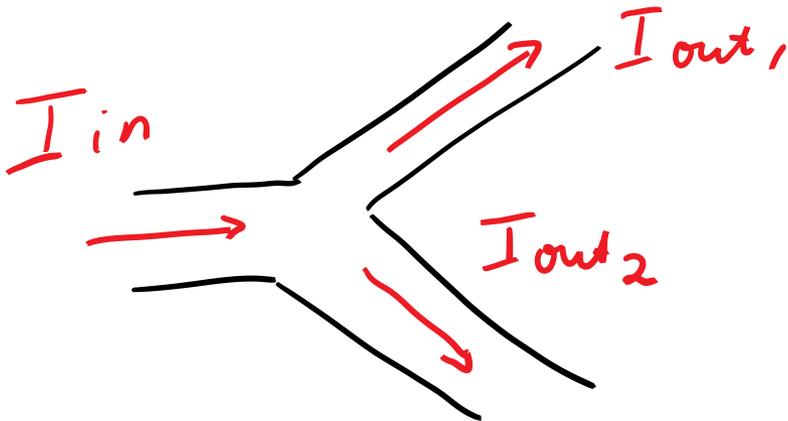Current is not “used up”. Charge cannot be created or destroyed.
“What goes in must come out”.



$$\sum I_{in} = \sum I_{out}$$


Kirchhoff's junction rule

Direction of current

Current is defined as the flow of **positive** charges. The actual charge carriers in metals are negative electrons. They move in the opposite direction.

$$I = \frac{\Delta q}{\Delta t}$$

Unit: 1C/1s= 1A Ampere

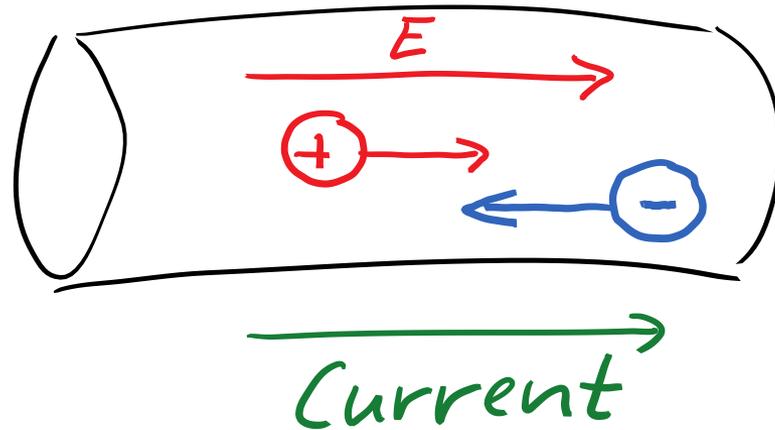

Batteries

Chemical reactions between electrolyte and electrodes cause separation of positive and negative charges
Work done comes from chemical energy

$$\mathcal{E} = W_{\text{chem}}/q \quad \text{electromotive force}$$

$$\Delta V_{\text{bat}} = \mathcal{E} \quad *$$

*In reality, slightly less because of internal resistance which we will ignore

Batteries in series: voltages add

Resistance and resistivity

Current increases proportional to applied voltage

$$I = \frac{\Delta V}{R}$$

$$R = \frac{\Delta V}{I}$$

Resistance

Unit: $1\text{V}/1\text{A} = 1\Omega$ Ohm

Resistance depends on:

- Material
- Length of wire
- Cross section

Resistance is a
device property.

$$R = \frac{\rho L}{A}$$

ρ resistivity (lower case Greek “rho”)

Unit: Ωm

Material property

Example


A Nichrome wire is 15 cm long. If a potential difference of 1.5V is applied, the current through the wire is 2.0A.
What is the diameter of the wire?

Ohm's Law and Power

$$I = \frac{\Delta V}{R}$$

Ohm's Law

Ohmic materials obey Ohm's Law

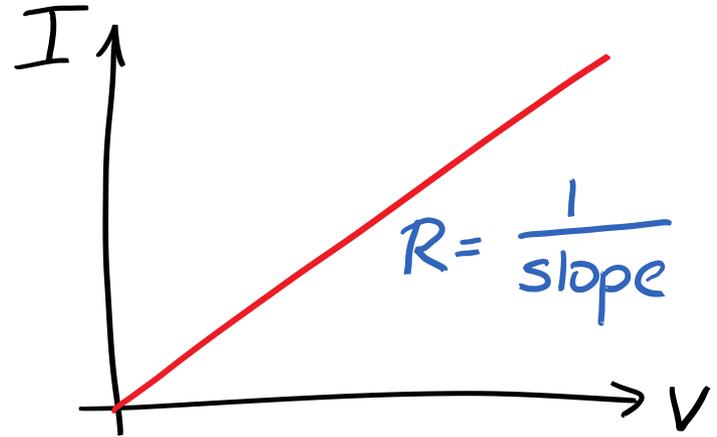


Exceptions: batteries, semiconductors, capacitors, other devices

Current flow through resistor

Assume “ideal wires” ($R=0$).

In reality: $R_{\text{wire}} \ll R_{\text{circuit element}}$

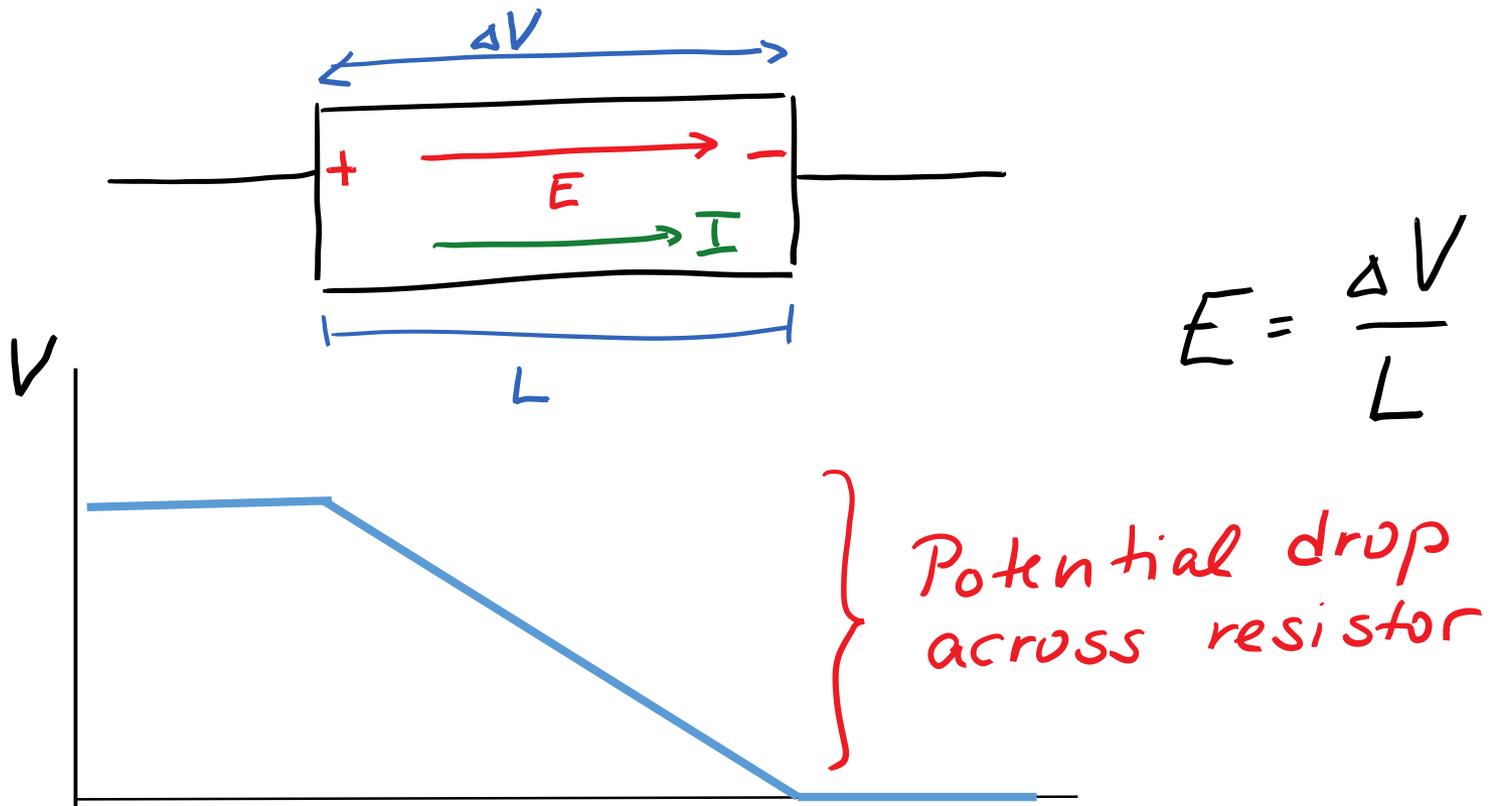Example: flashlight bulb $R=3\Omega$; wire connecting bulb to battery: $R=0.01\Omega$



Energy and Power

Battery supplies $\Delta U = q\varepsilon$ to each charge

Per time Δt , amount of charge Δq moves through battery

$$\text{Power: } P_{\text{battery}} = \frac{\Delta q \varepsilon}{\Delta t} = I\varepsilon$$

In resistor: charge loses potential energy (transformed to kinetic energy and then to heat)

$$P_R = I\Delta V_R$$

With Ohm's law:

$$P_R = I\Delta V_R = I^2 R = \frac{(\Delta V_R)^2}{R}$$

Demo

Example

An electric heater draws 15.0A on a 120V line.

How much power does it use?

How much energy does the heater use per hour?

How much does it cost to run it for 3 hours/day for 30 days, if electric company charges 9.3ct per kWh?