

Electricity & Magnetism

FE Review

Voltage

$$v = \frac{dw}{dq} \quad \frac{\text{joule}}{\text{coulomb}} = \frac{J}{C} = V \text{ (volts)}$$

1 V \equiv 1 J/C
1 J of work must be done to move a 1-C charge through a potential difference of 1V.

Current

$$i = \frac{dq}{dt} \quad \frac{\text{coulomb}}{\text{second}} = \frac{C}{s} = A \text{ (amperes)}$$

Power

$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi \quad \frac{\text{joule}}{\text{second}} = \frac{J}{s} = W \text{ (watts)}$$

Point Charge, Q

- Experiences a force $\mathbf{F}=\mathbf{Q}\mathbf{E}$ in the presence of electric field \mathbf{E} (\mathbf{E} is a vector with units volts/meter)
- Work done in moving Q within the \mathbf{E} field

$$W = -\int_0^r \mathbf{F} \cdot d\mathbf{r}$$

- \mathbf{E} field at distance r from charge Q in free space

$$\mathbf{E} = \frac{Q\mathbf{a}_r}{4\pi\epsilon_0 r^2} \quad \epsilon_0 = 8.85 \times 10^{-12} \text{ F/m (permittivity of free space)}$$


\mathbf{a}_r = unit vector in direction of \mathbf{E}

- Force on charge Q_1 a distance r from Q


$$\mathbf{F} = Q_1 \mathbf{E} = \frac{Q_1 Q \mathbf{a}_r}{4\pi\epsilon_0 r^2}$$

- Work to move Q_1 closer to Q
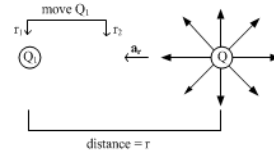
$$W = -\int_{r_1}^{r_2} \frac{Q_1 Q}{4\pi\epsilon_0 r^2} \mathbf{a}_r \cdot d\mathbf{r} = \frac{Q_1 Q}{4\pi\epsilon_0} \left(\frac{1}{r_2} - \frac{1}{r_1} \right)$$



Parallel Plate Capacitor

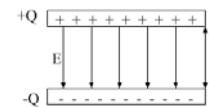

Q =charge on plate
 A =area of plate
 $\epsilon_0=8.85 \times 10^{-12}$ F/m

Electric Field between Plates

$$E = \frac{Q}{\epsilon_0 A}$$

Capacitance

$$C = \frac{\epsilon_0 A}{d}$$


Potential difference (voltage) between the plates

$$V = Ed = \frac{Qd}{\epsilon_0 A}$$

Resistivity $R = \frac{\rho L}{A} = \frac{L}{\sigma A}$

L = length
 A = cross-sectional area
 ρ = resistivity of material
 σ = conductivity of material

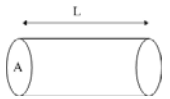Example: Find the resistance of a 2-m copper wire if the wire has a diameter of 2 mm.



$\rho_{Cu} = 2 \times 10^{-8} \Omega \cdot m$
 $A = \pi r^2 = \pi (0.001)^2$


$$R = \frac{\rho L}{A} = \frac{(2 \times 10^{-8} \Omega \cdot m)(2m)}{\pi (0.001)^2 m^2} = 1.273 \times 10^{-2} \Omega = 12.73 \text{ m}\Omega$$

Resistor $v = Ri$

Power absorbed $p = vi = Ri^2 = \frac{v^2}{R}$


Energy dissipated $w = \int p \, dt = \int_{\text{one period}} p \, dt$

Parallel Resistors

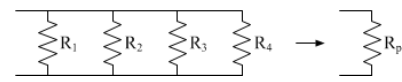

$$R_p = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

Series Resistors

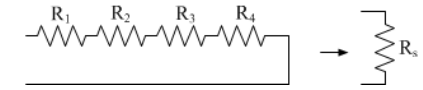


$$R_s = R_1 + R_2 + R_3 + R_4$$

Capacitor $i = C \frac{dv}{dt}$

Stores Energy $w = \frac{1}{2} Cv^2$


$$v = \frac{1}{C} \int_{-\infty}^t i \, d\lambda = v(0) + \frac{1}{C} \int_0^t i \, d\lambda$$

Parallel Capacitors

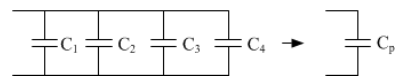

$$C_p = C_1 + C_2 + C_3 + C_4$$

Series Capacitors

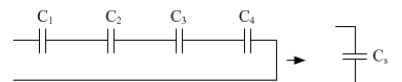


$$C_s = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4}}$$

Inductor $v = L \frac{di}{dt}$

Stores Energy $w = \frac{1}{2} Li^2$


$$i = \frac{1}{L} \int_{-\infty}^t v \, d\lambda = i(0) + \frac{1}{L} \int_0^t v \, d\lambda$$

Parallel Inductors

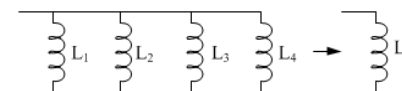

$$L_p = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4}}$$

Series Inductors

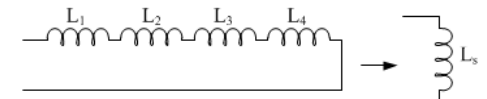

$$L_s = L_1 + L_2 + L_3 + L_4$$

KVL – Kirchhoff's Voltage Law


The sum of the voltage drops around a closed path is zero.

KCL – Kirchhoff's Current Law

The sum of the currents leaving a node is zero.


Voltage Divider
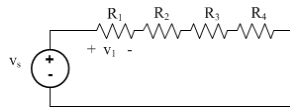
$$v_1 = \frac{R_1}{R_1 + R_2 + R_3 + R_4} v_s$$




Current Divider
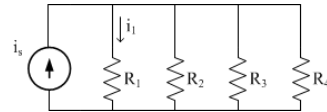
$$i_1 = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} i_s$$



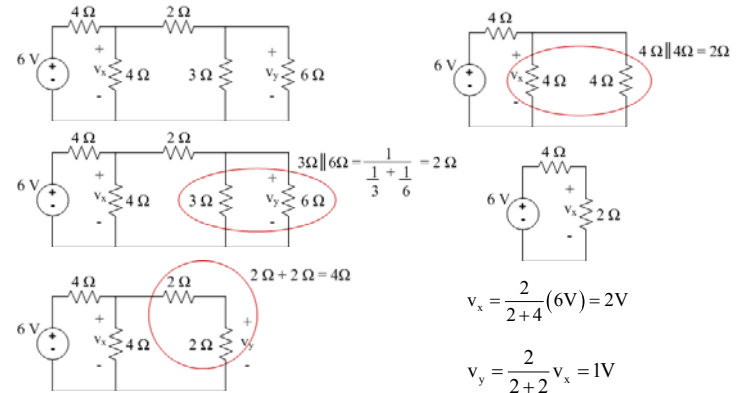Example: Find v_x and v_y and the power absorbed by the 6-Ω resistor.




$$v_x = \frac{2}{2+4} (6V) = 2V$$

$$v_y = \frac{2}{2+2} v_x = 1V$$


$$P_{6\Omega} = \frac{v_y^2}{R} = \frac{v_y^2}{6} = \frac{1}{6} W$$

Node Voltage Analysis

Find the node voltages, v_1 and v_2

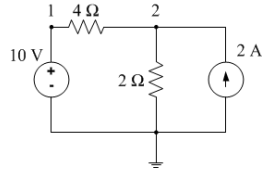

Look at voltage sources first

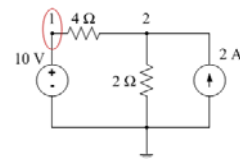


Node 1 is connected directly to ground by a voltage source $\rightarrow v_1 = 10V$

All nodes not connected to a voltage source are KCL equations

↓

Node 2 is a KCL equation

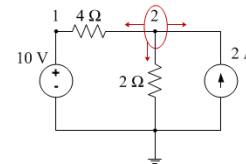

KCL at Node 2

$$\frac{v_2 - v_1}{4} + \frac{v_2}{2} - 2 = 0$$


$$-\frac{1}{4}v_1 + \frac{3}{4}v_2 = 2 \rightarrow -v_1 + 3v_2 = 8$$

$$v_2 = \frac{8 + v_1}{3} = \frac{8 + 10}{3} = 6V$$

$$\begin{matrix} v_1 = 10V \\ v_2 = 6V \end{matrix}$$

Mesh Current Analysis

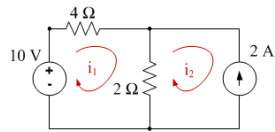Find the mesh currents i_1 and i_2 in the circuit



Look at current sources first

Mesh 2 has a current source in its outer branch

$$i_2 = -2A$$

All meshes not containing current sources are KVL equations

KVL at Mesh 1


$$-10 + 4i_1 + 2(i_1 - i_2) = 0$$

$$i_1 = \frac{10 + 2i_2}{6} = \frac{10 + 2(-2)}{6} = 1A$$

Find the power absorbed by the 4-Ω resistor

$$P_{4\Omega} = i^2 R = (1)^2 (4) = 4W$$

RL Circuit

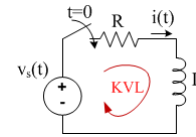

$$-v_s + Ri + L \frac{di}{dt} = 0$$

$$\frac{di}{dt} + \frac{R}{L}i = \frac{1}{L}v_s$$

Put in some numbers

$$R = 2 \Omega$$

$$L = 4 \text{ mH}$$

$$v_s(t) = 12 \text{ V}$$

$$i(0) = 0 \text{ A}$$

$$\frac{di}{dt} + 500i = 3000$$

$$i_n(t) = Ae^{-Rt/L} = Ae^{-500t}$$

$$i_p(t) = K$$

$$0 + 500K = 3000 \rightarrow K = \frac{v_s}{R} = 6$$


$$i(t) = Ae^{-500t} + 6$$

$$i(0) = 0 \rightarrow 0 = Ae^{-500(0)} + 6 \rightarrow A = -6$$

$$i(t) = \frac{v_s}{R} (1 - e^{-Rt/L}) = 6(1 - e^{-500t}) \text{ A}$$

$$v(t) = L \frac{di}{dt} = 0.004 \frac{d}{dt} (6 - 6e^{-500t}) = 12e^{-500t} \text{ V}$$

RC Circuit

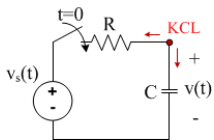

$$C \frac{dv}{dt} + \frac{v - v_s}{R} = 0$$

$$\frac{dv}{dt} + \frac{1}{RC}v = \frac{1}{RC}v_s$$

Put in some numbers

$$R = 2 \Omega$$

$$C = 2 \text{ mF}$$

$$v_s(t) = 12 \text{ V}$$

$$v(0) = 5 \text{ V}$$

$$\frac{dv}{dt} + 250v = 3000$$

$$v_n(t) = Ae^{-t/RC} = Ae^{-250t}$$

$$v_p(t) = K$$

$$0 + 250K = 3000 \rightarrow K = v_s = 12$$


$$v(t) = Ae^{-250t} + 12$$

$$v(0) = 5 \rightarrow 5 = Ae^{-250(0)} + 12 \rightarrow A = -7$$

$$v(t) = v_s - (v_s - v_0)e^{-t/RC} = 12 - 7e^{-250t} \text{ V}$$

$$i(t) = C \frac{dv}{dt} = 0.002 \frac{d}{dt} (12 - 7e^{-250t}) = 3.5e^{-250t} \text{ A}$$


DC Steady-State

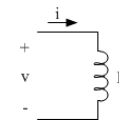

$$v = L \frac{di}{dt} = 0$$

$$i = \text{constant}$$

Short Circuit

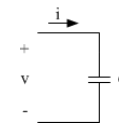


$$i = C \frac{dv}{dt} = 0$$

$$v = \text{constant}$$

Open Circuit

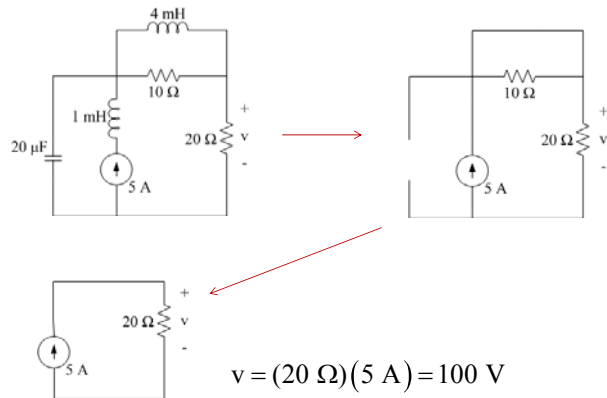Example: Find the DC steady-state voltage, v , in the following circuit.



Complex Arithmetic

Rectangular


$$a + jb$$

Exponential

$$Ae^{j\theta}$$

Polar

$$A \angle \theta$$

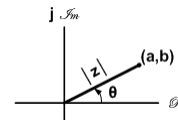

Plot $z = a + jb$ as an ordered pair on the real and imaginary axes

$$\tan \theta = \frac{b}{a}$$

$$|z| = |a + jb| = \sqrt{a^2 + b^2}$$

Complex Conjugate

$$(a + jb)^* = a - jb \quad (A \angle \theta)^* = A \angle -\theta$$

Euler's Identity

$$e^{j\theta} = \cos \theta + j \sin \theta$$

Complex Arithmetic

$$z_1 = Ae^{j\theta} = A \angle \theta = a_x + ja_y$$

$$z_2 = Be^{j\phi} = B \angle \phi = b_x + jb_y$$

$$\frac{20 \angle 40^\circ}{5 \angle 60^\circ} = \frac{20}{5} \angle (40^\circ - 60^\circ)$$

$$= 4 \angle -20^\circ$$

Addition

$$z_1 + z_2 = (a_x + ja_y) + (b_x + jb_y) = (a_x + b_x) + j(a_y + b_y)$$

Multiplication

$$z_1 \cdot z_2 = (A \angle \theta)(B \angle \phi)$$

$$= AB \angle (\theta + \phi)$$

Division

$$\frac{z_1}{z_2} = \frac{A \angle \theta}{B \angle \phi}$$

$$= \frac{A}{B} \angle (\theta - \phi)$$

Phasors

A complex number representing a sinusoidal current or voltage.

$$V_m \cos(\omega t + \phi) \rightarrow V_m \angle \phi$$

Only for:

- Sinusoidal sources
- Steady-state

Impedance

A complex number that is the ratio of the phasor voltage and current.

$$Z = \frac{V}{I} \quad \text{units} = \text{ohms } (\Omega)$$

Admittance

$$Y = \frac{I}{V} \quad \text{units} = \text{Siemens } (S)$$

Phasors

Converting from sinusoid to phasor

$$20 \cos(40t + 15^\circ) \text{ A} \rightarrow 20 \angle 15^\circ \text{ A}$$

$$100 \cos(10^3 t) \text{ V} \rightarrow 100 \angle 0^\circ \text{ V}$$

$$6 \sin(100t + 10^\circ) \text{ A} = 6 \cos(100t + 10^\circ - 90^\circ) \text{ A} \rightarrow 6 \angle -80^\circ \text{ A}$$

Ohm's Law for Phasors

$$\mathbf{V} = \mathbf{Z}\mathbf{I}$$



Ohm's Law
Voltage Divider
Node Voltage Analysis

Current Divider
KVL
KCL
Mesh Current Analysis



Impedance




$$\mathbf{Z} = R = R \angle 0^\circ$$

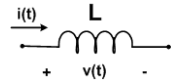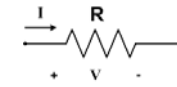

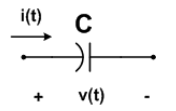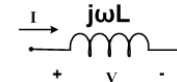
$$\mathbf{Z} = j\omega L = \omega L \angle 90^\circ$$


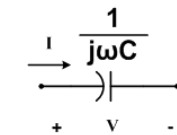
$$\mathbf{Z} = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$



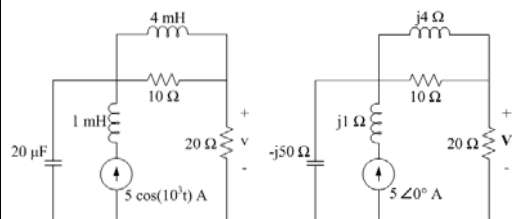Example: Find the steady-state output, $v(t)$.



$$\mathbf{I} = \frac{\frac{1}{20 + 1.38 + j3.45}}{\frac{1}{-j50} + \frac{1}{20 + 1.38 + j3.45}} 5 \angle 0^\circ$$


$$= 4.88 \angle -24.67^\circ \text{ A}$$

$$\mathbf{V} = \mathbf{Z}\mathbf{I} = 20(4.88 \angle -24.67^\circ)$$


$$= 97.61 \angle -24.67^\circ \text{ V}$$

$$v(t) = 97.61 \cos(10^3 t - 24.67^\circ) \text{ V}$$
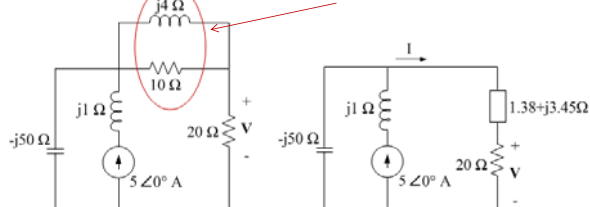
$$10 \Omega \parallel j4 \Omega = 3.71 \angle 68.20^\circ \Omega = 1.38 + j3.45 \Omega$$



Source Transformations

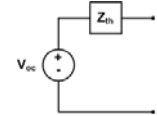



Thévenin Equivalent



Norton Equivalent

$$\mathbf{V}_{oc} = \mathbf{I}_{sc} \cdot \mathbf{Z}_{th}$$

Two special cases

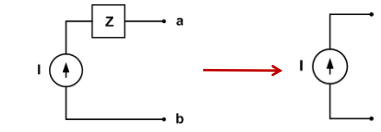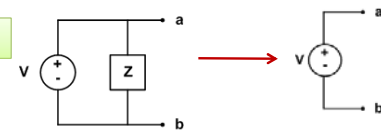

Example: Find the steady-state voltage, $v_{out}(t)$

$I = \frac{10\angle 0^\circ}{-j2} = 5\angle 90^\circ \text{ A}$

$Z = \frac{1}{\frac{1}{-j2} + \frac{1}{-j2}} = -j1 \Omega$

$V = (5\angle 90^\circ)(-j1) = 5\angle 0^\circ \text{ V}$

$I = \frac{5\angle 0^\circ}{j1} = 5\angle -90^\circ \text{ A}$

$Z = \frac{1}{\frac{1}{j1} + \frac{1}{j1}} = j0.5 \Omega$

$V = (5\angle -90^\circ)(j0.5) = 2.5\angle 0^\circ \text{ V}$

No current flows through the impedance

$V_{out} = 2.5\angle 0^\circ \text{ V}$

$v_{out}(t) = 2.5\cos(2t) \text{ V}$

Thévenin Equivalent

AC Power

Complex Power $S = \frac{1}{2} \mathbf{VI}^* = P + jQ$ units = VA (volt-amperes)


Average Power $P = \frac{1}{2} V_m I_m \cos \theta$ units = W (watts)
a.k.a. "Active" or "Real" Power

Reactive Power $Q = \frac{1}{2} V_m I_m \sin \theta$ units = VAR (volt-ampere reactive)


Power Factor $PF = \cos \theta$ $\theta = \text{impedance angle}$

leading or lagging
 current is leading the voltage $\theta < 0$ current is lagging the voltage $\theta > 0$

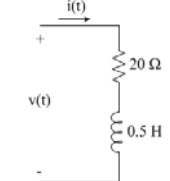Example: $v(t) = 2000 \cos(100t) \text{ V}$



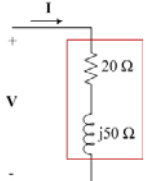$\mathbf{V} = 2000 \angle 0^\circ \text{ V}$



$Z = 20 + j50 \Omega$
 $= 53.85 \angle 68.20^\circ \Omega$

Current, I
 $\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{2000 \angle 0^\circ}{20 + j50} = 37.14 \angle -68.20^\circ \text{ A}$

Power Factor
 $\text{PF} = \cos \theta = \cos(68.20^\circ) = 0.371 \text{ lagging}$

Complex Power Absorbed
 $S = \frac{1}{2} \mathbf{V} \mathbf{I}^* = \frac{1}{2} (2000 \angle 0^\circ) (37.14 \angle +68.20^\circ)$
 $= 37139 \angle 68.20^\circ \text{ VA}$
 $= 13793 + j34483 \text{ VA}$

Average Power Absorbed
 $P = 13793 \text{ W}$

Power Factor Correction

We want the power factor close to 1 to reduce the current.


Correct the power factor to 0.85 lagging

$\theta_{\text{new}} = \cos^{-1} 0.85 = +31.79^\circ$

Total Complex Power

Add a capacitor in parallel with the load.

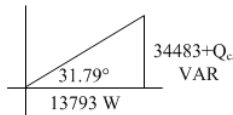$S_{\text{total}} = S + S_{\text{cap}} = (13793 + j34483) + (0 + jQ_{\text{cap}})$



$Q_{\text{cap}} = P \tan \theta_{\text{new}} - Q = 13793 \tan(31.79^\circ) - 34483 = -24934 \text{ VAR}$

$Q_{\text{cap}} = -25934 \text{ VAR} \rightarrow S_{\text{cap}} = -j25934 \text{ VA}$

S for an ideal capacitor
 $S = -j \frac{1}{2} \omega C V_m^2$

$-j25934 = -j \frac{1}{2} (100) C (2000)^2$

$C = 0.13 \text{ mF}$

$S_{\text{total}} = S + S_{\text{cap}} = (13793 + j34483) + (0 - j25934)$
 $= 13793 + j8549 \text{ VA} = 16227.5 \angle 31.79^\circ \text{ VA}$

Without the capacitor
 $\mathbf{I} = 37.14 \angle -68.20^\circ \text{ A}$

Current after capacitor added
 $S = \frac{1}{2} \mathbf{V} \mathbf{I}^* \rightarrow \mathbf{I} = \left(\frac{2S}{\mathbf{V}} \right)^* = \left(\frac{2(13793 + j8549)}{2000 \angle 0^\circ} \right)^* = 16.23 \angle -31.79^\circ \text{ A}$

RMS Current & Voltage a.k.a. "Effective" current or voltage

$V_{\text{rms}} = \left(\frac{1}{T} \int_0^T v^2 dt \right)^{1/2}$ $I_{\text{rms}} = \left(\frac{1}{T} \int_0^T i^2 dt \right)^{1/2}$

RMS value of a sinusoid
 $A \cos(\omega t + \phi) \rightarrow \frac{A}{\sqrt{2}}$

$P = V_{\text{rms}} \cdot I_{\text{rms}} \cos \theta$

Balanced Three-Phase Systems

Line Voltages

$$\mathbf{V}_{ab} = \mathbf{V}_{an} - \mathbf{V}_{bn} = (\sqrt{3}\angle 30^\circ)\mathbf{V}_{an} = V_L\angle\psi$$

$$\mathbf{V}_{bc} = V_L\angle\psi - 120^\circ$$

$$\mathbf{V}_{ca} = V_L\angle\psi + 120^\circ$$

Phase Voltages

$$\mathbf{V}_{an} = V_m\angle 0^\circ$$

$$\mathbf{V}_{bn} = V_m\angle -120^\circ$$

$$\mathbf{V}_{cn} = V_m\angle 120^\circ$$

Line Currents

$$\mathbf{I}_{aA} = \mathbf{I}_{AN} = \frac{\mathbf{V}_{AN}}{Z_{LN}} = I_L\angle\varphi$$

$$\mathbf{I}_{bB} = \mathbf{I}_{BN} = \frac{\mathbf{V}_{BN}}{Z_{LN}} = I_L\angle\varphi - 120^\circ$$

$$\mathbf{I}_{cC} = \mathbf{I}_{CN} = \frac{\mathbf{V}_{CN}}{Z_{LN}} = I_L\angle\varphi + 120^\circ$$

Balanced Three-Phase Systems

Line Voltages

$$\mathbf{V}_{ab} = V_m\angle 0^\circ$$

$$\mathbf{V}_{bc} = V_m\angle -120^\circ$$

$$\mathbf{V}_{ca} = V_m\angle 120^\circ$$

Phase Currents

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{Z_{LL}} = I_L\angle\varphi$$

$$\mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{Z_{LL}} = I_L\angle\varphi - 120^\circ$$

$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{Z_{LL}} = I_L\angle\varphi + 120^\circ$$

Line Currents

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA} = (\sqrt{3}\angle -30^\circ)\mathbf{I}_{AB} = I_L\angle\psi$$

$$\mathbf{I}_{bB} = I_L\angle\psi - 120^\circ$$

$$\mathbf{I}_{cC} = I_L\angle\psi + 120^\circ$$

Currents and Voltages are specified in RMS

S for peak voltage & current

S for RMS voltage & current

S for 3-phase voltage & current

$$S = \frac{1}{2}\mathbf{VI}^* \rightarrow S = \mathbf{VI}^* \rightarrow S = 3\mathbf{VI}^*$$

Complex Power for Y-connected load

$$S = 3\mathbf{V}_{AN}\mathbf{I}_{AN}^* = \sqrt{3}V_L I_L\angle\theta$$

Complex Power for Δ-connected load

$$S = 3\mathbf{V}_{AB}\mathbf{I}_{AB}^* = \sqrt{3}V_L I_L\angle\theta$$

Average Power

$$P = \sqrt{3}V_L I_L \cos\theta$$

Power Factor

PF = $\cos\theta$ (leading or lagging)

$V_L = \text{line voltage} = |\mathbf{V}_{ab}|$

$I_L = \text{line current} = |\mathbf{I}_{aA}|$

$\theta = \text{impedance angle} = \angle Z$

Example:

Find the total real power supplied by the source in the balanced wye-connected circuit

Given:

$$\mathbf{V}_{an} = 540\angle 0^\circ \text{ V}$$


$$Z_{LN} = 270 + j270 \text{ } \Omega$$

$$\mathbf{I}_{aA} = \mathbf{I}_{AN} = \frac{\mathbf{V}_{AN}}{Z_{LN}} = \frac{540\angle 0^\circ}{270 + j270} = 1.41\angle -45^\circ \text{ A}$$

$$S = 3\mathbf{V}_{AN}\mathbf{I}_{AN}^* = 3(540\angle 0^\circ)(1.41\angle 45^\circ) = 2291\angle 45^\circ \text{ VA} = 1620 + j1620 \text{ VA}$$


P=1620 W

Ideal Operational Amplifier (Op Amp)

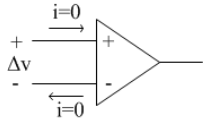

With negative feedback
 $i=0$
 $\Delta v=0$

Linear Amplifier

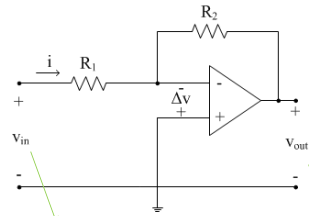

KVL: $-v_{in} + R_1 i - \Delta v = 0 \rightarrow i = \frac{v_{in}}{R_1}$
 KVL: $-v_{in} + R_1 i + R_2 i + v_{out} = 0$
 $-v_{in} + R_1 \left(\frac{v_{in}}{R_1}\right) + R_2 \left(\frac{v_{in}}{R_1}\right) + v_{out} = 0$
 $v_{out} = -\frac{R_2}{R_1} v_{in}$

mV or μ V reading from sensor

0-5 V output to A/D converter

Magnetic Fields

$\oint_S \mathbf{B} \cdot d\mathbf{s} = 0$ $\oint_L \mathbf{H} \cdot d\mathbf{l} = \oint_S \mathbf{J} \cdot d\mathbf{S} = I$

Net magnetic flux through a closed surface is zero.

B – magnetic flux density (tesla)
H – magnetic field strength (A/m)
J - current density

$\mathbf{B} = \mu\mathbf{H}$

Magnetic Flux ϕ passing through a surface

$\phi = \int_S \mathbf{B} \cdot d\mathbf{S}$

Energy stored in the magnetic field

$w = \frac{1}{2} \iiint_V \mu |\mathbf{H}|^2 dV$

Enclosing a surface with N turns of wire produces a voltage across the terminals

$v = -N \frac{d\phi}{dt}$

Magnetic field produces a force perpendicular to the current direction and the magnetic field direction

$\mathbf{F} = I\mathbf{L} \times \mathbf{B}$

Example:

A coaxial cable with an inner wire of radius 1 mm carries 10-A current. The outer cylindrical conductor has a diameter of 10 mm and carries a 10-A uniformly distributed current in the opposite direction. Determine the approximate magnetic energy stored per unit length in this cable. Use μ_0 for the permeability of the material between the wire and conductor.


$\int \mathbf{H} \cdot d\mathbf{l} = H_\phi 2\pi r = I_0 = 10 \text{ A}$
 $H_\phi = \frac{10}{2\pi r}$ for $10^{-3} \text{ m} < r < 10^{-2} \text{ m}$



$w = \frac{1}{2} \iiint_V \mu |\mathbf{H}|^2 dV = \frac{1}{2} \int_0^{10^{-2}} \int_0^{2\pi} \int_0^{0.001} \mu_0 \left(\frac{10}{2\pi r}\right)^2 r dr d\phi dz = 18.3 \mu_0 \text{ J}$

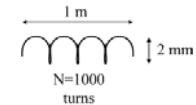Example:

A cylindrical coil of wire has an air core and 1000 turns. It is 1 m long with a diameter of 2 mm so has a relatively uniform field. Find the current necessary to achieve a magnetic flux density of 2 T.



$\int \mathbf{H} \cdot d\mathbf{l} = NI_0$
 $HL = NI_0$

$\left(\frac{B}{\mu_0}\right)L = NI_0 \rightarrow I = \frac{BL}{N\mu_0} = \frac{(2\text{T})(1\text{m})}{1000(4\pi \times 10^{-7})} = 1590 \text{ A}$

Questions?

