

Electricity & Magnetism

FE Review

Voltage

$$v = \frac{dw}{dq} \quad \frac{\text{joule}}{\text{coulomb}} = \frac{J}{C} = V \quad (\text{volts})$$

$$1 \text{ V} \equiv 1 \text{ J/C}$$

1 J of work must be done to move a 1-C charge through a potential difference of 1V.

Current

$$i = \frac{dq}{dt} \quad \frac{\text{coulomb}}{\text{second}} = \frac{C}{s} = A \quad (\text{amperes})$$

Power

$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi \quad \frac{\text{joule}}{\text{second}} = \frac{J}{s} = W \quad (\text{watts})$$

Point Charge, Q

- Experiences a force $\mathbf{F} = Q\mathbf{E}$ in the presence of electric field \mathbf{E} (\mathbf{E} is a vector with units volts/meter)
- Work done in moving Q within the \mathbf{E} field

$$W = -\int_0^{r_1} \mathbf{F} \cdot d\mathbf{r}$$

- \mathbf{E} field at distance r from charge Q in free space

$$\mathbf{E} = \frac{Q\mathbf{a}_r}{4\pi\epsilon_0 r^2}$$

$\epsilon_0 = 8.85 \times 10^{-12}$ F/m (permittivity of free space)


\mathbf{a}_r = unit vector in direction of \mathbf{E}

- Force on charge Q_1 a distance r from Q


$$\mathbf{F} = Q_1\mathbf{E} = \frac{Q_1Q\mathbf{a}_r}{4\pi\epsilon_0 r^2}$$

- Work to move Q_1 closer to Q
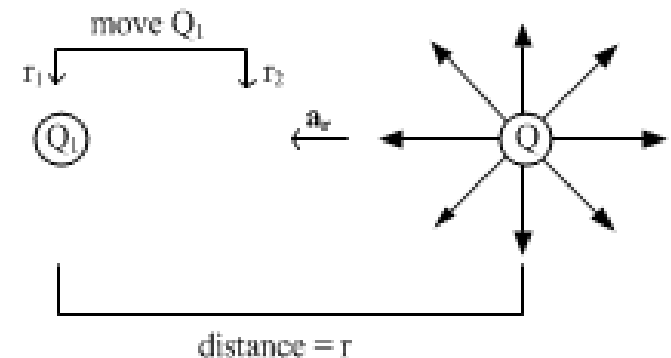
$$W = -\int_{r_1}^{r_2} \frac{Q_1Q}{4\pi\epsilon_0 r^2} \mathbf{a}_r \cdot \mathbf{a}_r dr = \frac{Q_1Q}{4\pi\epsilon_0} \left(\frac{1}{r_2} - \frac{1}{r_1} \right)$$



Parallel Plate Capacitor

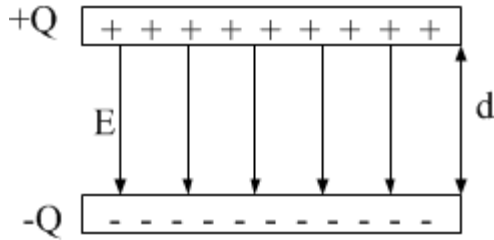

Q=charge on plate

A=area of plate

$\epsilon_0=8.85 \times 10^{-12}$ F/m

Electric Field between Plates

$$E = \frac{Q}{\epsilon_0 A}$$

Potential difference (voltage) between the plates

$$V = Ed = \frac{Qd}{\epsilon_0 A}$$

Capacitance

$$C = \frac{\epsilon_0 A}{d}$$

Resistivity

$$R = \frac{\rho L}{A} = \frac{L}{\sigma A}$$


L = length

A = cross-sectional area

ρ = resistivity of material

σ = conductivity of material

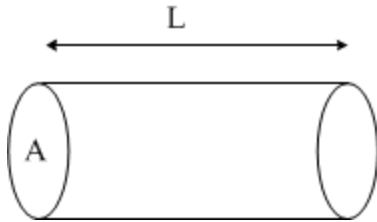Example: Find the resistance of a 2-m copper wire if the wire has a diameter of 2 mm.




$$\rho_{\text{Cu}} = 2 \times 10^{-8} \Omega \cdot \text{m}$$

$$A = \pi r^2 = \pi (0.001)^2$$

$$R = \frac{\rho L}{A} = \frac{(2 \times 10^{-8} \Omega \cdot \text{m})(2 \text{ m})}{\pi (0.001)^2 \text{ m}^2} = 1.273 \times 10^{-2} \Omega = 12.73 \text{ m}\Omega$$

Resistor

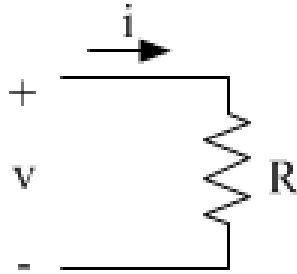

$$v = Ri$$


Power absorbed

$$p = vi = Ri^2 = \frac{v^2}{R}$$

Energy dissipated


$$w = \int p \, dt = \int_{\text{one period}} p \, dt$$

Parallel Resistors

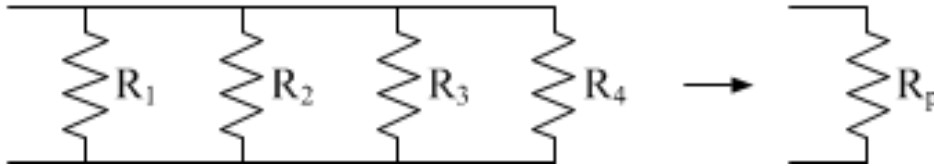


$$R_p = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$$

Series Resistors

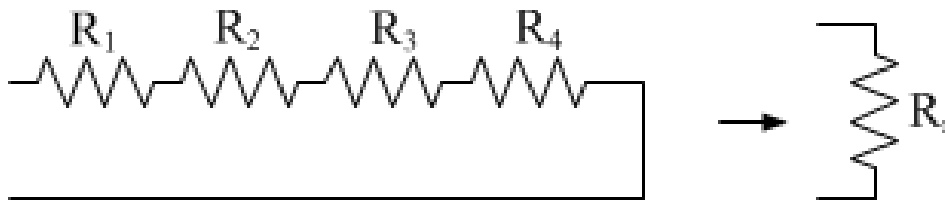

$$R_s = R_1 + R_2 + R_3 + R_4$$

Capacitor

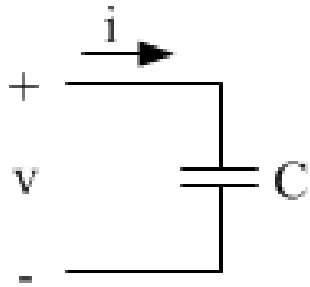


$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_{-\infty}^t i \, d\lambda = v(0) + \frac{1}{C} \int_0^t i \, d\lambda$$

Stores Energy


$$w = \frac{1}{2} C v^2$$

Parallel Capacitors

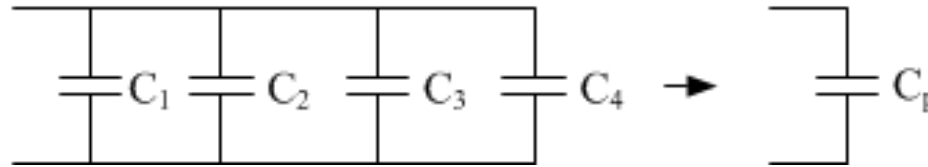


$$C_p = C_1 + C_2 + C_3 + C_4$$

Series Capacitors

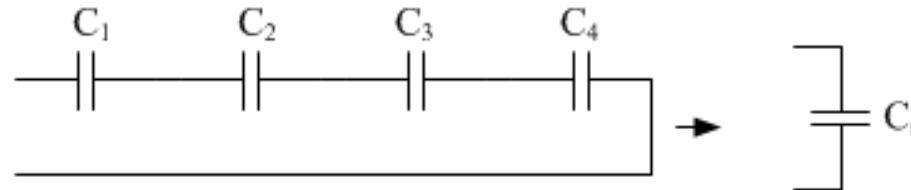

$$C_s = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4}}$$

Inductor

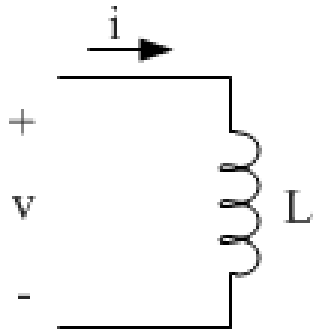


$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_{-\infty}^t v \, d\lambda = i(0) + \frac{1}{L} \int_0^t v \, d\lambda$$

Stores Energy


$$w = \frac{1}{2} Li^2$$

Parallel Inductors

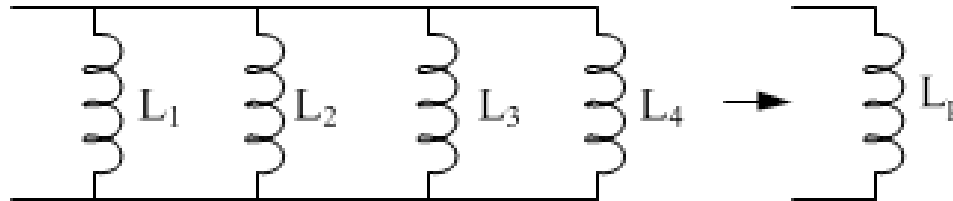

$$L_p = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4}}$$

Series Inductors

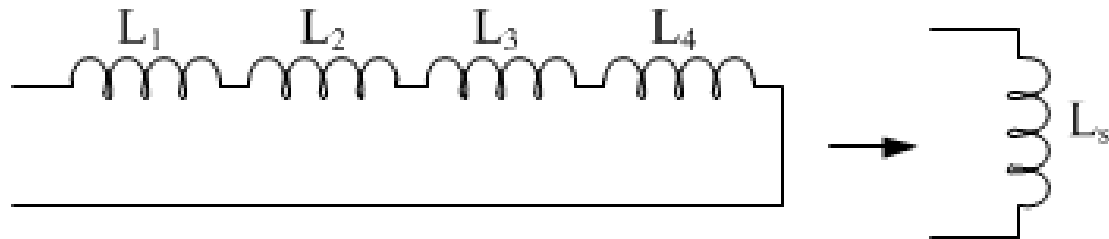

$$L_s = L_1 + L_2 + L_3 + L_4$$

KVL – Kirchhoff's Voltage Law


The sum of the voltage drops around a closed path is zero.

KCL – Kirchhoff's Current Law

The sum of the currents leaving a node is zero.


Voltage Divider
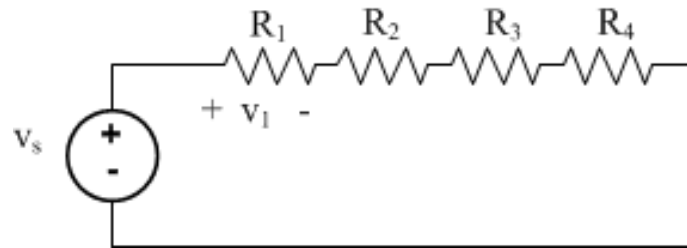
$$v_1 = \frac{R_1}{R_1 + R_2 + R_3 + R_4} v_s$$








Current Divider
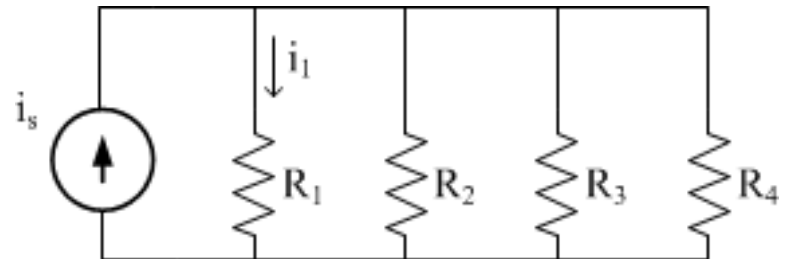
$$i_1 = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} i_s$$



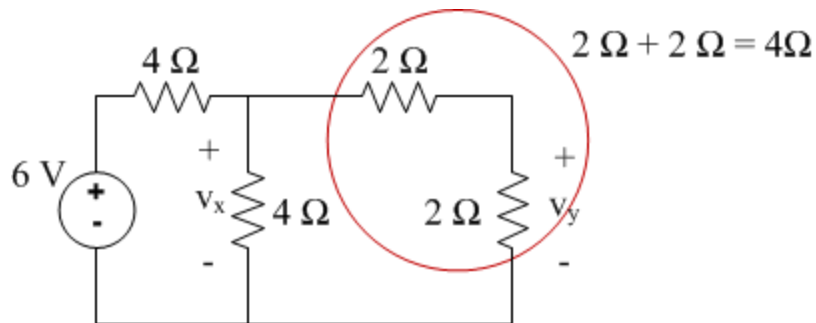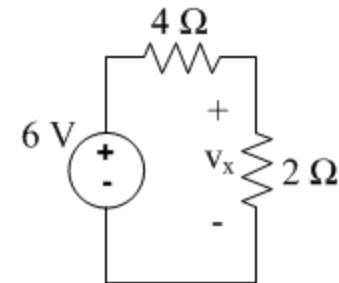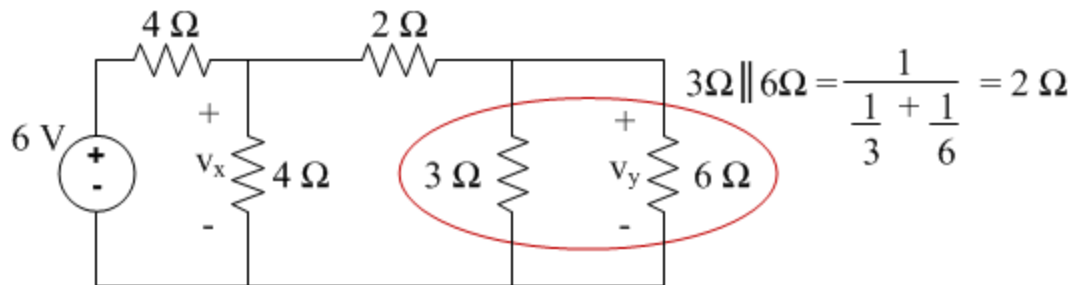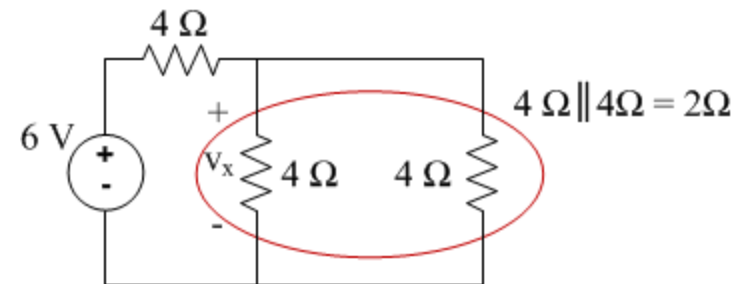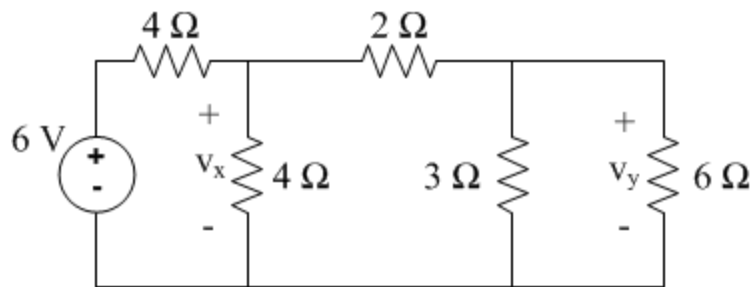Example: Find v_x and v_y and the power absorbed by the 6- Ω resistor.




$$v_x = \frac{2}{2 + 4} (6\text{V}) = 2\text{V}$$

$$v_y = \frac{2}{2 + 2} v_x = 1\text{V}$$


$$P_{6\Omega} = \frac{v^2}{R} = \frac{v_y^2}{6} = \frac{1}{6}\text{W}$$

Node Voltage Analysis

Find the node voltages, v_1 and v_2

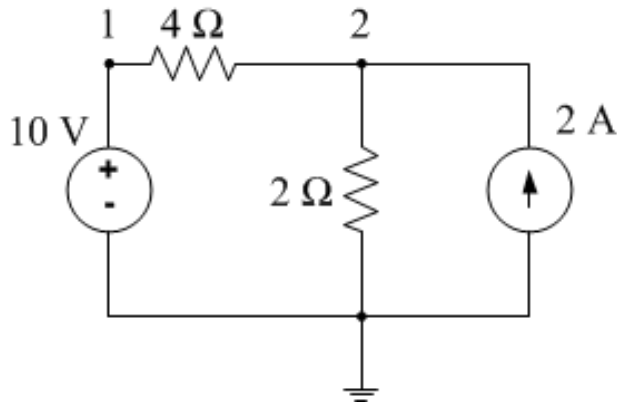

Look at voltage sources first

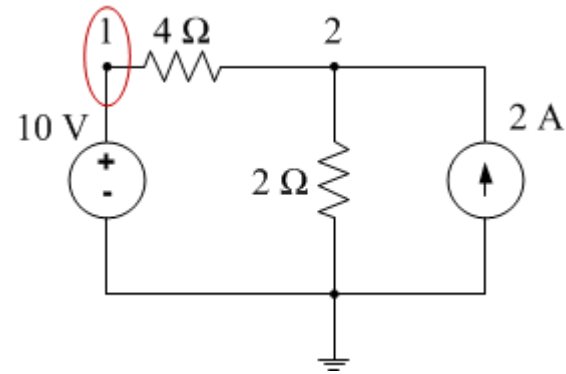


Node 1 is connected directly to ground by a voltage source $\rightarrow v_1 = 10 \text{ V}$

All nodes not connected to a voltage source are KCL equations



Node 2 is a KCL equation

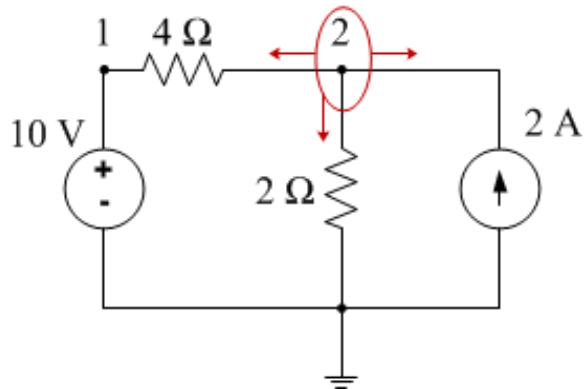

KCL at Node 2

$$\frac{v_2 - v_1}{4} + \frac{v_2}{2} - 2 = 0$$


$$-\frac{1}{4}v_1 + \frac{3}{4}v_2 = 2 \rightarrow -v_1 + 3v_2 = 8$$

$$v_2 = \frac{8 + v_1}{3} = \frac{8 + 10}{3} = 6\text{V}$$

$$\begin{aligned} v_1 &= 10\text{V} \\ v_2 &= 6\text{V} \end{aligned}$$

Mesh Current Analysis

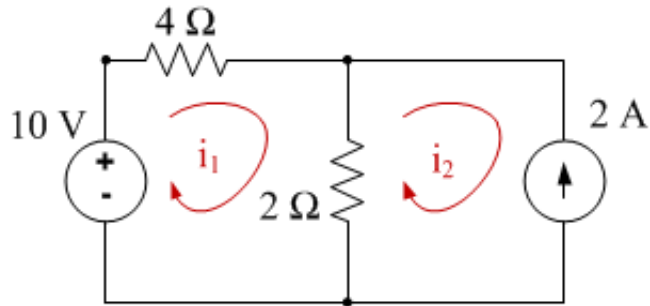Find the mesh currents i_1 and i_2 in the circuit



Look at current sources first

Mesh 2 has a current source in its outer branch

$$i_2 = -2\text{ A}$$

All meshes not containing current sources are KVL equations

KVL at Mesh 1


$$-10 + 4i_1 + 2(i_1 - i_2) = 0$$

$$i_1 = \frac{10 + 2i_2}{6} = \frac{10 + 2(-2)}{6} = 1\text{ A}$$

Find the power absorbed by the 4-Ω resistor

$$P_{4\Omega} = i^2 R = (1)^2 (4) = 4\text{ W}$$

RL Circuit

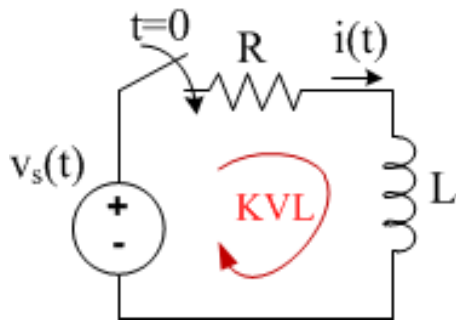

$$-v_s + Ri + L \frac{di}{dt} = 0$$

$$\frac{di}{dt} + \frac{R}{L}i = \frac{1}{L}v_s$$

Put in some numbers

$$R = 2 \Omega$$

$$L = 4 \text{ mH}$$

$$v_s(t) = 12 \text{ V}$$

$$i(0) = 0 \text{ A}$$

$$\frac{di}{dt} + 500i = 3000$$

$$i_n(t) = Ae^{-Rt/L} = Ae^{-500t}$$

$$i_p(t) = K$$

$$0 + 500K = 3000 \rightarrow K = \frac{v_s}{R} = 6$$


$$i(t) = Ae^{-500t} + 6$$

$$i(0) = 0 \rightarrow 0 = Ae^{-500(0)} + 6 \rightarrow A = -6$$

$$i(t) = \frac{v_s}{R}(1 - e^{-Rt/L}) = 6(1 - e^{-500t}) \text{ A}$$

$$v(t) = L \frac{di}{dt} = 0.004 \frac{d}{dt}(6 - 6e^{-500t}) = 12e^{-500t} \text{ V}$$

RC Circuit

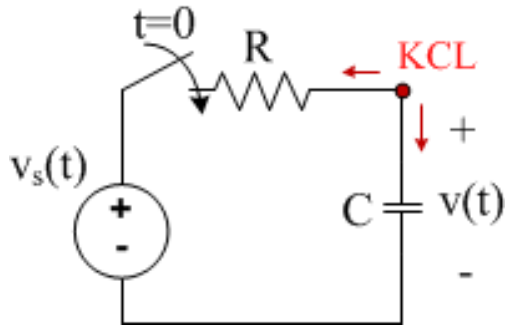

$$C \frac{dv}{dt} + \frac{v - v_s}{R} = 0$$

$$\frac{dv}{dt} + \frac{1}{RC} v = \frac{1}{RC} v_s$$

Put in some numbers

$$R = 2 \Omega$$

$$C = 2 \text{ mF}$$

$$v_s(t) = 12 \text{ V}$$

$$v(0) = 5 \text{ V}$$

$$\frac{dv}{dt} + 250v = 3000$$

$$v_n(t) = Ae^{-t/RC} = Ae^{-250t}$$

$$v_p(t) = K$$

$$0 + 250K = 3000 \rightarrow K = v_s = 12$$


$$v(t) = Ae^{-250t} + 12$$

$$v(0) = 5 \rightarrow 5 = Ae^{-250(0)} + 12 \rightarrow A = -7$$

$$v(t) = v_s - (v_s - v_0)e^{-t/RC} = 12 - 7e^{-250t} \text{ V}$$

$$i(t) = C \frac{dv}{dt} = 0.002 \frac{d}{dt} (12 - 7e^{-250t}) = 3.5e^{-250t} \text{ A}$$

DC Steady-State

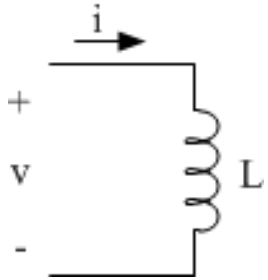


$$v = L \frac{di}{dt} = 0$$

$$i = \text{constant}$$



Short Circuit

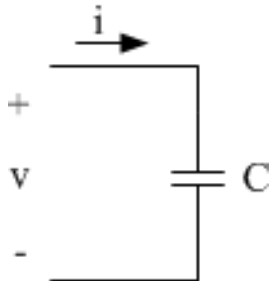

$$i = C \frac{dv}{dt} = 0$$


$$v = \text{constant}$$



Open Circuit

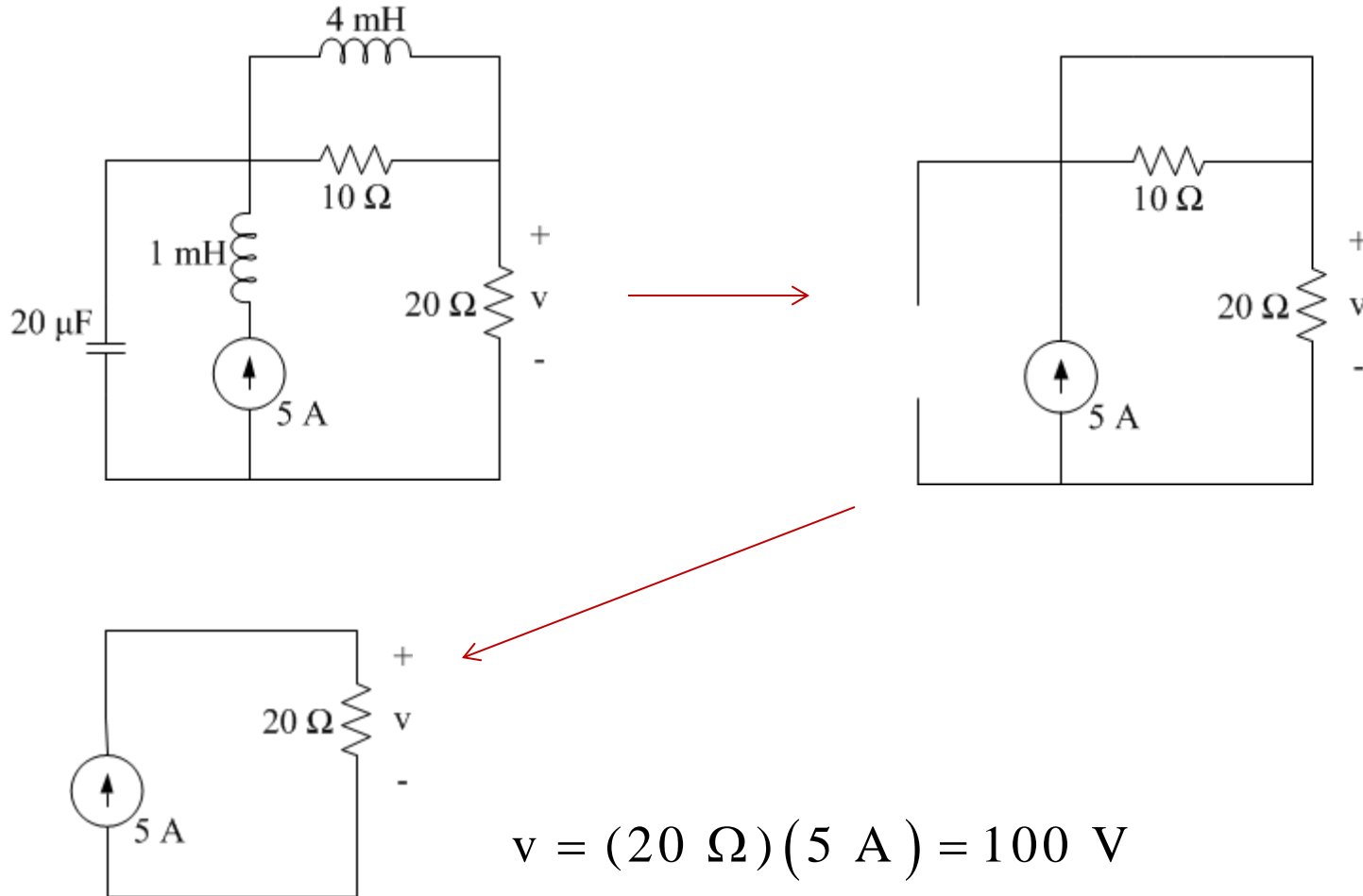Example:

Find the DC steady-state voltage, v , in the following circuit.



Complex Arithmetic

Rectangular


$$a+jb$$

Exponential

$$Ae^{j\theta}$$

Polar

$$A\angle\theta$$

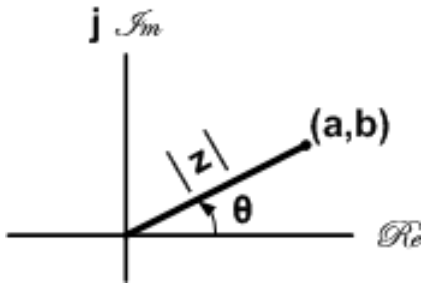

Plot $z=a+jb$ as an ordered pair on the real and imaginary axes

$$\tan \theta = \frac{b}{a}$$

$$|z| = |a+jb| = \sqrt{a^2 + b^2}$$

Complex Conjugate

$$(a+jb)^* = a-jb$$

$$(A\angle\theta)^* = A\angle-\theta$$

Euler's Identity

$$e^{j\theta} = \cos\theta + j \sin\theta$$

Complex Arithmetic

$$z_1 = Ae^{j\theta} = A \angle \theta = a_x + ja_y$$

$$z_2 = Be^{j\varphi} = B \angle \varphi = b_x + jb_y$$

Addition

$$z_1 + z_2 = (a_x + ja_y) + (b_x + jb_y) = (a_x + b_x) + j(a_y + b_y)$$

Multiplication

$$\begin{aligned} z_1 \cdot z_2 &= (A \angle \theta)(B \angle \varphi) \\ &= AB \angle (\theta + \varphi) \end{aligned}$$

Division

$$\begin{aligned} \frac{z_1}{z_2} &= \frac{A \angle \theta}{B \angle \varphi} \\ &= \frac{A}{B} \angle (\theta - \varphi) \end{aligned}$$

$$\begin{aligned} \frac{20 \angle 40^\circ}{5 \angle 60^\circ} &= \frac{20}{5} \angle (40^\circ - 60^\circ) \\ &= 4 \angle -20^\circ \end{aligned}$$

Phasors

A complex number representing a sinusoidal current or voltage.

$$V_m \cos(\omega t + \varphi) \rightarrow V_m \angle \varphi$$

Only for:

- Sinusoidal sources
- Steady-state

Impedance

A complex number that is the ratio of the phasor voltage and current.

$$Z = \frac{\mathbf{V}}{\mathbf{I}}$$

units = ohms (Ω)

Admittance

$$Y = \frac{\mathbf{I}}{\mathbf{V}}$$

units = Siemens (S)

Phasors

Converting from sinusoid to phasor


$$20 \cos(40t + 15^\circ) \text{ A} \rightarrow 20 \angle 15^\circ \text{ A}$$

$$100 \cos(10^3 t) \text{ V} \rightarrow 100 \angle 0^\circ \text{ V}$$


$$6 \sin(100t + 10^\circ) \text{ A} = 6 \cos(100t + 10^\circ - 90^\circ) \text{ A} \rightarrow 6 \angle -80^\circ \text{ A}$$

Ohm's Law for Phasors


$$\mathbf{V} = \mathbf{Z}\mathbf{I}$$

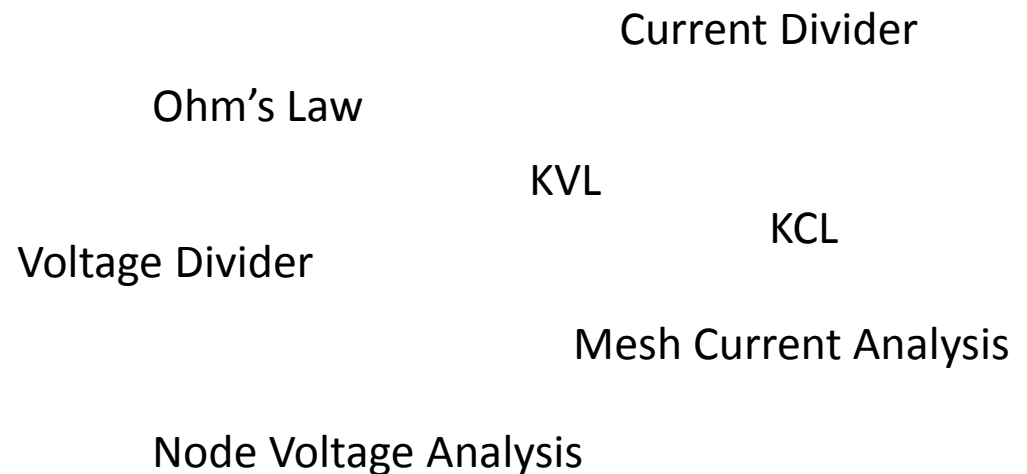



Impedance

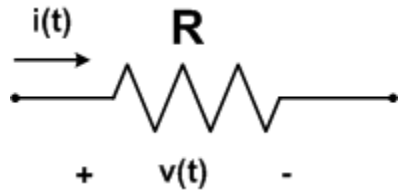


$$Z = R = R \angle 0^\circ$$

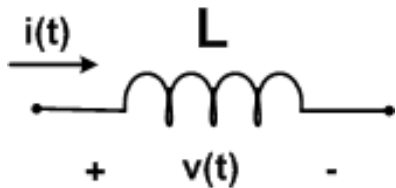

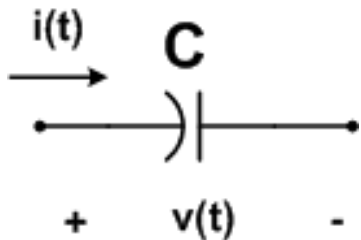
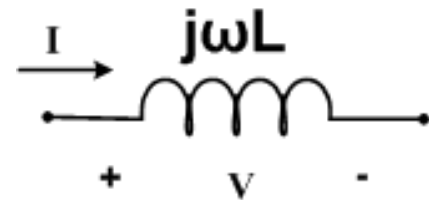
$$Z = j\omega L = \omega L \angle 90^\circ$$


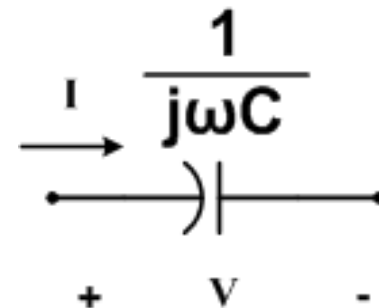
$$Z = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$



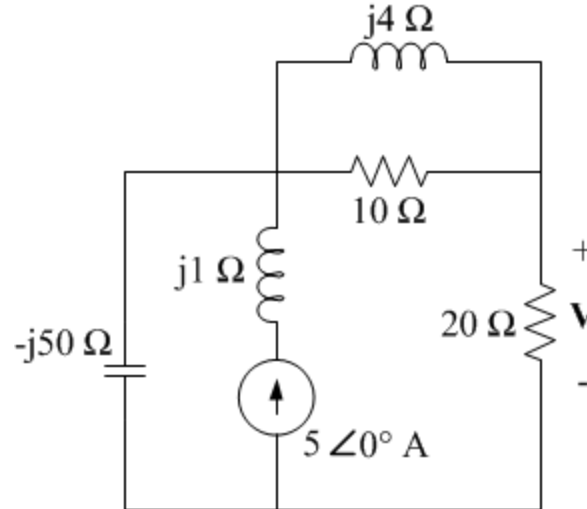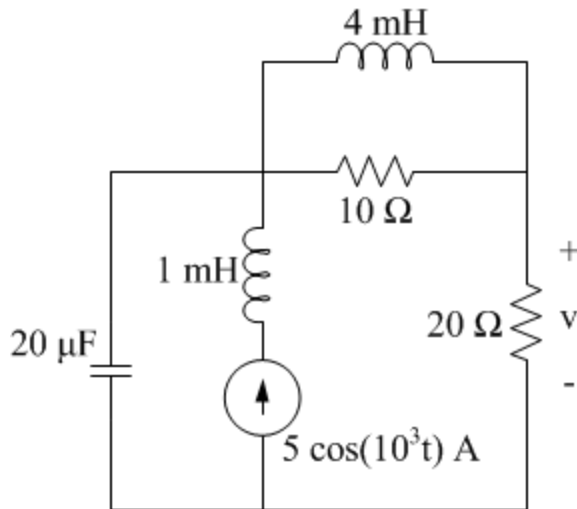Example: Find the steady-state output, $v(t)$.



$$I = \frac{1}{\frac{1}{-j50} + \frac{1}{20 + 1.38 + j3.45}} 5 \angle 0^\circ$$



$$= 4.88 \angle -24.67^\circ \text{ A}$$

$$V = ZI = 20(4.88 \angle -24.67^\circ)$$


$$= 97.61 \angle -24.67^\circ \text{ V}$$

$$v(t) = 97.61 \cos(10^3 t - 24.67^\circ) \text{ V}$$

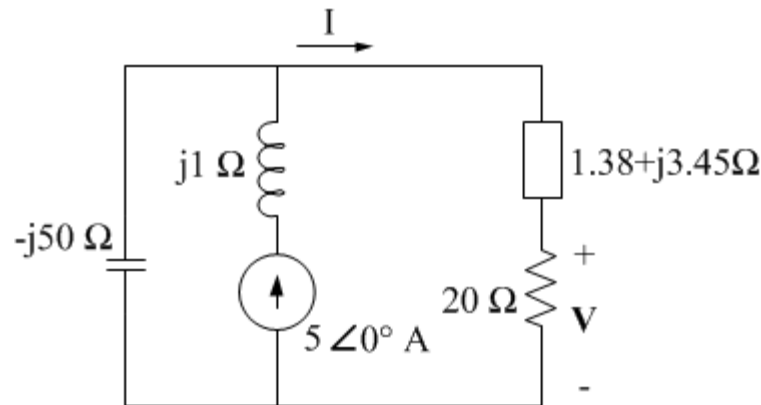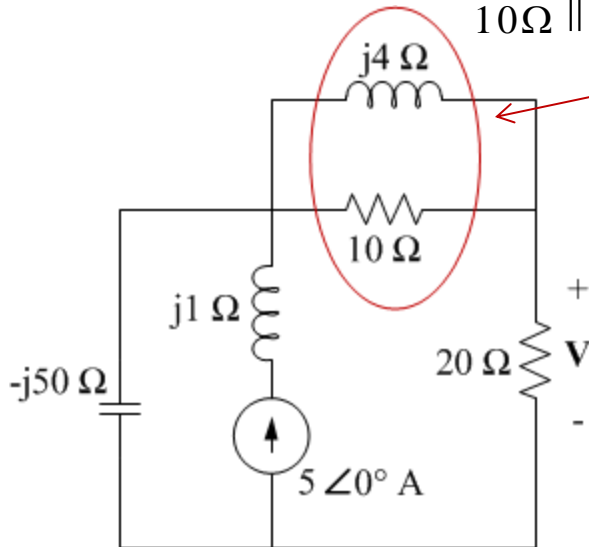
$$10 \Omega \parallel j4 \Omega = 3.71 \angle 68.20^\circ \Omega = 1.38 + j3.45 \Omega$$



Source Transformations

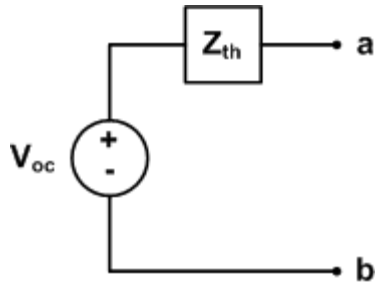



Thévenin Equivalent

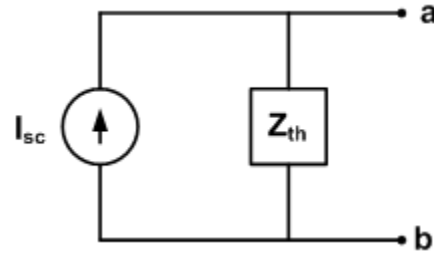



Norton Equivalent

$$V_{oc} = I_{sc} \cdot Z_{th}$$


Two special cases

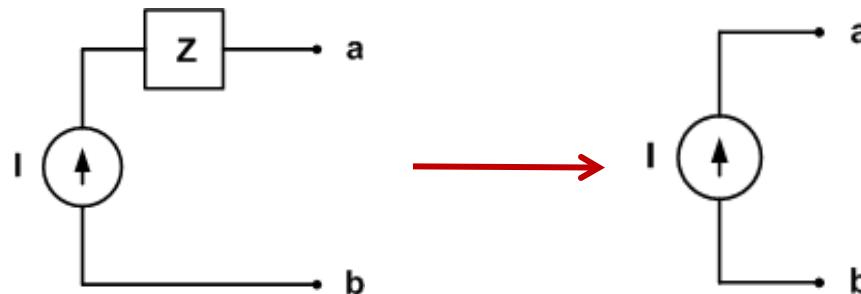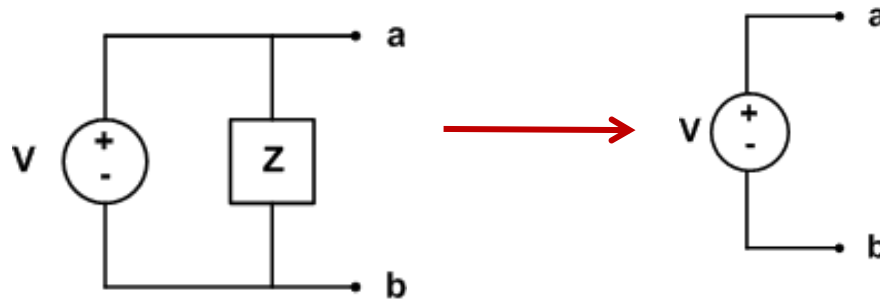

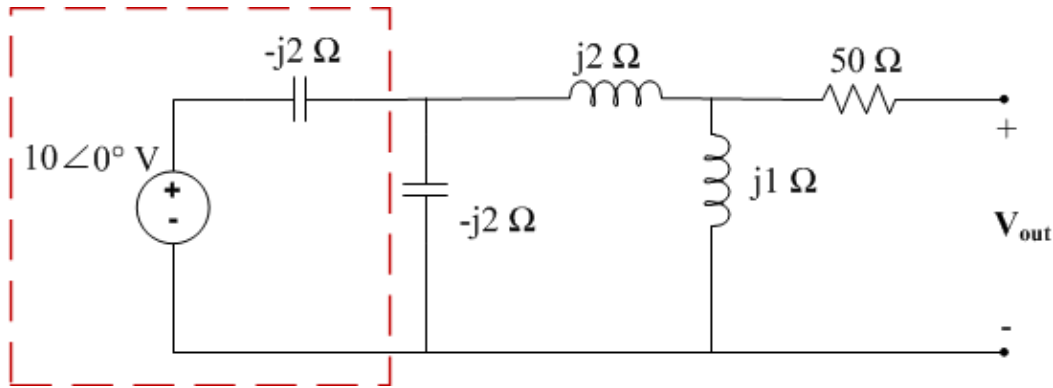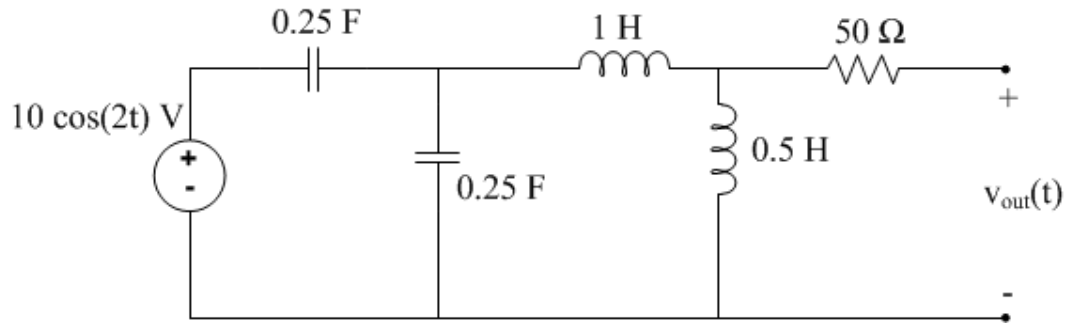
Example: Find the steady-state voltage, $v_{out}(t)$



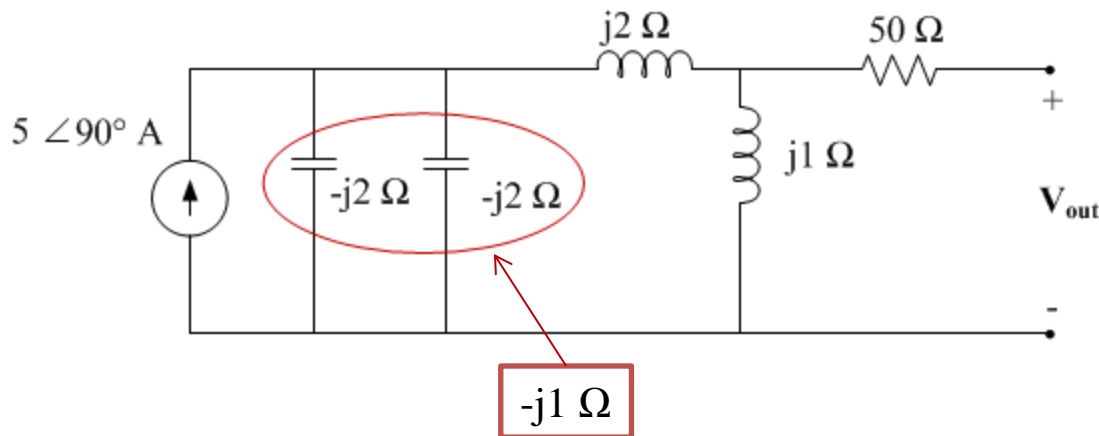
$$I = \frac{10 \angle 0^\circ}{-j2} = 5 \angle 90^\circ \text{ A}$$



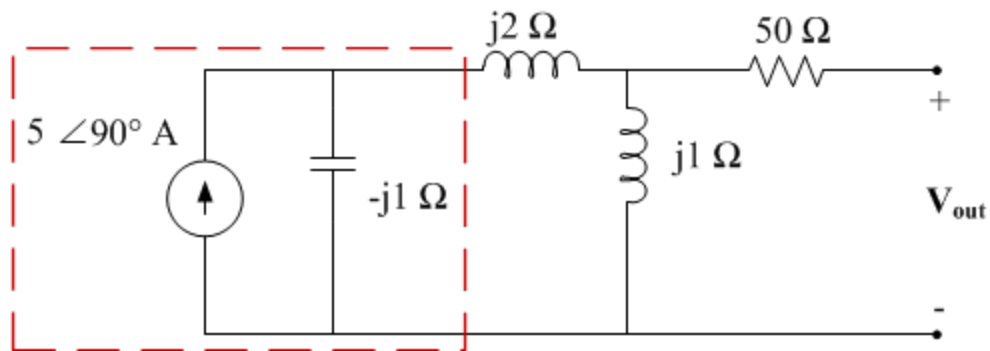
$$Z = \frac{1}{\frac{1}{-j2} + \frac{1}{-j2}} = -j1 \Omega$$



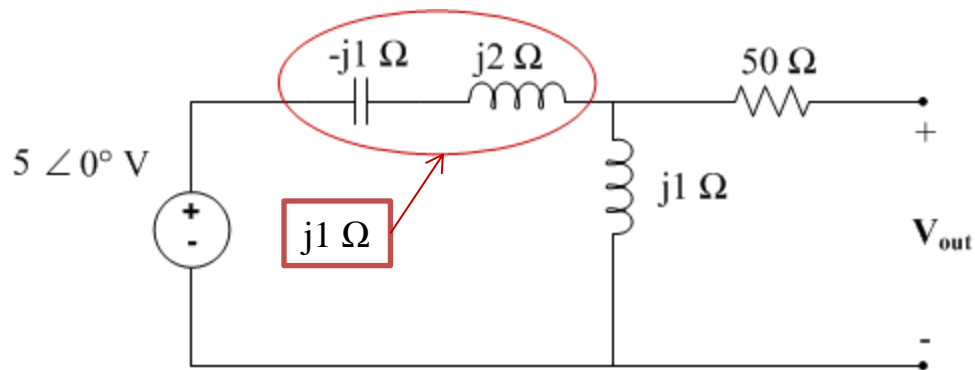
$$V = (5 \angle 90^\circ)(-j1) = 5 \angle 0^\circ \text{ V}$$




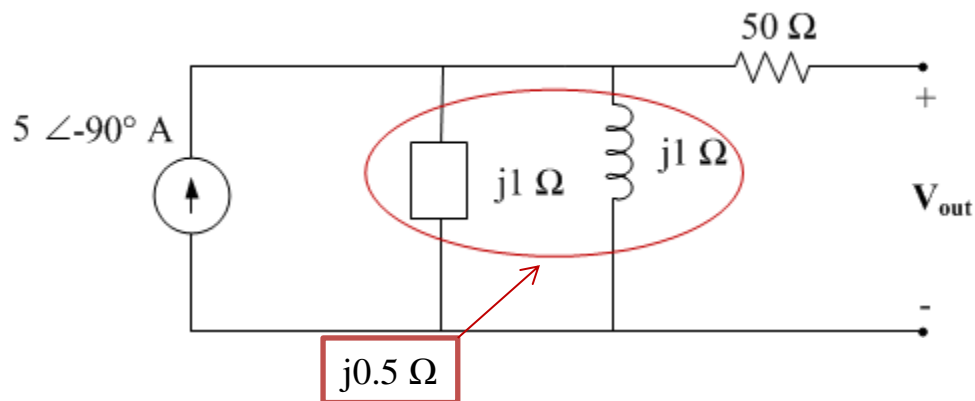
$$I = \frac{5 \angle 0^\circ}{j1} = 5 \angle -90^\circ \text{ A}$$


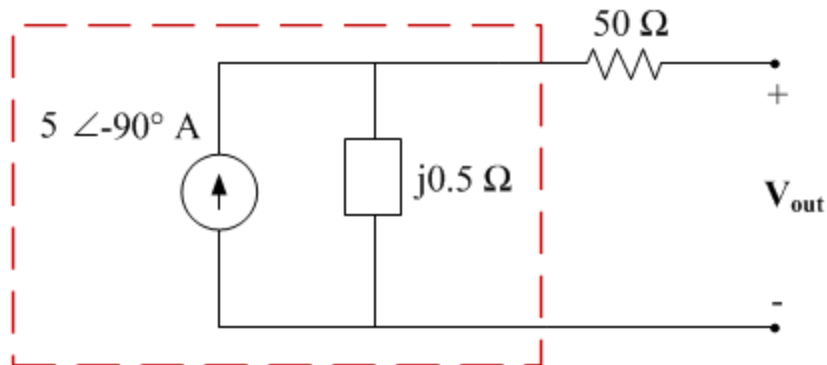
$$Z = \frac{1}{\frac{1}{j1} + \frac{1}{j1}} = j0.5 \Omega$$


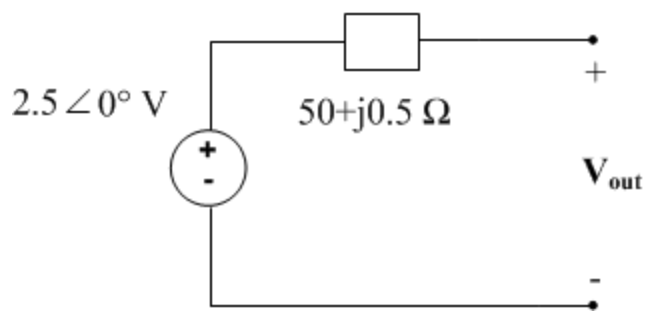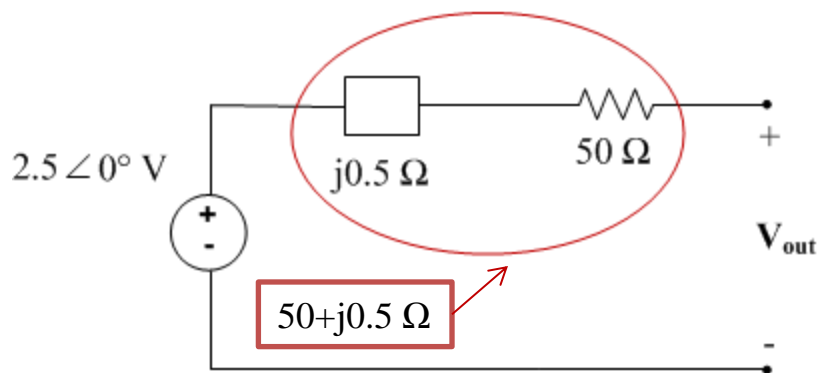
$$V = (5 \angle -90^\circ)(j0.5) = 2.5 \angle 0^\circ \text{ V}$$



Thévenin Equivalent

No current flows through the impedance

$$V_{\text{out}} = 2.5 \angle 0^\circ \text{ V}$$

$$v_{\text{out}}(t) = 2.5 \cos(2t) \text{ V}$$

AC Power

Complex Power

$$S = \frac{1}{2} \mathbf{V} \mathbf{I}^* = P + jQ$$

units = VA (volt-amperes)

Average Power

$$P = \frac{1}{2} V_m I_m \cos \theta$$

units = W (watts)

a.k.a. "Active" or "Real" Power

Reactive Power

$$Q = \frac{1}{2} V_m I_m \sin \theta$$

units = VAR
(volt-ampere reactive)

Power Factor

$$PF = \cos \theta$$

θ = impedance angle


leading or lagging

current is leading the voltage
 $\theta < 0$


current is lagging the voltage
 $\theta > 0$

Example:

$$v(t) = 2000 \cos(100t) \text{ V}$$

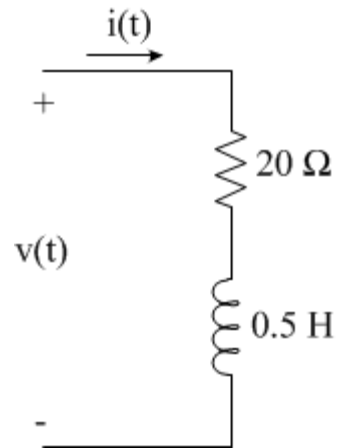
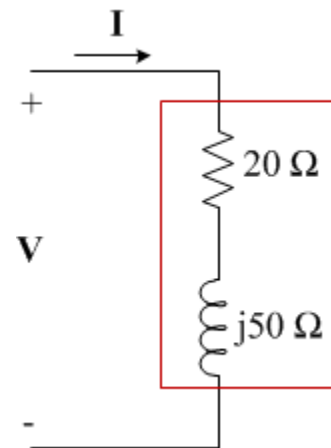
$$\mathbf{V} = 2000 \angle 0^\circ \text{ V}$$



$$\begin{aligned} \mathbf{Z} &= 20 + j50 \Omega \\ &= 53.85 \angle 68.20^\circ \Omega \end{aligned}$$

Current, \mathbf{I}

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{2000 \angle 0^\circ}{20 + j50} = 37.14 \angle -68.20^\circ \text{ A}$$

Power Factor

$$\text{PF} = \cos \theta = \cos(68.20^\circ) = 0.371 \text{ lagging}$$

Complex Power Absorbed

$$\begin{aligned} \mathbf{S} &= \frac{1}{2} \mathbf{V} \mathbf{I}^* = \frac{1}{2} (2000 \angle 0^\circ) (37.14 \angle +68.20^\circ) \\ &= 37139 \angle 68.20^\circ \text{ VA} \\ &= 13793 + j34483 \text{ VA} \end{aligned}$$

Average Power Absorbed

$$P = 13793 \text{ W}$$

Power Factor Correction



We want the power factor close to 1 to reduce the current.

Correct the power factor to 0.85 lagging

$$\theta_{\text{new}} = \cos^{-1} 0.85 = +31.79^\circ$$

Total Complex Power
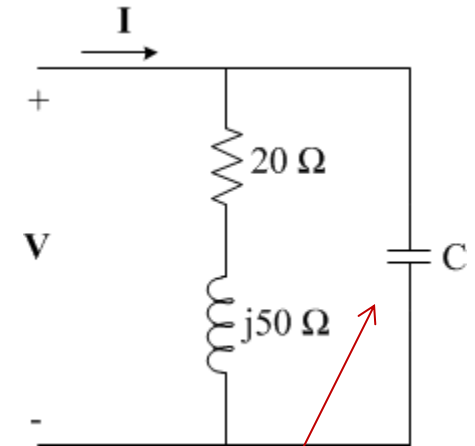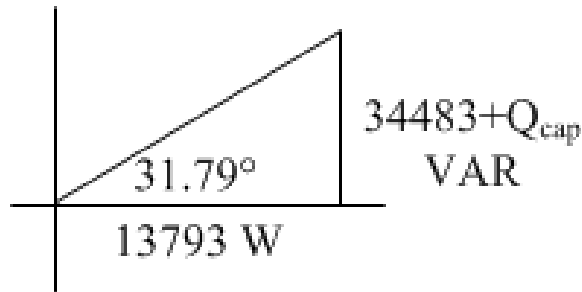
$$S_{\text{total}} = S + S_{\text{cap}} = (13793 + j34483) + (0 + jQ_{\text{cap}})$$



Add a capacitor in parallel with the load.

$$Q_{\text{cap}} = P \tan \theta_{\text{new}} - Q = 13793 \tan (31.79^\circ) - 34483 = -24934 \text{ VAR}$$

$$Q_{\text{cap}} = -25934 \text{ VAR} \rightarrow S_{\text{cap}} = -j25934 \text{ VA}$$

S for an ideal capacitor

$$S = -j \frac{1}{2} \omega C V_m^2$$

$$v(t) = 2000 \cos(100t) \text{ V}$$

$$-j25934 = -j \frac{1}{2} (100) C (2000)^2$$

$$C = 0.13 \text{ mF}$$

$$\begin{aligned} S_{\text{total}} &= S + S_{\text{cap}} = (13793 + j34483) + (0 - j25934) \\ &= 13793 + j8549 \text{ VA} = 16227.5 \angle 31.79^\circ \text{ VA} \end{aligned}$$

Without the capacitor

$$I = 37.14 \angle -68.20^\circ \text{ A}$$

Current after capacitor added

$$S = \frac{1}{2} \mathbf{V} \mathbf{I}^* \rightarrow \mathbf{I} = \left(\frac{2S}{\mathbf{V}} \right)^* = \left(\frac{2(13793 + j8549)}{2000 \angle 0^\circ} \right)^* = 16.23 \angle -31.79^\circ \text{ A}$$

RMS Current & Voltage

a.k.a. “Effective” current or voltage


$$V_{\text{rms}} = \left(\frac{1}{T} \int_0^T v^2 dt \right)^{1/2} \quad I_{\text{rms}} = \left(\frac{1}{T} \int_0^T i^2 dt \right)^{1/2}$$

RMS value of a sinusoid

$$A \cos(\omega t + \varphi) \rightarrow \frac{A}{\sqrt{2}}$$

$$P = V_{\text{rms}} \cdot I_{\text{rms}} \cos \theta$$

Balanced Three-Phase Systems

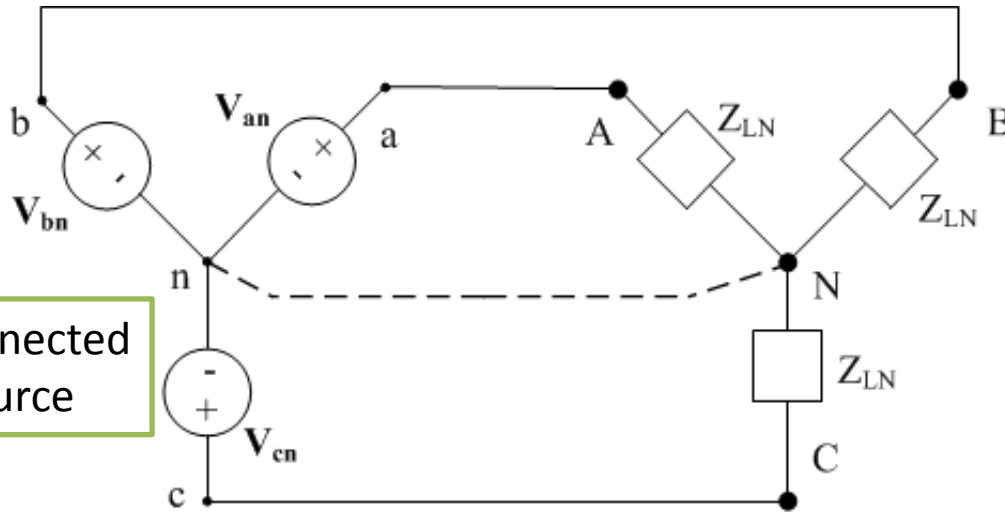

Y-connected source

Y-connected load

Line Voltages

$$\mathbf{V}_{ab} = \mathbf{V}_{an} - \mathbf{V}_{bn} = (\sqrt{3} \angle 30^\circ) \mathbf{V}_{an} = \mathbf{V}_L \angle \psi$$

$$\mathbf{V}_{bc} = \mathbf{V}_L \angle \psi - 120^\circ$$

$$\mathbf{V}_{ca} = \mathbf{V}_L \angle \psi + 120^\circ$$

Phase Voltages

$$\mathbf{V}_{an} = V_m \angle 0^\circ$$

$$\mathbf{V}_{bn} = V_m \angle -120^\circ$$

$$\mathbf{V}_{cn} = V_m \angle 120^\circ$$


Line Currents

$$\mathbf{I}_{aA} = \mathbf{I}_{AN} = \frac{\mathbf{V}_{AN}}{Z_{LN}} = I_L \angle \varphi$$

$$\mathbf{I}_{bB} = \mathbf{I}_{BN} = \frac{\mathbf{V}_{BN}}{Z_{LN}} = I_L \angle \varphi - 120^\circ$$

$$\mathbf{I}_{cC} = \mathbf{I}_{CN} = \frac{\mathbf{V}_{CN}}{Z_{LN}} = I_L \angle \varphi + 120^\circ$$

Balanced Three-Phase Systems

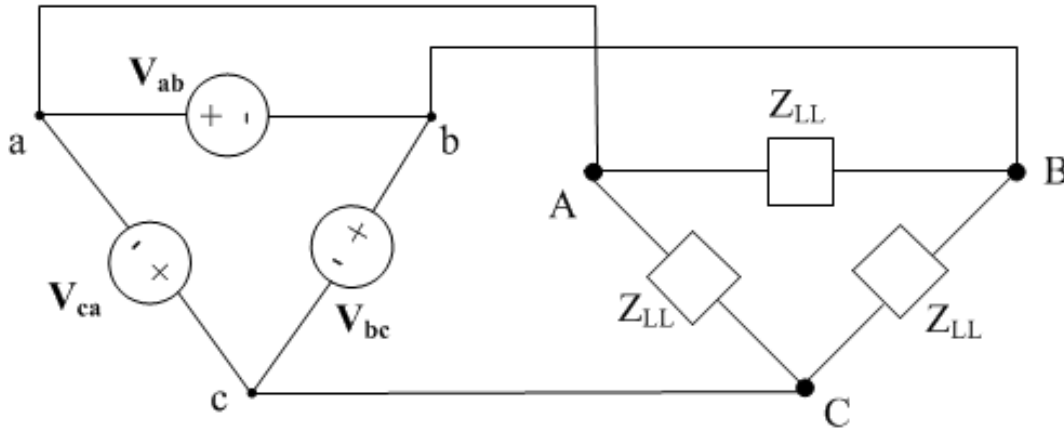

Δ -connected
source

Δ -connected
load

Line Currents

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA} = (\sqrt{3} \angle -30^\circ) \mathbf{I}_{AB} = I_L \angle \psi$$

$$\mathbf{I}_{bB} = I_L \angle \psi - 120^\circ$$

$$\mathbf{I}_{cC} = I_L \angle \psi + 120^\circ$$

Line Voltages

$$\mathbf{V}_{ab} = V_m \angle 0^\circ$$

$$\mathbf{V}_{bc} = V_m \angle -120^\circ$$

$$\mathbf{V}_{ca} = V_m \angle 120^\circ$$

Phase Currents

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{Z_{LL}} = I_L \angle \varphi$$

$$\mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{Z_{LL}} = I_L \angle \varphi - 120^\circ$$

$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{Z_{LL}} = I_L \angle \varphi + 120^\circ$$

Currents and Voltages are specified in RMS

$$S = \frac{1}{2} \mathbf{V} \mathbf{I}^* \rightarrow S = \mathbf{V} \mathbf{I}^* \rightarrow S = 3 \mathbf{V} \mathbf{I}^*$$

S for peak
voltage
& current

S for RMS
voltage
& current

S for 3-phase
voltage
& current

$$\begin{aligned} V_L &= \text{line voltage} = |\mathbf{V}_{ab}| \\ I_L &= \text{line current} = |\mathbf{I}_{aA}| \\ \theta &= \text{impedance angle} = \angle Z \end{aligned}$$

Average Power

$$P = \sqrt{3} V_L I_L \cos \theta$$

Complex Power
for Y-connected load

$$\begin{aligned} S &= 3 \mathbf{V}_{AN} \mathbf{I}_{AN}^* \\ &= \sqrt{3} V_L I_L \angle \theta \end{aligned}$$

Complex Power
for Δ -connected load


$$\begin{aligned} S &= 3 \mathbf{V}_{AB} \mathbf{I}_{AB}^* \\ &= \sqrt{3} V_L I_L \angle \theta \end{aligned}$$

Power Factor

$$\text{PF} = \cos \theta \quad (\text{leading or lagging})$$

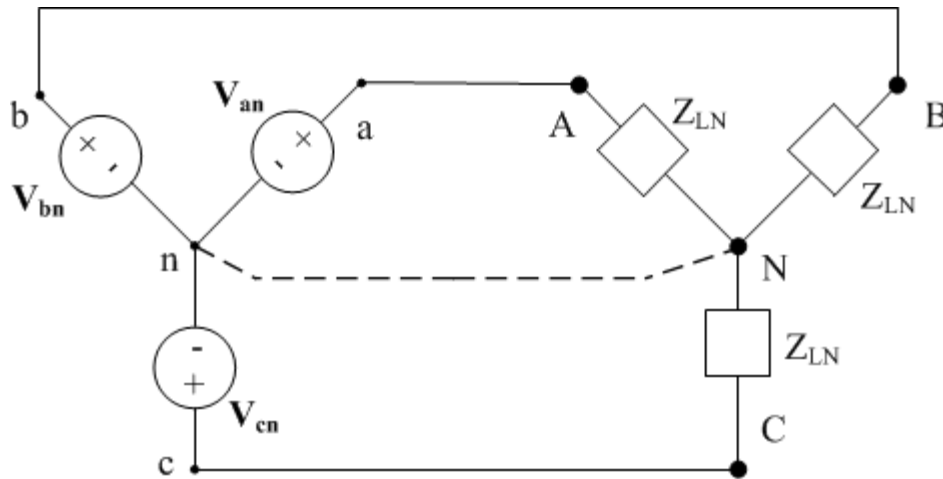Example:

Find the total real power supplied by the source in the balanced wye-connected circuit



Given:

$$\mathbf{V}_{an} = 540 \angle 0^\circ \text{ V}$$


$$\mathbf{Z}_{LN} = 270 + j270 \ \Omega$$

$$\mathbf{I}_{aA} = \mathbf{I}_{AN} = \frac{\mathbf{V}_{AN}}{\mathbf{Z}_{LN}} = \frac{540 \angle 0^\circ}{270 + j270} = 1.41 \angle -45^\circ \text{ A}$$

$$\mathbf{S} = 3 \mathbf{V}_{AN} \mathbf{I}_{AN}^* = 3 (540 \angle 0^\circ) (1.41 \angle 45^\circ) = 2291 \angle 45^\circ \text{ VA} = 1620 + j1620 \text{ VA}$$

$$P = 1620 \text{ W}$$

Ideal Operational Amplifier (Op Amp)

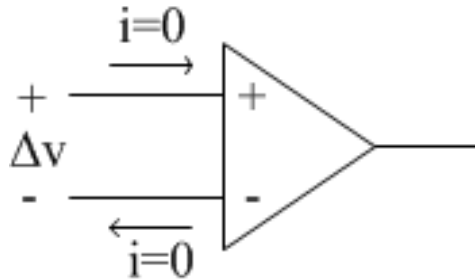


With negative feedback

$$i=0$$

$$\Delta v=0$$

Linear Amplifier

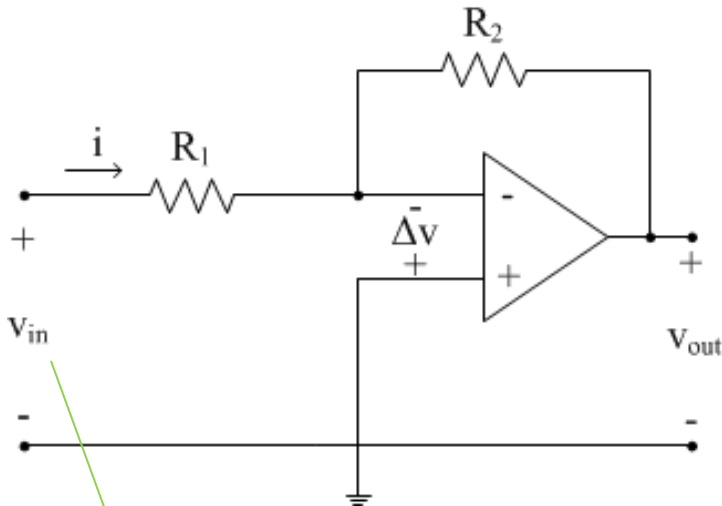

$$\text{KVL: } -v_{in} + R_1 i - \overset{0}{\Delta v} = 0 \rightarrow i = \frac{v_{in}}{R_1}$$

$$\text{KVL: } -v_{in} + R_1 i + R_2 i + v_{out} = 0$$

$$-v_{in} + R_1 \left(\frac{v_{in}}{R_1} \right) + R_2 \left(\frac{v_{in}}{R_1} \right) + v_{out} = 0$$

$$v_{out} = -\frac{R_2}{R_1} v_{in}$$

mV or μ V reading from sensor

0-5 V output to A/D converter

Magnetic Fields

$$\oint_s \mathbf{B} \cdot d\mathbf{s} = 0$$

$$\oint_l \mathbf{H} \cdot d\mathbf{l} = \oint_s \mathbf{J} \cdot d\mathbf{S} = I$$

Net magnetic flux through a closed surface is zero.

B – magnetic flux density (tesla)
H – magnetic field strength (A/m)
J - current density

$$\mathbf{B} = \mu \mathbf{H}$$

Magnetic Flux ϕ passing through a surface

$$\phi = \int_s \mathbf{B} \cdot d\mathbf{S}$$

Energy stored in the magnetic field

$$w = \frac{1}{2} \iiint_v \mu |\mathbf{H}|^2 dV$$

Enclosing a surface with N turns of wire produces a voltage across the terminals

$$v = -N \frac{d\phi}{dt}$$

Magnetic field produces a force perpendicular to the current direction and the magnetic field direction

$$\mathbf{F} = I\mathbf{L} \times \mathbf{B}$$


Example:

A coaxial cable with an inner wire of radius 1 mm carries 10-A current. The outer cylindrical conductor has a diameter of 10 mm and carries a 10-A uniformly distributed current in the opposite direction. Determine the approximate magnetic energy stored per unit length in this cable. Use μ_0 for the permeability of the material between the wire and conductor.

$$\int \mathbf{H} \cdot d\mathbf{l} = H_{\phi} 2\pi r = I_0 = 10 \text{ A}$$


$$H_{\phi} = \frac{10}{2\pi r} \quad \text{for} \quad 10^{-3} \text{ m} < r < 10^{-2} \text{ m}$$

$$w = \frac{1}{2} \iiint_V \mu |\mathbf{H}|^2 dV = \frac{1}{2} \int_0^1 \int_0^{2\pi} \int_{0.001}^{0.01} \mu_0 \left(\frac{10}{2\pi r} \right)^2 r dr d\phi dz = 18.3 \mu_0 \text{ J}$$

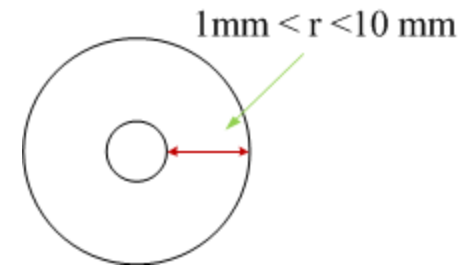

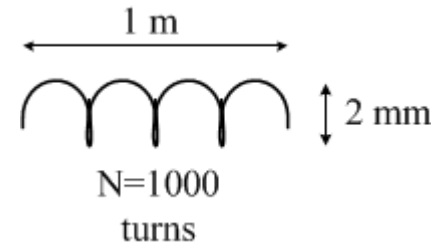Example:

A cylindrical coil of wire has an air core and 1000 turns. It is 1 m long with a diameter of 2 mm so has a relatively uniform field. Find the current necessary to achieve a magnetic flux density of 2 T.



$$\int \mathbf{H} \cdot d\mathbf{l} = NI_0$$

$$HL = NI_0$$

$$\left(\frac{B}{\mu_0} \right) L = NI_0 \rightarrow I = \frac{BL}{N\mu_0} = \frac{(2\text{T})(1\text{m})}{1000(4\pi \times 10^{-7})} = 1590 \text{ A}$$

Questions?

