

EE213

WIMP51

Adding
Bit Addressable Internal Registers
to the Wimp51

*Cooperative Engineering Program:
Missouri University of Science & Technology &
Missouri State University*

under the direction of

Professor Rohit Dua PhD

Abstract: Starting with a simple FPGA based processor of the Von Neumann Architecture design called Wimp51 (Weekend Instructional Micro Processor), the group implemented the added capability of a Bit Addressable Register.

Table of Contents

Abstract	2
Table of Contents	2-3
Introduction	3
Chosen Design	4
Description of Work	4
Figures	4-8
Register_Top (figure 1)	4
REG_we (figure 2)	5
Register_Top (figure 3)	5
Bit_Address_en (figure 4)	5
Reg_in (figure 5)	6
PC_ALU (figure 6)	6
AUX_WE (figure 7)	7
BIT_SEL_CONTROL (figure 8)	7
Register (figure 9)	8
Operation Code	9
Conclusion	10

Introduction

This project was designed with the intent of having participants become intimately familiar with the internal functions of a simple processor. To accomplish this the group was provided with a simple WIMP51 processor designed on an Altera DE2 FPGA board with the assignment of designing and implementing additional functionality to the processor.

Chosen design

The project approved was to add bit addressability to the internal registers. The original Wimp51 was built such that the entire value of each register was set at once. With this design the value of bit can be set or cleared as desired.

Description of work

In order to
instructio
recognize
differentl
design. T

Registe

In the ori
accumula
selected.
desired. I
2nd_regi

Bit_Ad

The Bit A
decodes i
available

REG_in

When the
the 8-2-1

PC_ALU

Inside the PC_A
increment on the
set.

AUX_WE

In this block, fig
device detects th

BIT_SEL_C

The BIT_SEL_C
which 8 are loca
each register

e used. This required
, logic had to be created to
ypical input and would be routed
ed in order to implement this

ive a full byte from the
f these registers could not be
ster can be set or cleared as
g the bits in and in figure_2, the

input of an instruction pair and
d set of an instruction pair is

the output will go low. This tells
the Standard Register

ve the program counter
of a two byte instruction

ode requirements. When this
h the data at the inputs

de of each Register, of
lect the individual bits of

REG_we

Decoding of our
 able to store the
 wouldn't save a

so that we would be
 in the AUX, but it

Register

The Register, f
 BIT_SEL_COM

on of 8
 n in each register.

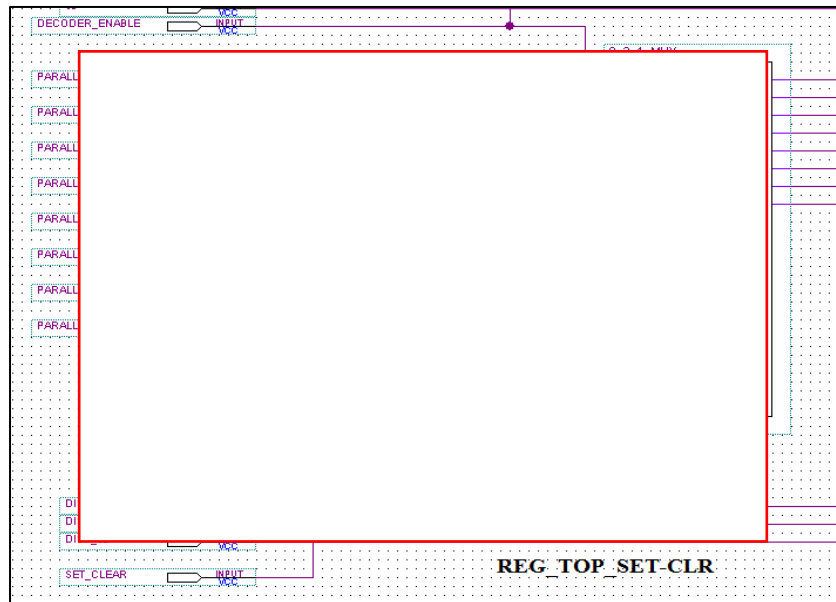


Figure 1: Register_Top (8-2-1 MUX controls each bit of the selected register)

 


Figure 2: REG_we (Decoding for storing the bit in REG_TOP)

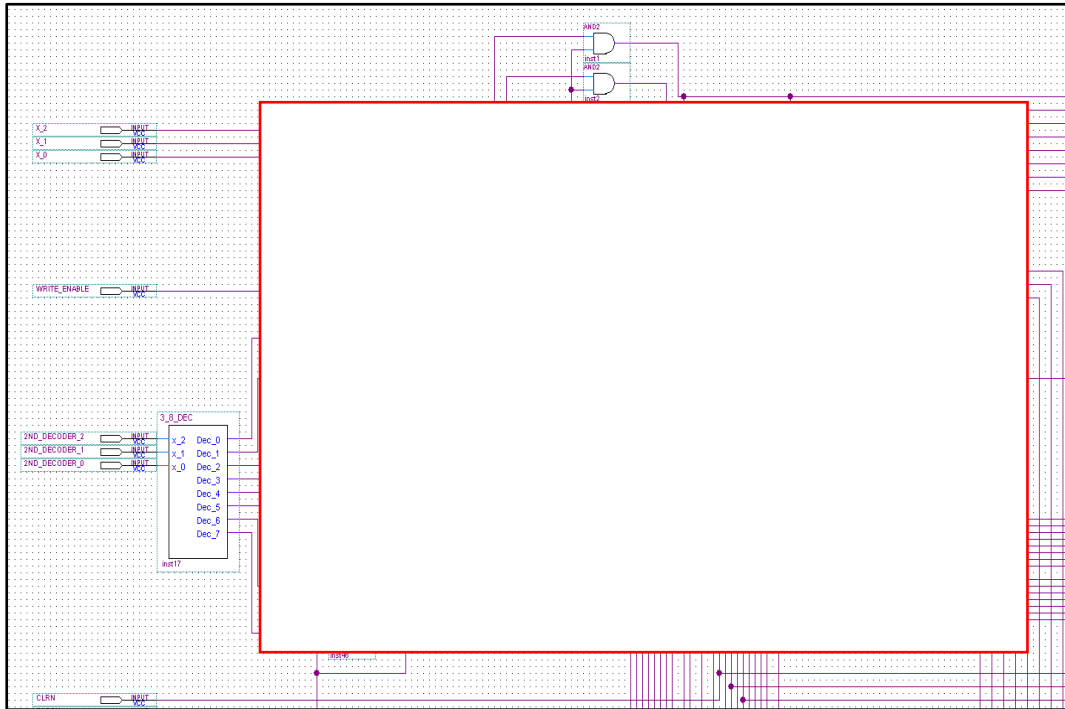


Figure 3: Register_Top (2nd_Decoder provides each bit)

 


Figure 4: Bit Address Enable

 


Figure 5: Register In

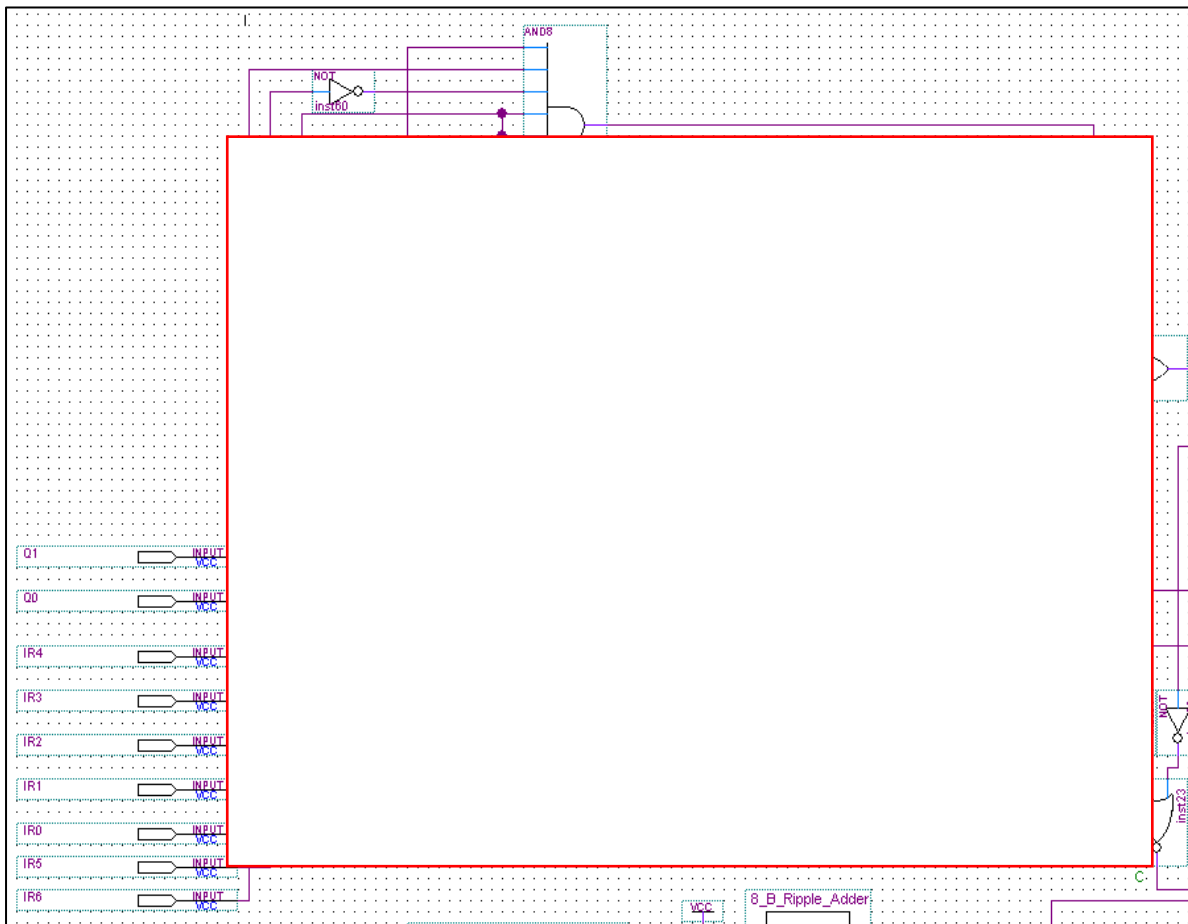


Figure 6: Inside PC ALU

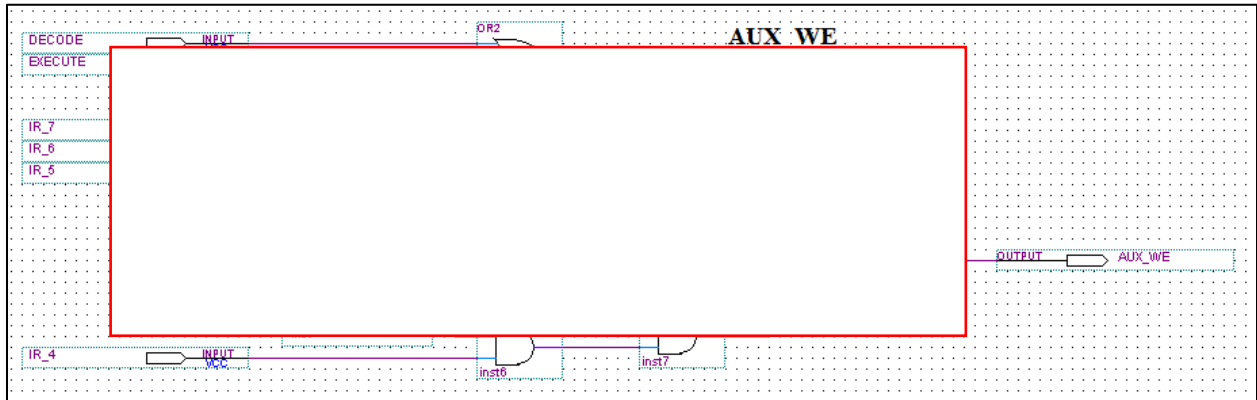


Figure 7: AUX_WE

 


Figure 8: BIT_SEL_CONTROL

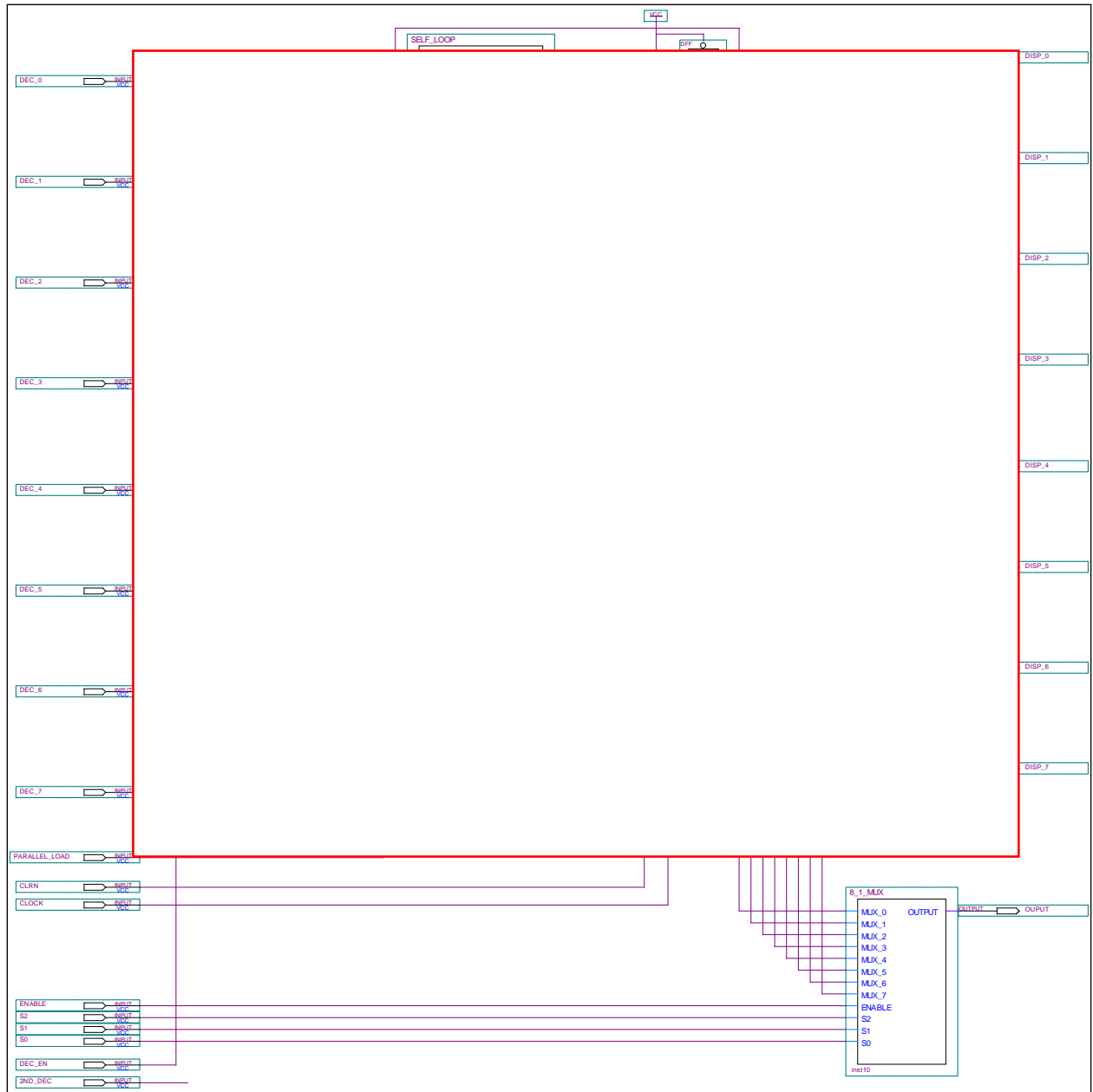


Figure 9: Register


```

;=====
;                               Test Code for Setting and Clearing Internal Registers
;=====
00H      DFH   SETB R7.7           ; R7=80,           1000 0000
01H      0FH
02H      DEH   SETB R6.6           ; R6=40,           0100 0000
03H      0EH
04H      DDH   SETB R5.5           ; R5=20,           0010 0000
05H      0DH
06H      DCH   SETB R4.4           ; R4=10,           0001 0000
07H      0CH
08H      DBH   SETB R3.3           ; R3=08,           0000 1000
09H      0BH
0AH      DAH   SETB R2.2           ; R2=04,           0000 0100
0BH      0AH
0CH      D9H   SETB R1.1           ; R1=02,           0000 0010
0DH      09H
0EH      D8H   SETB R0.0           ; R0=01,           0000 0001
0FH      08H
10H      EFH   MOV A,R7            ; A = R7 = 80,     1000 0000
11H      4DH   ORL A,R5            ; A = A0 =         1010 0000
12H      C4H   SWAP A              ; A = 0A =         0000 1010
13H      34H   ADDC A, #96         ; A = A0 =         1010 0000
14H      96H
15H      C3H   CLR C               ; Clear Carry
16H      3BH   ADDC A, R3          ; A = A8 =         1010 1000
17H      49H   ORL A, R1          ; A = AA =         1010 1010
18H      F8H   MOV R0, A          ; R0 = AA
19H      74H   MOV A, #55         ; A = 55 =         0101 0101
1AH      55H
1BH      68H   XRL A, R0           ; A = FF =         1111 1111
1CH      F8H   MOV R0, A          ; R0 = FF =         1111 1111
1DH      D8H   SETB_C R0.7        ; R0 = 7F =         0111 1111
1EH      07H
1FH      D8H   SETB_C R0.6        ; R0 = 3F =         0011 1111
20H      06H
21H      D8H   SETB_C R0.5        ; R0 = 1F =         0001 1111
22H      05H
23H      D8H   SETB_C R0.4        ; R0 = 0F =         0000 1111
24H      04H
25H      D8H   SETB_C R0.2        ; R0 = 0B =         0000 1011
26H      02H
27H      D8H   SETB_C R0.0        ; R0 = 0A =         0000 1010
28H      00H
29H      58H   ANL A, R0          ; A = 0A =         0000 1111
2AH      F8H   MOV R0,A          ; R0 = A = 0A =     0000 1010
2BH      74H   MOV A, #00         ; A = 0
2CH      00H
2DH      60H   JZ 03              ; Jump 3
2EH      03H
32H      80H   SJMP HALT
33H      FEH

```

Conclusion:

After drafting and programming the bit addressability to the WIMP51, a deep insight to the inner processes of the 8051 architecture was gained. Due to our initial lack of knowledge, many timing and gate errors were made; causing a better understanding of the internal operations and general flow of the microprocessor.