

figure – 2 (Class A Input to the Op-Amp, and Output from the power amplifier)

Class B Amplifier

After the class B amplifier was built and connected to the DC Power Supply the output signal showed



bipolar transistors. Both transistors have
input signal will supply the turn on
the FFT the frequencies that compose the
frequency. In figure-5 the 1st Harmonic
4. From this graph (figure-5) the total



figure – 3 (Class B amplifier diagram)

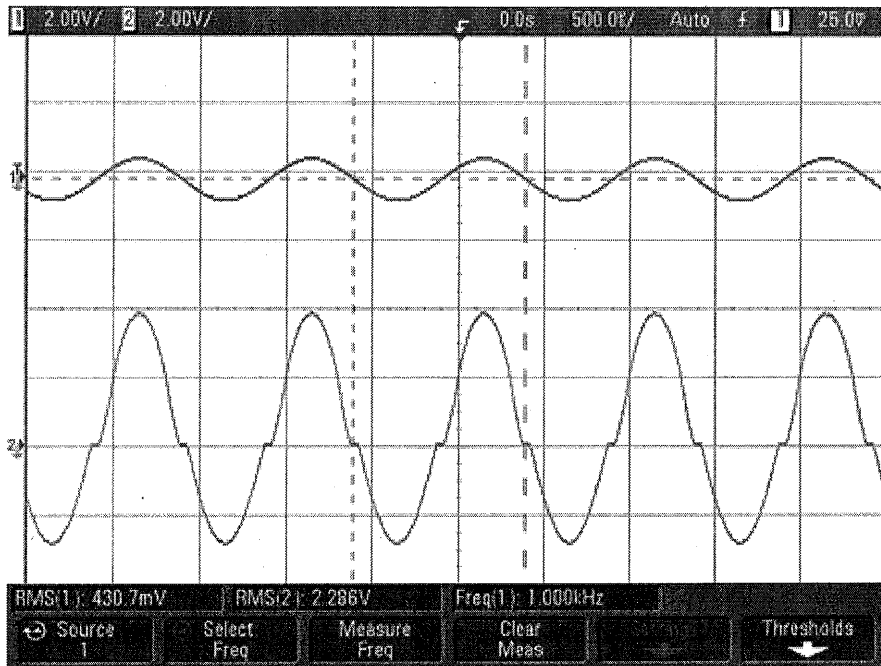


Figure – 4 (Class B input and output to the Op Amp)

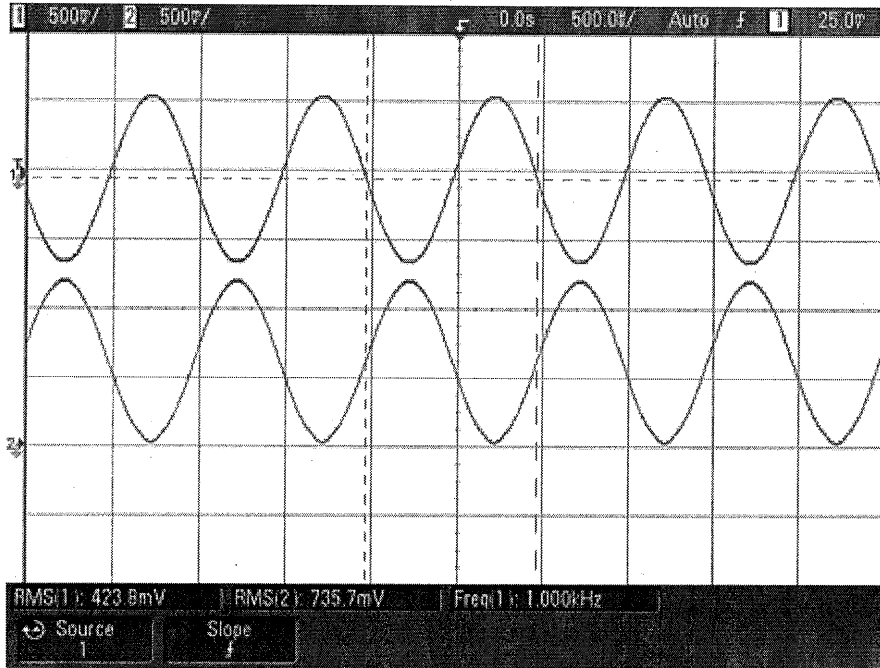


Figure – 7 (Class AB Amplifier Output Ch2, Op Amp Input Ch1)