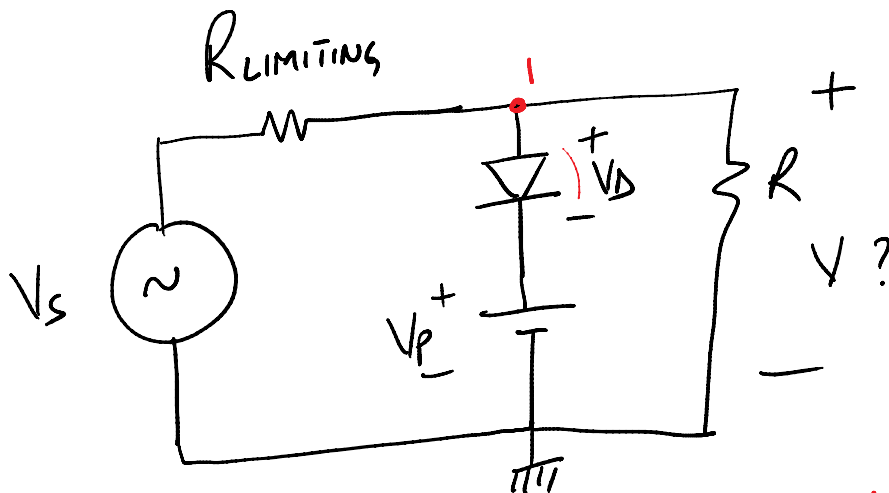


LECTURE-19

DIODE AS A CLIPPER OR LIMITER

DIODE \rightarrow TURN ON VOLTAGE V_{to}
REVERSE SAT. CURRENT I_0
 $-I_0$




WHEN THE DIODE ~~IS~~ IS TURNED ON
 $V_D = V_{to}$

① $V_s < \underbrace{(V_{to} + V_p)}_V \rightarrow$ DIODE AND V_p ACT AS OPEN CIRCUIT $\therefore V$ FOLLOWS V_s

② $V_s > (V_{to} + V_p) +$ SOME DROP ACROSS $R_{LIMITING}$

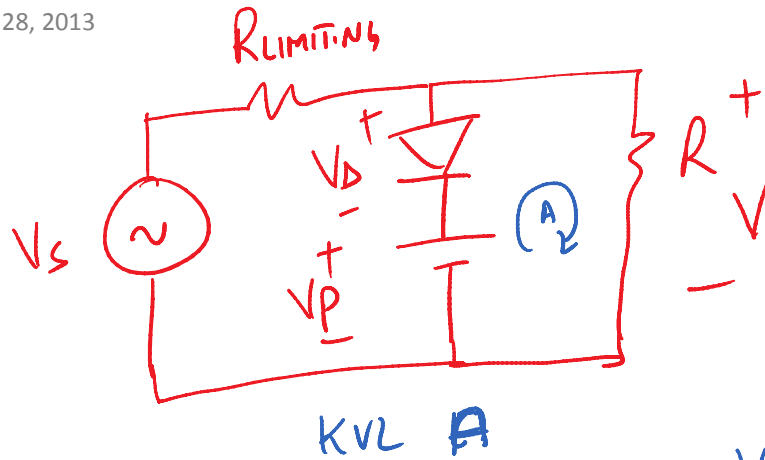DIODE IS ON \rightarrow OUTPUT IS CLIPPED TO
 $V_{to} + V_p = V$




$$-V_p - V_D + V = 0$$

$$V = V_p + V_D$$

IF DIODE IS ON $\therefore V_D = V_{to}$

$$\therefore V = V_{to} + V_p$$

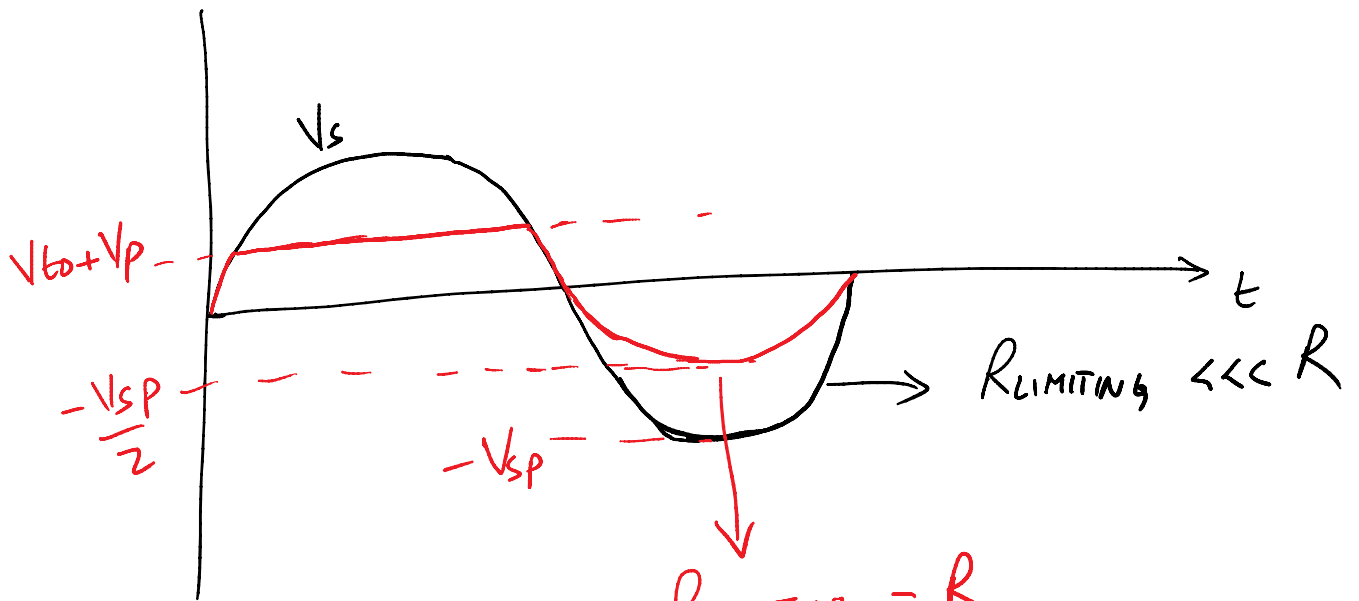

$$R_{LIMITING} = R$$

WHEN DIODE IS OFF





$$V = \frac{V_s R}{R_{LIMIT} + R}$$

$\therefore V$





KUMPI ...
 $V = \frac{1}{2} V_s$



Monday, January 28, 2013
10:55 AM

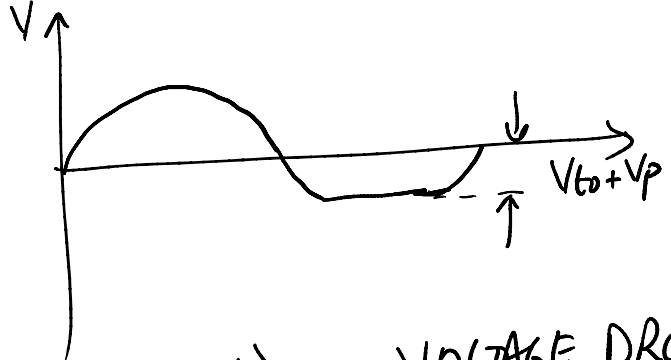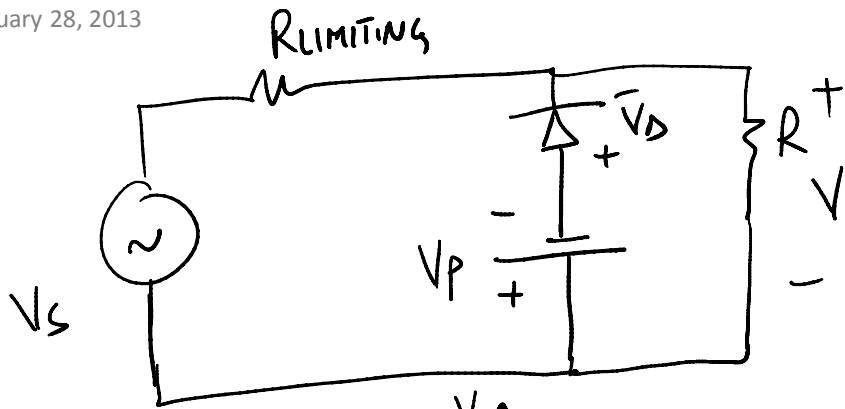

- * IF $V_s < -(V_{to} + V_p)$ - VOLTAGE DROP ACROSS R_{LIMIT} IS CLIPPED TO $-(V_{to} + V_p)$
- * IF $V_s > -(V_{to} + V_p)$ THEN DIODE IS OFF!

Monday, January 28, 2013
10:58 AM

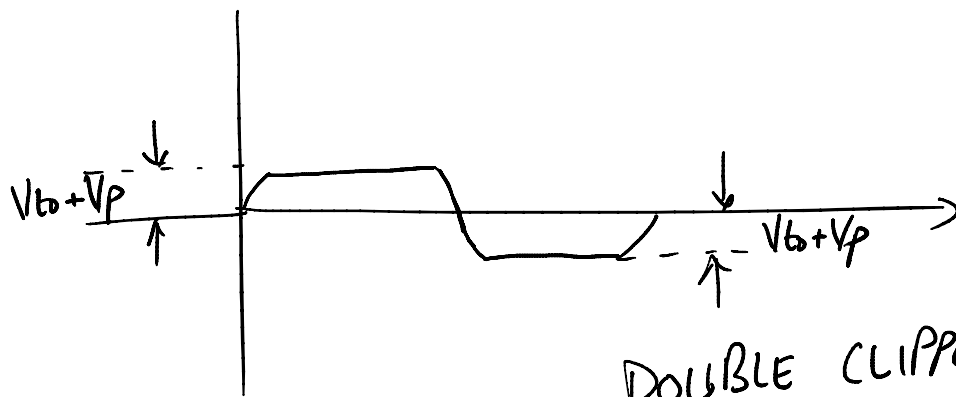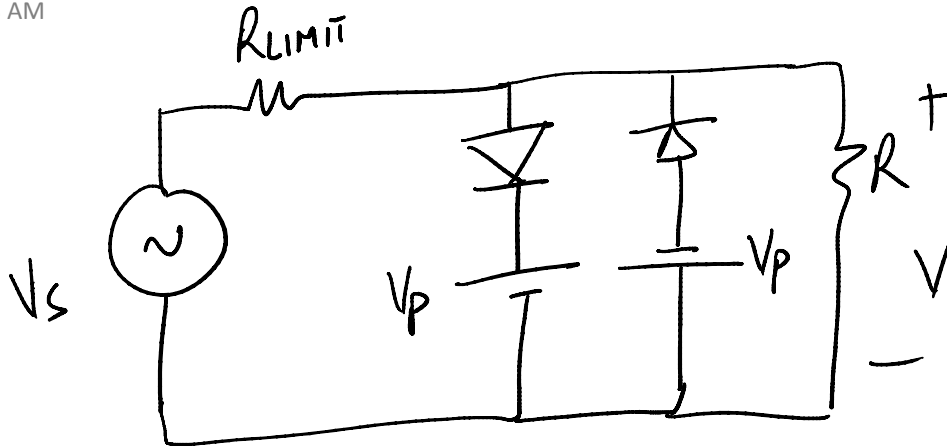

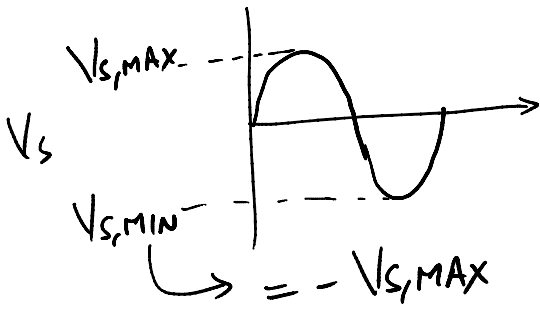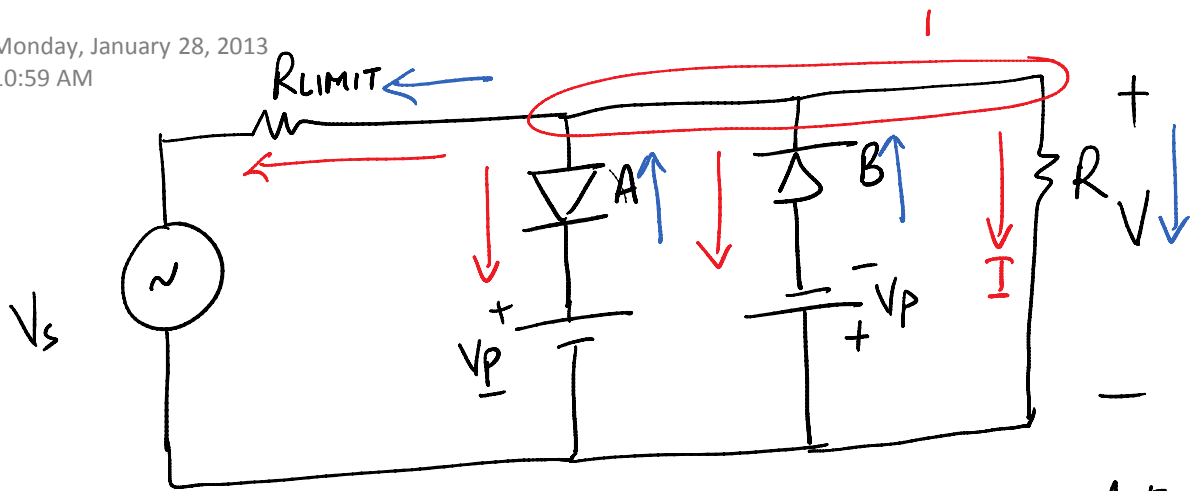

TURN-ON VOLTAGE = V_{to}
REVERSE SAT. CURRENT = $-I_0$

DIODE IS ON IF $|V| = |V_{to} + V_p|$
DIODE IS OFF IF $|V| < |V_{to} + V_p|$

SOURCE $|V_s| > |V_{to} + V_p|$

$$(1) \quad V_{s,MAX} \Rightarrow V_s = V_{s,MAX} \quad \begin{array}{l} A \text{ IS FB} \\ B \text{ IS RB} \end{array}$$

$$V_{D,A} = V_{to,A} \Rightarrow V = V_{to,A} + V_p$$

$$I_{D,B} = -I_{0,B}$$

$$I = V/R = \frac{(V_{to,A} + V_p)}{R}$$

KCL NODE 1

$$\frac{V - V_{s,MAX}}{R_{LIMIT}} + I_{D,A} + I_{D,B} + \frac{V}{R} = 0$$

$$I_{D,A} = - \left(\frac{V - V_{s,MAX}}{R_{LIMIT}} \right) - I_{D,B} - \frac{V}{R}$$

2) FOR $V_S = -V_{S,MAX}$
DIODE A IS RB, DIODE B IS FB

$$\bar{I}_{D,A} = -I_{0,A}$$

$$V_{D,B} = V_{t0,B}$$


$$V = - (V_{t0,B} + V_P)$$

$$I = \frac{V}{R} = - \frac{(V_{t0,B} + V_P)}{R}$$

KCL AT NODE 1 TO FIND $\bar{I}_{D,B}$

$$\frac{V + V_{S,MAX}}{R_{LIMIT}} - \bar{I}_{D,B} - I_{0,A} + \frac{V}{R} = 0$$
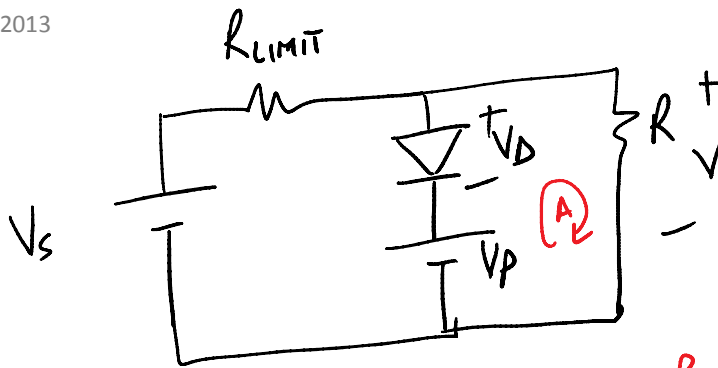
$$\bar{I}_{D,B} = \frac{V + V_{S,MAX}}{R_{LIMIT}} - I_{0,A} + \frac{V}{R}$$




KVL LOOP (A)

$$-V_P - V_D + V = 0$$

$$V = V_P + V_D$$

① $R_{LIMIT} = 0$

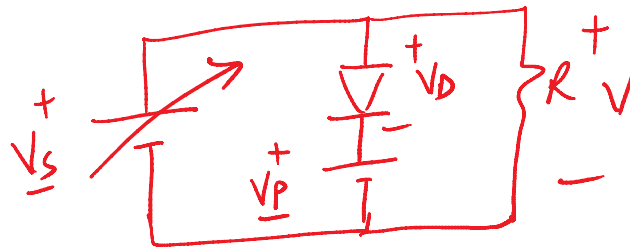


$$V_D = 0.7V$$

IF $V_S > 0.7 + V_P \quad \therefore V = V_P + 0.7V$

$V_S < 0.7 + V_P \quad \rightarrow$ DIODE IS OFF (OPEN CIRCUIT)

$V = V_S$

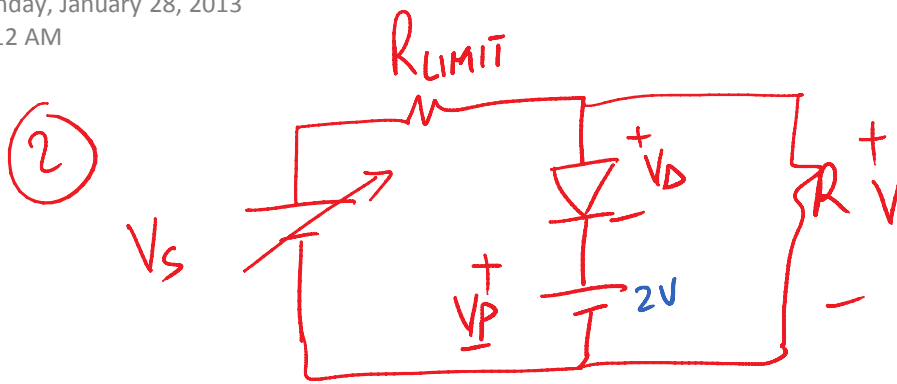

$V_{to} = 0.7V$
 $V = V_{to} + V_P = 2.7V$

$R_{LIMIT} = R$

V_s	V	V_D	$V_{R_{LIMIT}}$
0	0		0
0.5	0.25		0.25
2	1		1
6	2.7	0.7	3.3
10V	2.7	0.7	7.3