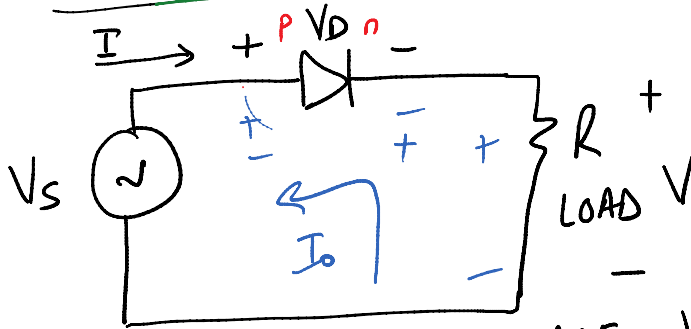



LECTURE - 20

RECTIFIER CIRCUITS → CONVERT AC TO DC

HALF WAVE RECTIFIER (HWR)



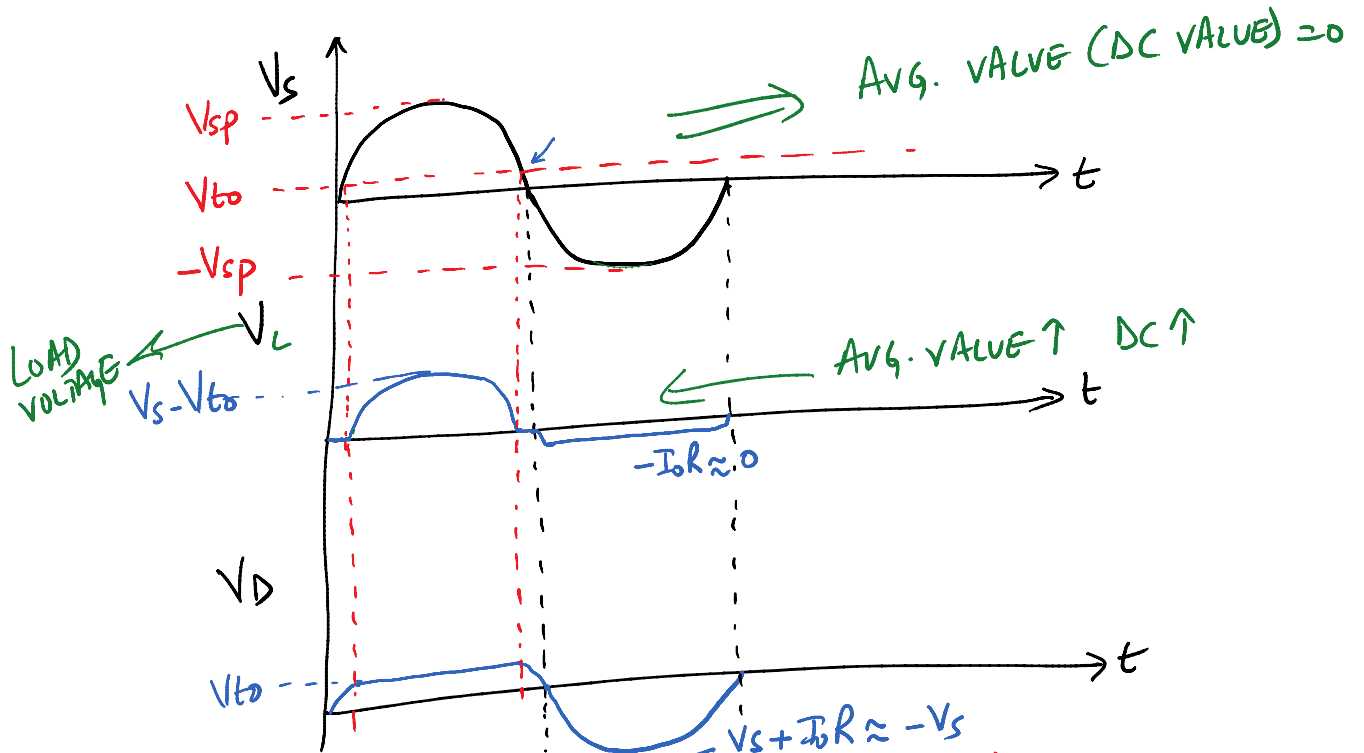- * TURN ON VOLTAGE V_{to}
- * REVERSE SATURATION CURRENT I_o




* FB → DIODE CONDUCTS (TURNS-ON) WHEN $V_s > V_{to}$

GOAL → DC VOLTAGE
f=0

GOAL \rightarrow 

HALF WAVE RECTIFIER WITH ~~EE~~ FILTER

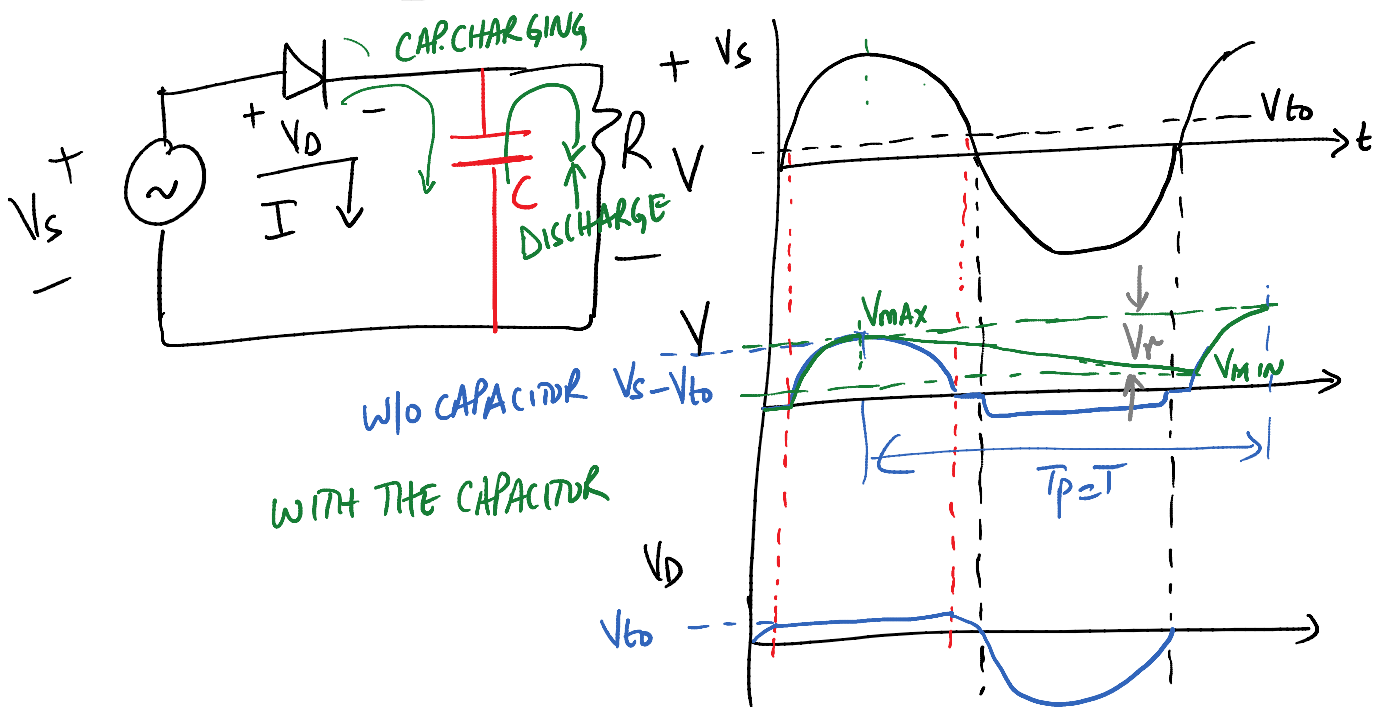

$C \rightarrow$ CAPACITOR IS THE FILTER CIRCUIT

CHARGING AND DISCHARGING OF CAPACITOR EFFECTIVELY INCREASES THE DC VALUE OF ~~THE~~ LOAD VOLTAGE
AVERAGE VALUE


DISCHARGE RATE DEPENDS UPON RC TIME CONSTANT

$$\tau = RC$$

DESIGN \leftarrow V_r \rightarrow RIPPLE VOLTAGE = $V_{max} - V_{min}$

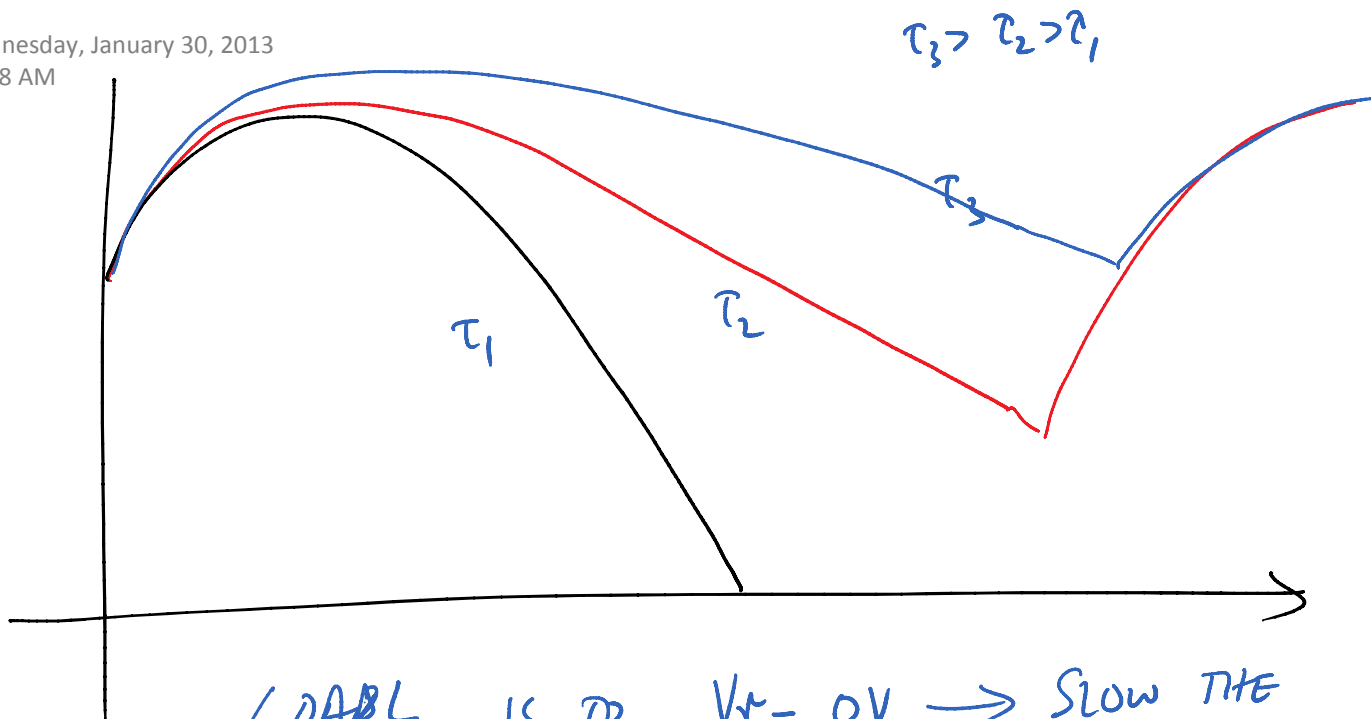\leftarrow GOAL $\rightarrow V_r \downarrow \downarrow$







GOAL IS TO $V_r = 0V \rightarrow$ SLOW THE DISCHARGE OR INCREASE τ

$$V_r = V_m \left(\frac{T_p}{RC} \right)$$

$T_p \rightarrow V_m =$ MAXIMUM OUTPUT VOLTAGE
HWR $T_p = T$
FWR $T_p = \frac{T}{2}$

$T_p \Rightarrow$ TIME BETWEEN PEAKS OF OUTPUT VOLTAGE
 $T \Rightarrow$ TIME PERIOD

FWR → FULL WAVE BRIDGE RECTIFIER

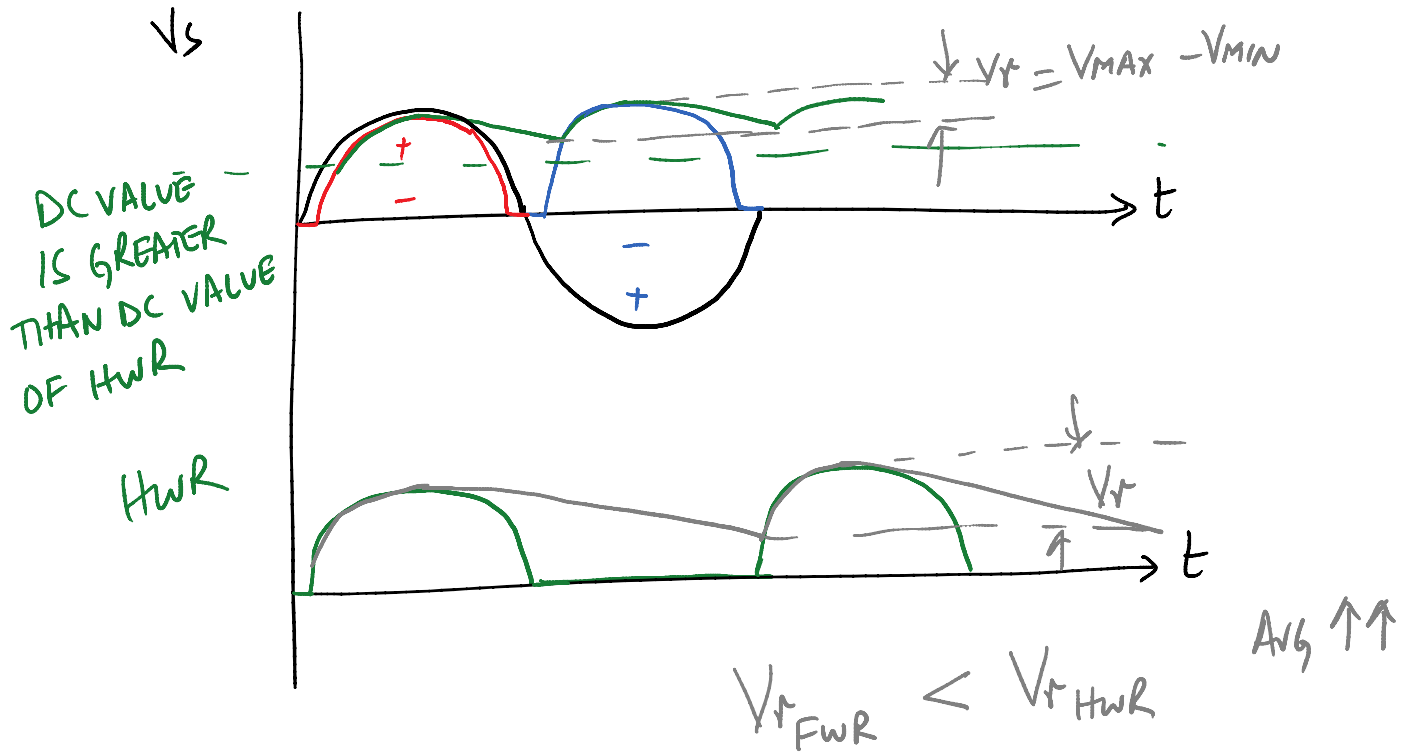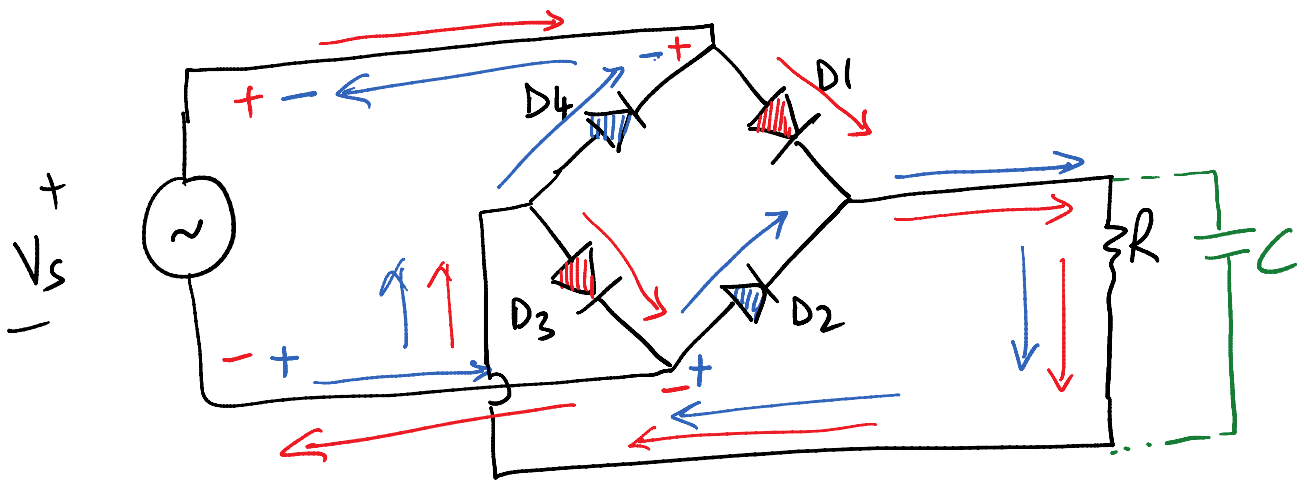

RIPPLE VOLTAGE FOR FWR IS LESS THAN
RIPPLE VOLTAGE FOR HWR