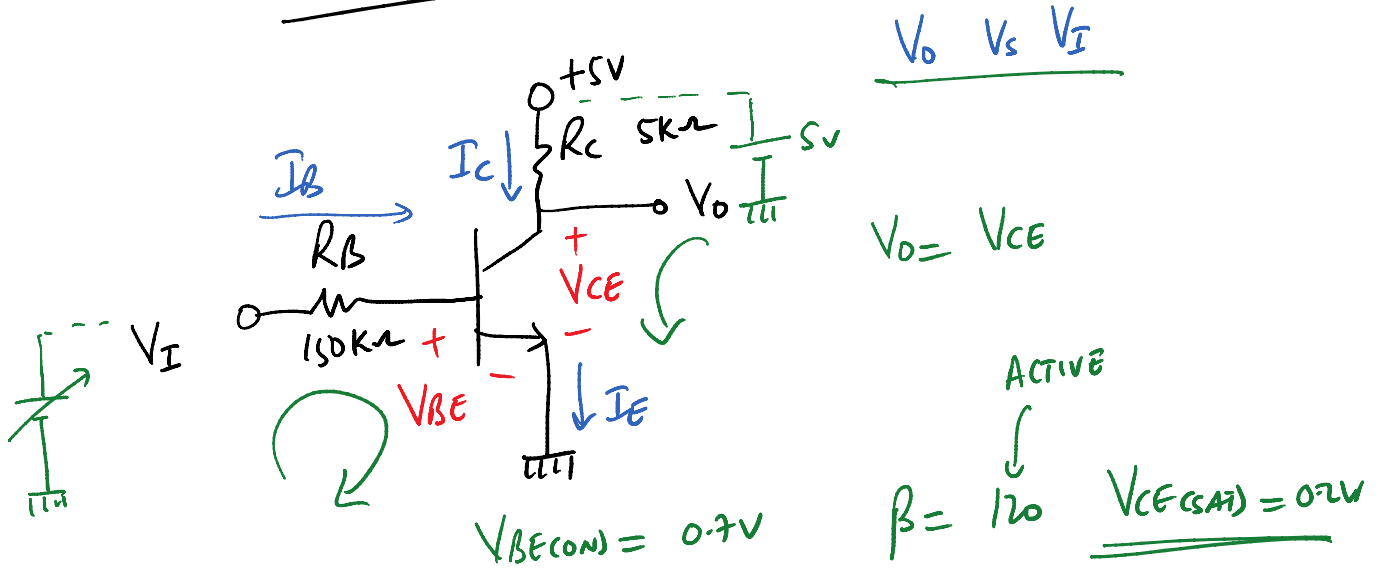


LECTURE - 28

VOLTAGE TRANSFER CURVES



IF $V_I \leq 0.7V$ TRANSISTOR IS OFF $\therefore I_B = 0A$
 $I_C = 0$
 LOAD LINE EQ. $V_{CE} = V_{CC} - I_C R_C$
 $V_{CE} = V_{CC}$
 $V_0 = V_{CE} = 5V$

FOR $V_I > 0.7V$ TRANSISTOR IS ON, INITIALLY IN ACTIVE REGION

KVL BE LOOP

$$-V_I + I_B R_B + V_{BE(ON)} = 0$$

$$I_B = \frac{V_I - 0.7}{R_B}$$

ONLY FOR ACTIVE REGION

$$I_C = \beta I_B = \frac{\beta (V_I - 0.7)}{R_B}$$

$$I_c = \beta I_B = \frac{\beta (V_{CE} - 0.7)}{R_B}$$

KVL CE LOOP

$$-5 + I_c R_c + V_o = 0$$

$$V_o = 5 - I_c R_c$$

$V_{CE} \uparrow \quad V_o \downarrow$

$$V_o = 5 - \frac{\beta (V_{CE} - 0.7) R_c}{R_B}$$

V_{CE}



Now $V_{CE} = V_o = 0.2V \rightarrow$ THEN TRANSISTOR
IS IN SATURATION
[\therefore OF LOTS OF I_c , LOTS OF DROP
ACROSS $R_c \therefore V_{CE} \downarrow$]

\therefore ACTIVE REGION $0.2 \leq V_o < 5V$


$$\text{FOR } V_o = 0.2V = 5 - \frac{(120)(V_I - 0.7)R_c}{R_B}$$

$V_I = 1.9V \quad \therefore$ FOR $V_I > 1.9V$
TRANSISTOR IS IN SATURATION



Friday, February 15, 2013
10:52 AM

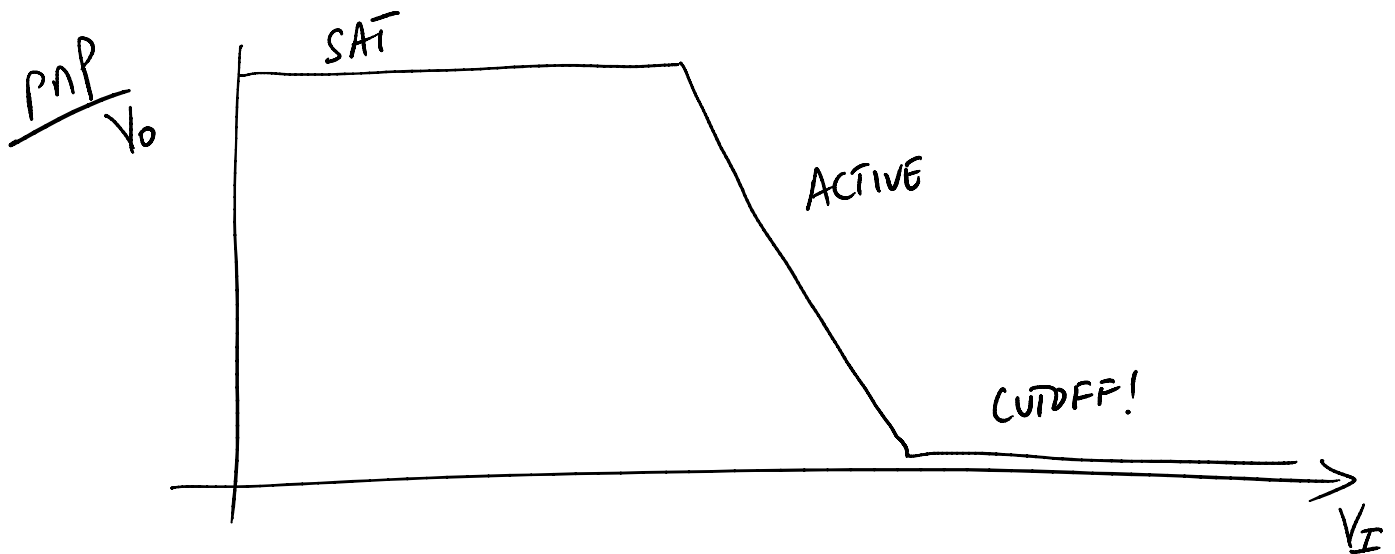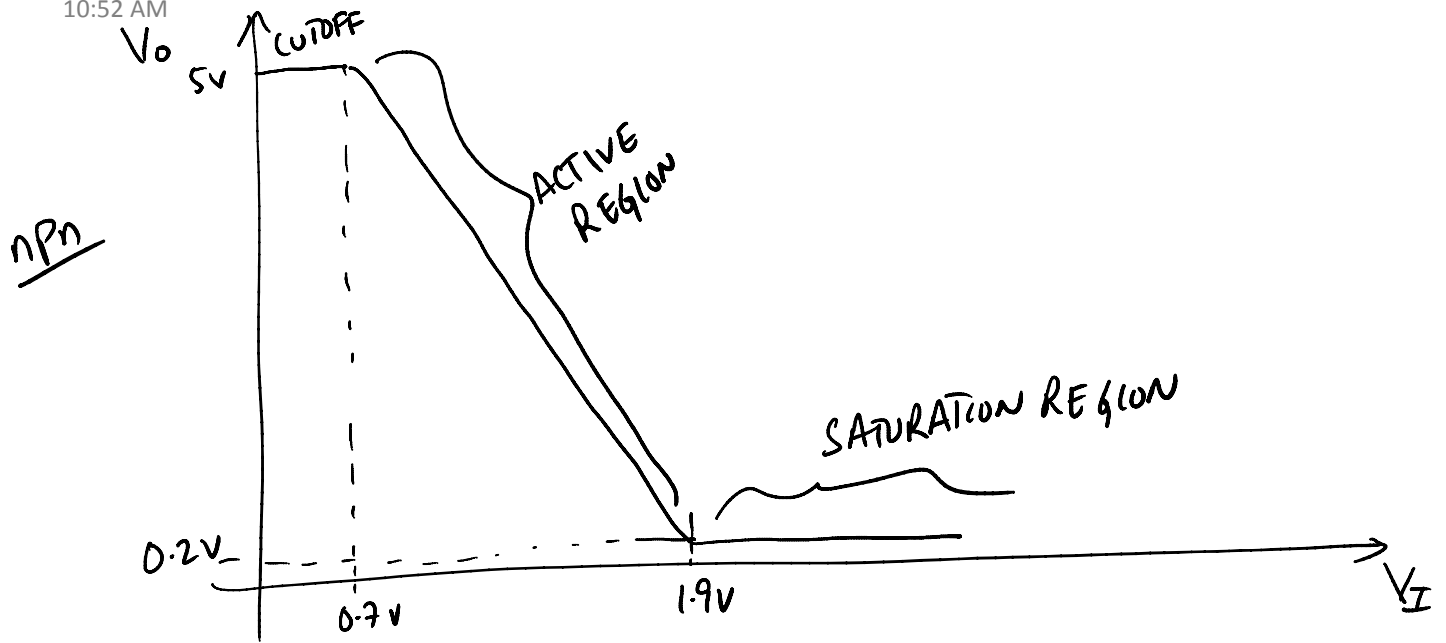

AMPLIFIER

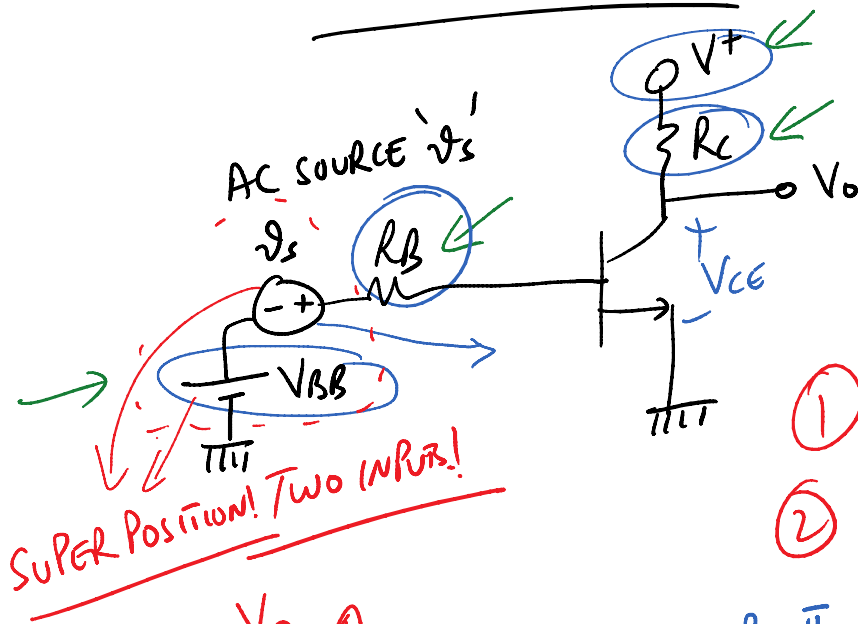

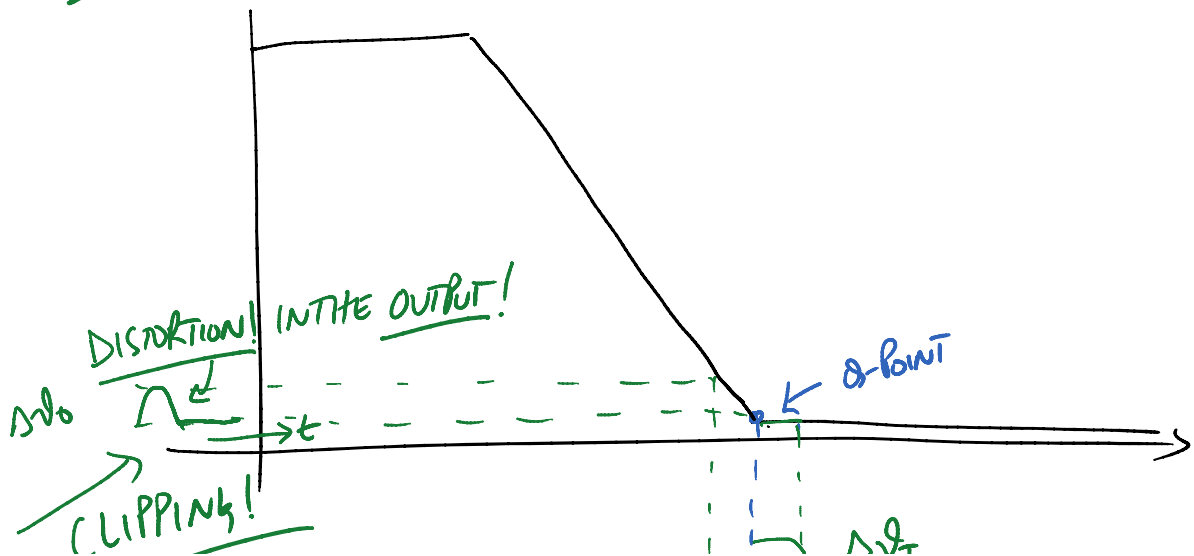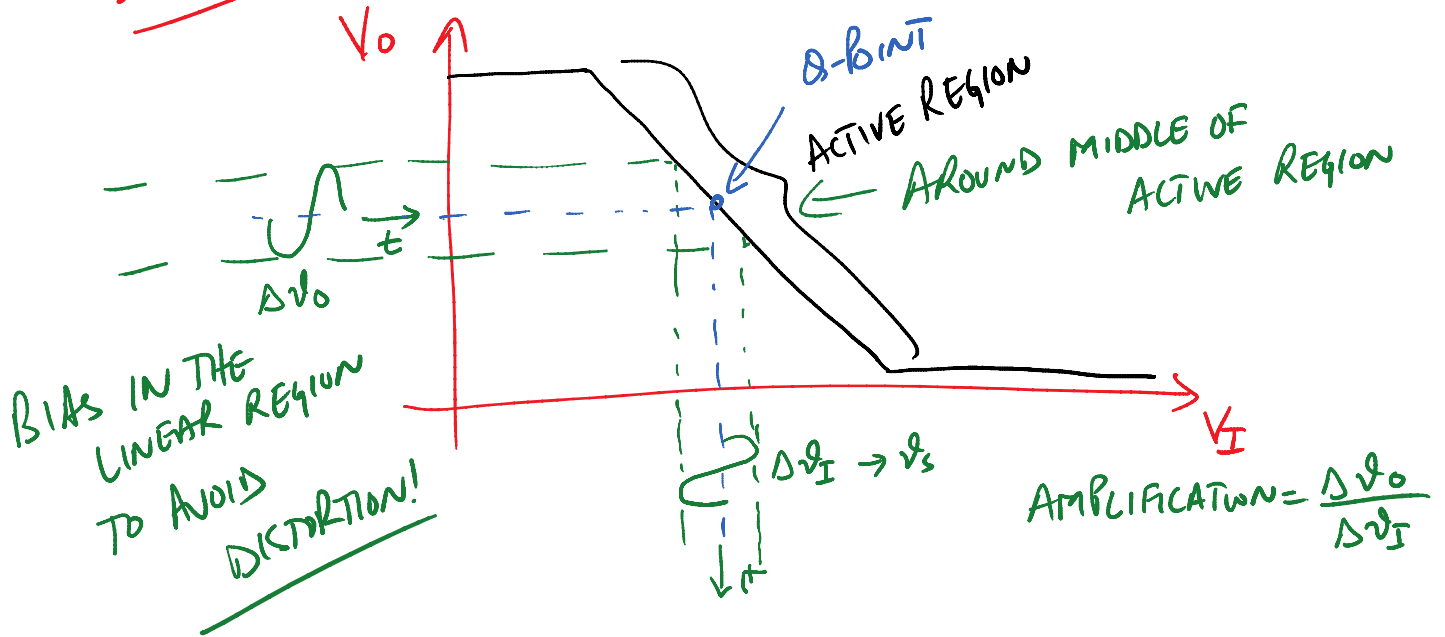- ① SET Q-POINT USING DC SOURCES
- ② THEN DO AC ANALYSIS



CLIPPING!



* BIASING FOR AMPLIFICATION IS IMPORTANT
" DONE BY USING EXTERNAL DC SUPPLY AND RESISTOR CIRCUIT "

* Q-POINT SHOULD LIE IN THE ACTIVE REGION

HOW TO??