

LECTURE - 37


P-CHANNEL → PMOS

SAME OPERATION!

ENHANCEMENT MODE

$$V_{TP} < 0$$

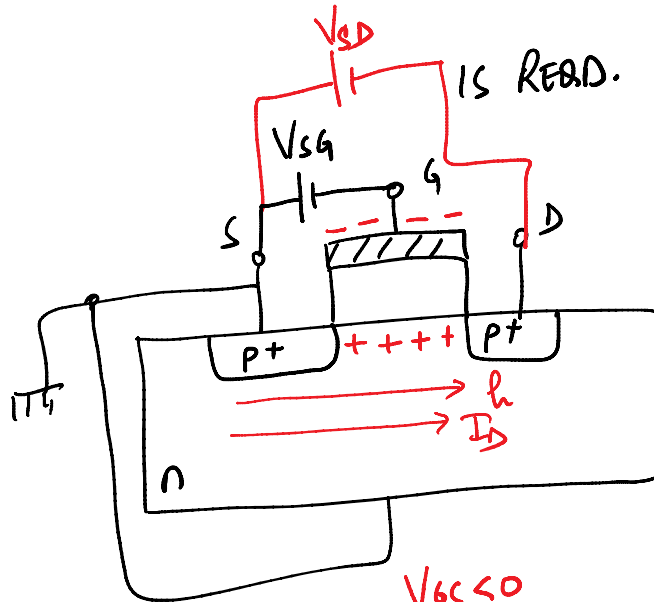∴ NEGATIVE VOLTAGE
TO CREATE AN INVERSION
LAYER



$$\underline{\underline{V_{GS} < 0}}$$

$$\underline{\underline{V_{TP} < 0}}$$

$V_{SG} > 0$ GATE IS NEGATIVE
 $V_{SD} > 0$ DRAIN IS
NEGATIVE W.R.T
SOURCE

EQUATIONS

$$V_{TP} < 0$$

$$V_{SD(CSAT)} = V_{SG} + V_{TP} \quad I_D = I_{SD}$$

TRIODE

$$I_D = K_P \left[2 (V_{SG} + V_{TP}) V_{SD} - V_{SD}^2 \right]$$

SAT.

$$I_D = K_P \left[V_{SG} + V_{TP} \right]^2$$


$$V_{SD} > V_{SD(SAT)} = V_{SG} + V_{TP}$$

$K_p \rightarrow$ CONDUCTION PARAMETER


CIRCUIT SYMBOLS

→ ENHANCEMENT
MODE


n MOS

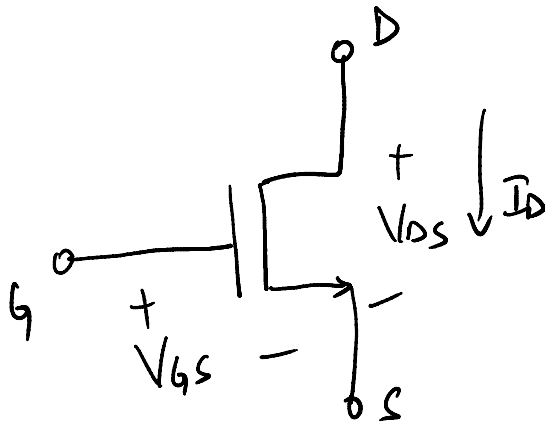

p MOS

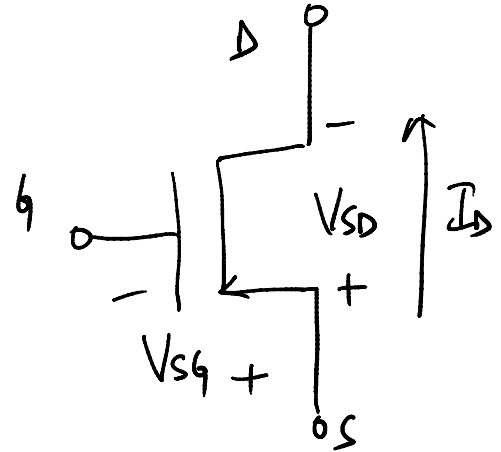


n-CHANNEL DEPLETION MODE MOSFET

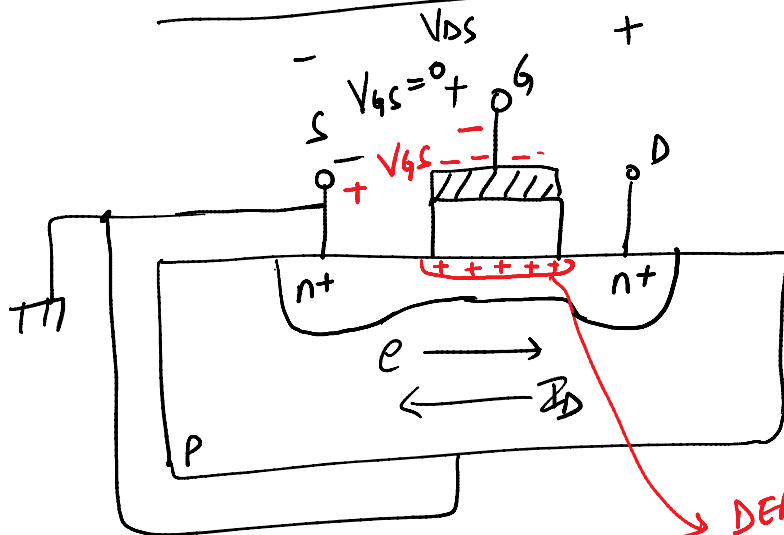



$V_{GS} = 0$
CHANNEL EXISTS
 $\therefore I_D > 0$ IF $V_{DS} > 0$
NORMALLY ON DEVICE

SPECIFICATION
 $V_{TN} < 0$

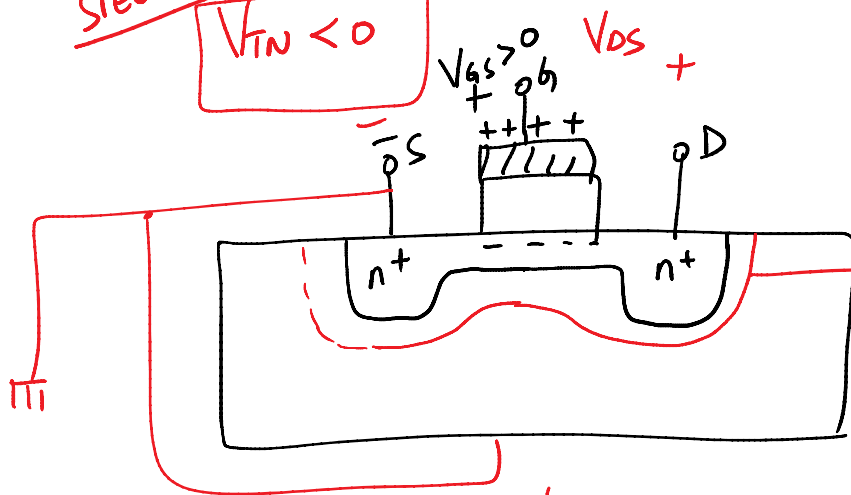


CHANNEL EXPANDS FURTHER
 $I_D \uparrow$

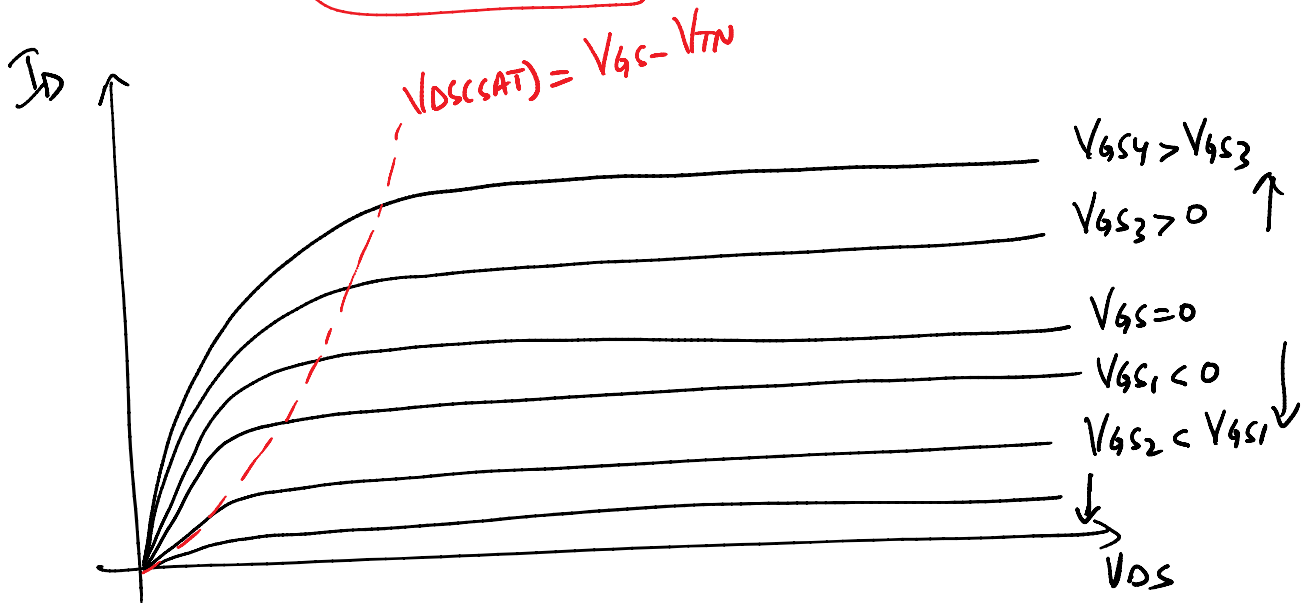

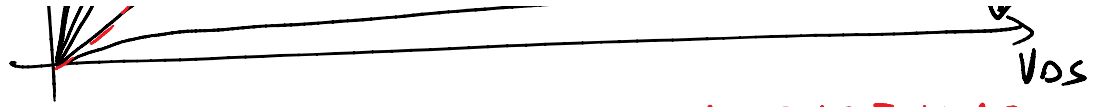


- * V_{TN} IS POSITIVE FOR ENHANCEMENT MODE
- * V_{TN} IS NEGATIVE FOR DEPLETION MODE

CIRCUIT SYMBOLS


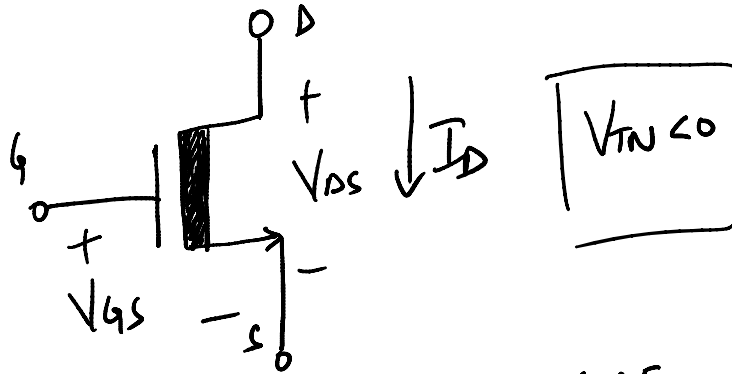


NMOS DEPLETION MODE

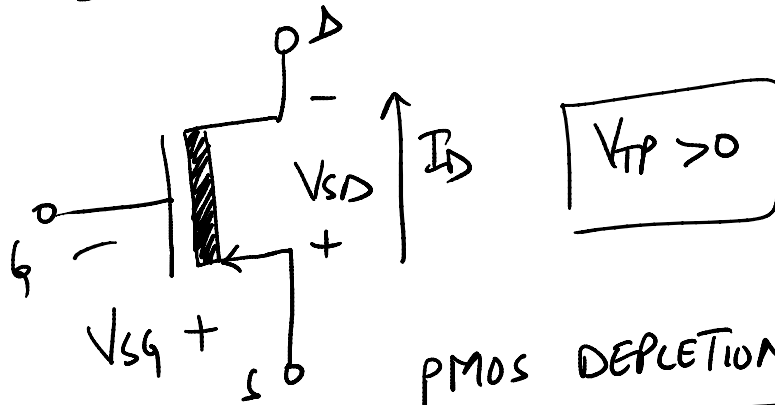

PMOS DEPLETION MODE

N-CHANNEL ENHANCEMENT LOAD DEVICE

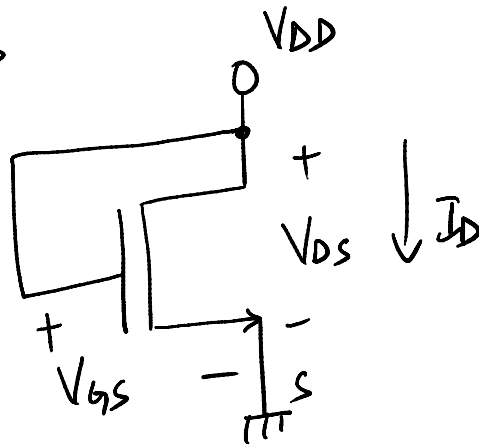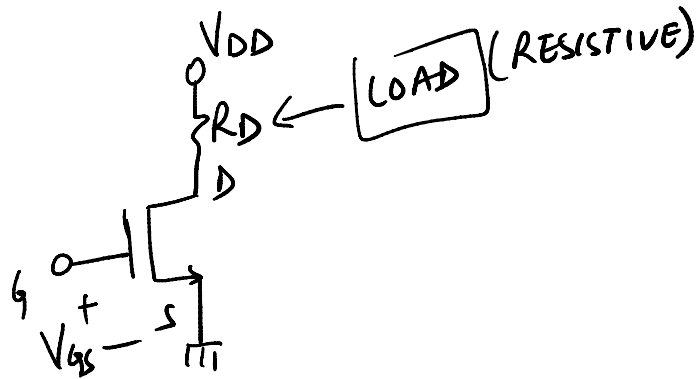

$$V_{TN} > 0$$

$$\boxed{V_{GS} = V_{DS}} > V_{DSCSAT}$$


$$V_{DSCSAT} = V_{GS} - V_{TN}$$


∴ ALWAYS IN SATURATION

$$I_D = K_n (V_{GS} - V_{TN})^2$$

I_D ↑

← NON-LINEAR RESISTOR

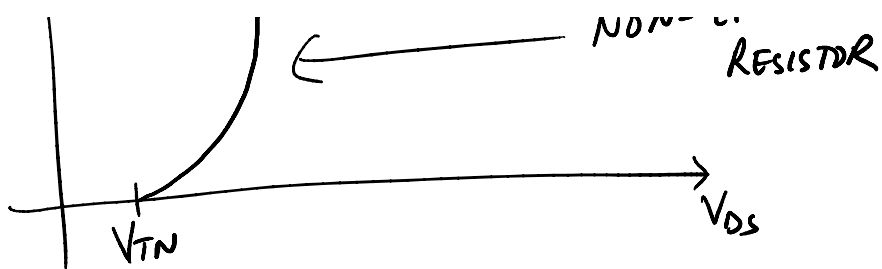

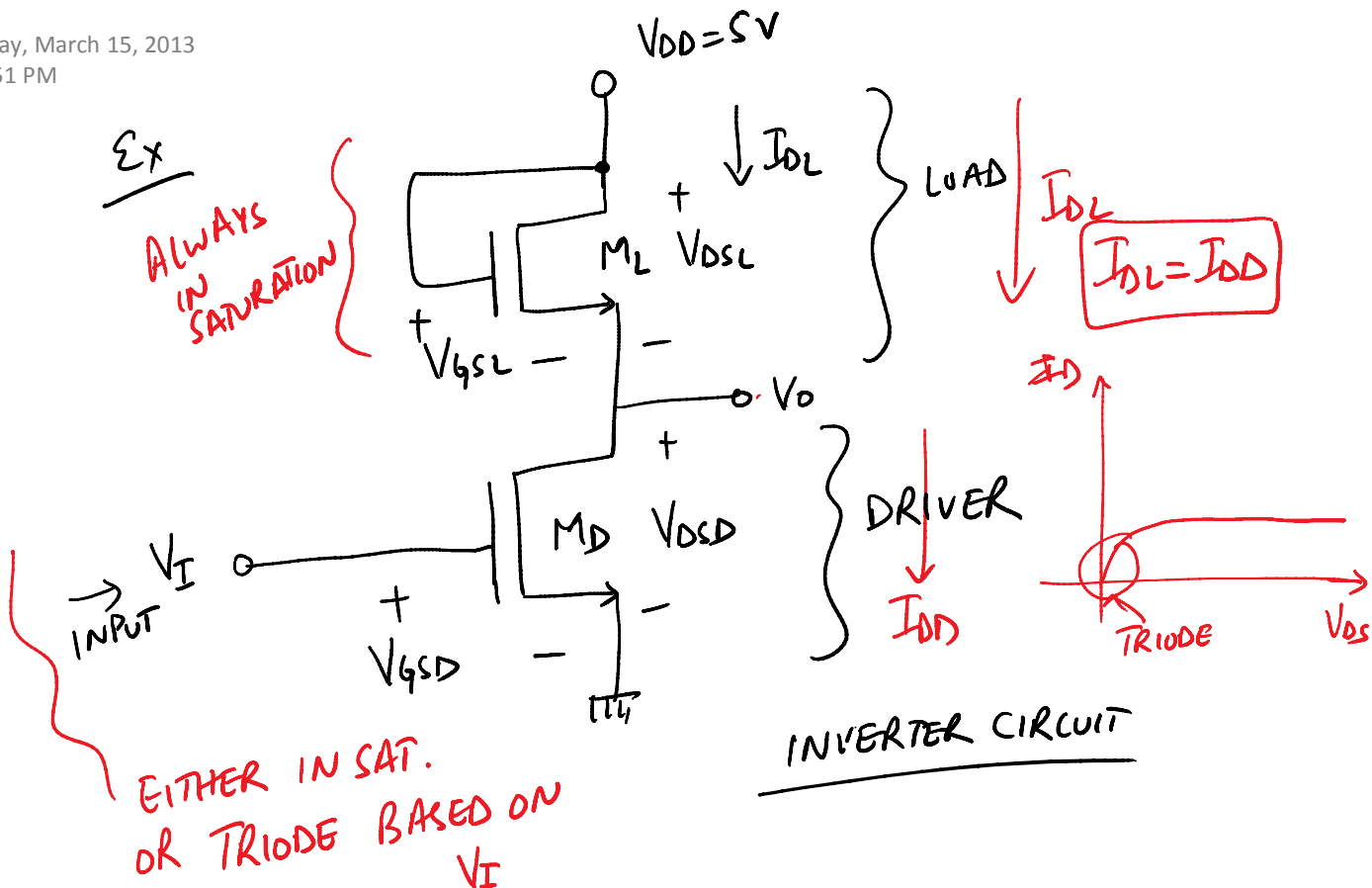

$$V_{TND} = V_{TNL} = \underline{1V}$$

$$K_{nD} = 50 \mu A/V^2 \quad K_{nL} = 10 \mu A/V^2$$

$$V_I = 5V, 1.5V \quad V_o?$$

INVERTER

IF INPUT IS HIGH, OUTPUT SHOULD BE LOW!

WOULD PREFER THE DRIVER TO BE IN TRIODE REGION

$$I_{DL} = I_{DD}$$

$$K_{nD} [2(V_{gsD} - V_{TND})V_{dsD} - V_{dsD}^2] = K_{nL} [V_{gsL} - V_{TNL}]^2$$

$$V_{GS D} = \underline{V_I} \quad V_{DS D} = \underline{V_O} \quad V_{GS L} = V_{DS L} = \underline{V_{DD} - V_O}$$

$$K_{ND} \left[2 (V_I - V_{TND}) V_O - V_O^2 \right] = K_{NL} \left[V_{DD} - V_O - V_{TNL} \right]^2$$

$$\text{so } \left[2 (5 - 1) V_O - V_O^2 \right] = (10) (5 - V_O - 1)^2$$

$$\therefore 3 V_O^2 - 24 V_O + 8 = 0$$

$$V_O = \cancel{7.65}, 0.349 \checkmark$$

o/p is low!

$$V_{DS D} = V_O = 0.349 \text{ V} < V_{GS D} - V_{TND} \left(\begin{array}{l} (5-1) \\ = 4 \text{ V} \end{array} \right)$$

\therefore DRIVER IS IN TRIODE REGION!

$$\underline{I_D = 133 \mu\text{A}}$$

$$V_I = 1.5V$$
$$V_{TND} = 1V \quad V_{GSD} = V_I = 1.5V$$

$$V_{GSD} - V_{TND} = 0.5V = V_{DSD(SAT)}$$

ASSUME THAT MD IS IN SAT. REGION \rightarrow O/P IS HIGH

$$I_{OD} = I_{OL}$$

$$K_{ND} [V_{GSD} - V_{TND}]^2 = K_{NL} [V_{GSL} - V_{TNL}]^2$$

$$V_{GSD} = V_I \quad V_{GSL} = V_{DSL} = V_{DD} - V_o$$

$$K_{ND} [V_I - V_{TND}]^2 = K_{NL} [V_{DD} - V_o - V_{TNL}]^2$$

$$\sqrt{50} [1.5 - 1] = \sqrt{10} [5 - V_o - 1]$$


$$V_o = 2.88V$$

$$V_{DSD} = V_o = \underline{\underline{2.88V}} > V_{GSD} - V_{TND} = 1.5 - 1 = \underline{\underline{0.5V}}$$


\therefore DRIVER IS IN SAT.

$$I_D = 12.5\mu A$$


N-CHANNEL DEPLETION LOAD DEVICE

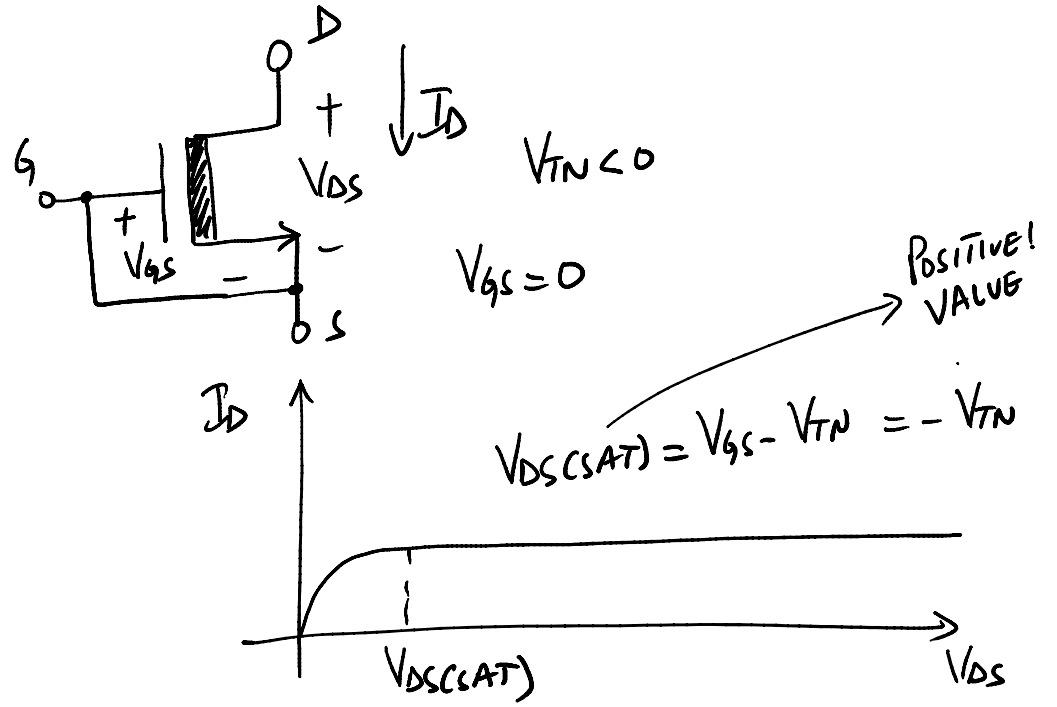

INVERTER

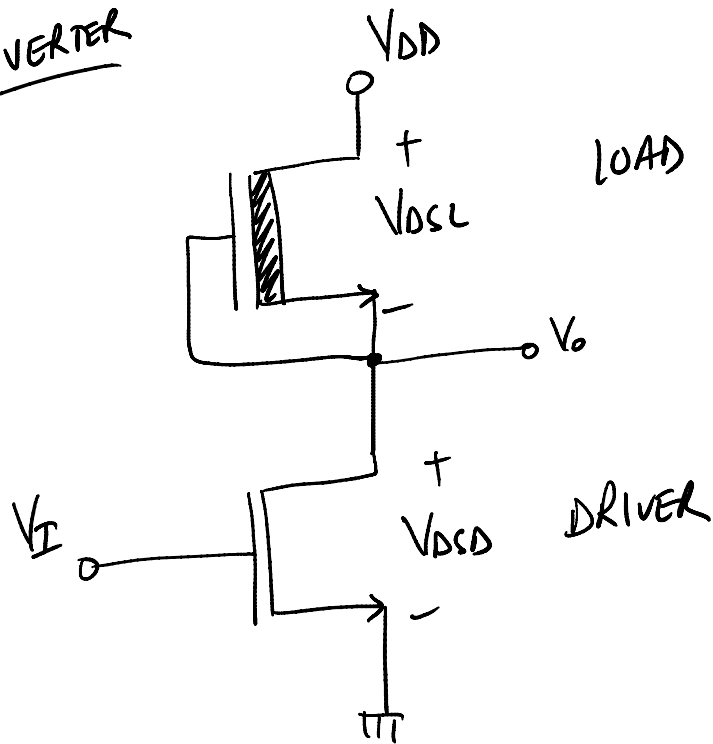

CMOS → COMPLEMENTARY MOS

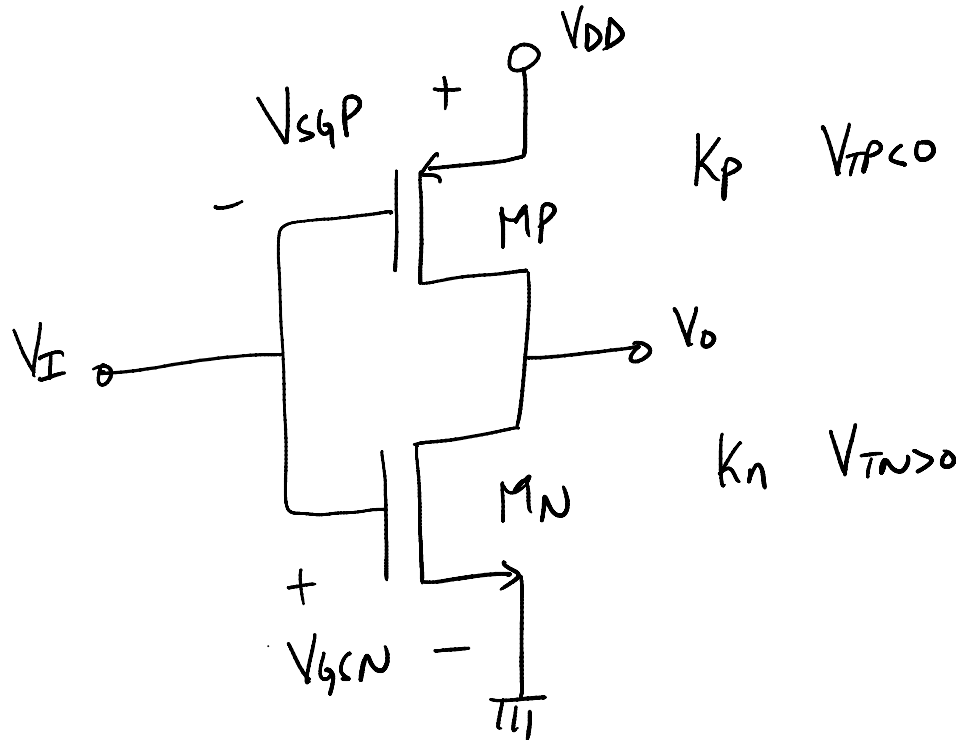

IF $V_{TP} = -1V$ $V_{TN} = 1V$

$V_I = \underbrace{0V \leftrightarrow 1V}_{\text{Low}}$

NMOS IS OFF
PMOS IS ON
 $\therefore V_o = V_{DD}$ (HIGH)

$V_I = \underbrace{V_{DD}}_{\text{HIGH}}$

NMOS IS ON
PMOS IS OFF $\therefore V_o = 0$ (LOW)