

LECTURE 260 – SHUNT-SHUNT FEEDBACK (READING: GHLM – 563-569)

Objective

The objective of this presentation is:

- 1.) Show how to identify the type of feedback topology
- 2.) Illustrate the analysis of shunt-shunt feedback circuits

Outline

- Feedback identification procedure
- Shunt-shunt feedback with nonideal source and load
- Examples
- Summary

IDENTIFICATION OF THE FOUR, SINGLE-LOOP FEEDBACK TOPOLOGIES Two-Terminal Representation of a Single-Loop, Negative Feedback System

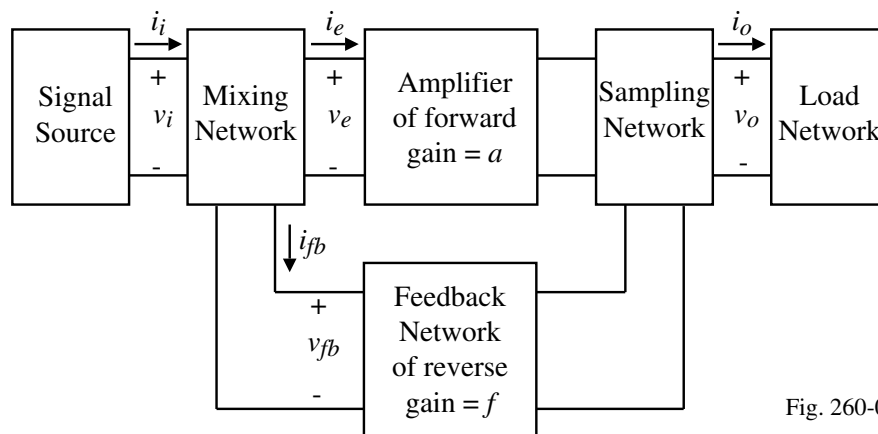



Fig. 260-01

Feedback Topology Identification Procedure

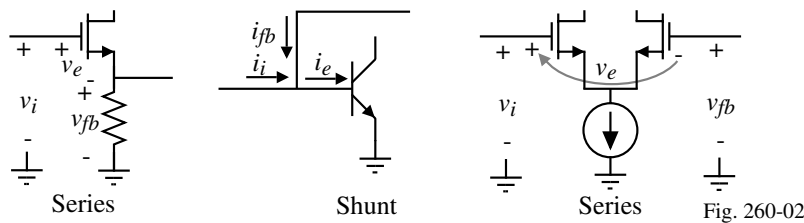- 1.) Identify the feedback loop by tracing around the feedforward and feedback path. Also check to see if the feedback is positive or negative.
- 2.) Identify whether or not the mixing network is series or shunt. If the signal source has one terminal on ac ground then:
 - a.) If the input active device has one of its input terminals on ac ground, then the mixing network must be shunt.
 - b.) If the signal and feedback sources are applied to different input terminals of the input active device, then the mixing network is series (this includes differential amplifiers where two devices form the input active device).
 - c.) If the signal source does not have one of its input terminals on ac ground or to check the above steps, try to assign the variables x_i , x_{fb} , and x_e on the schematic in such a manner as to implement the equation,


$$x_e = x_i \pm x_{fb}$$

If this equation can be written using voltages (currents) then the mixing circuit is series (shunt).



Feedback Topology Identification Procedure - Continued

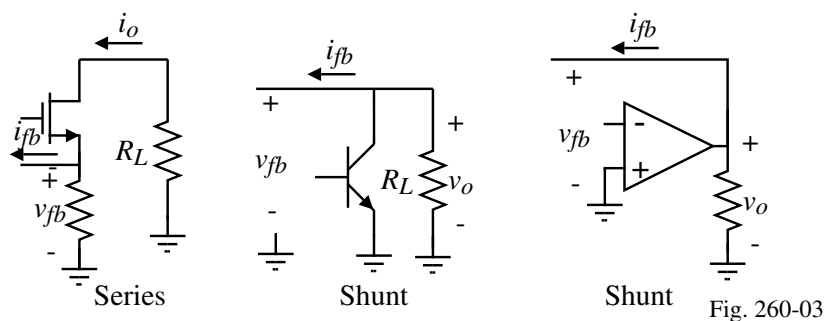- 3.) Next identify the sampling circuit as series or shunt. If the load is grounded then,
 - a.) If the out active device has one of its two possible output terminals grounded, then the feedback is shunt.
 - b.) If the output active device has neither of its output terminals on ground and if the output signal is taken from one of its output terminals and the fed back signal from the other output terminal, then the feedback is series.
 - c.) If the load is not grounded or to check the above test, identify the load resistor, R_L , and apply the following test:
 - i.) If x_{fb} becomes zero when $R_L = 0$, then the sampling network is shunt.
 - ii.) If x_{fb} becomes zero when $R_L = \infty$, then the sampling network is series.



Transistor Examples of Negative Feedback Topology Identification

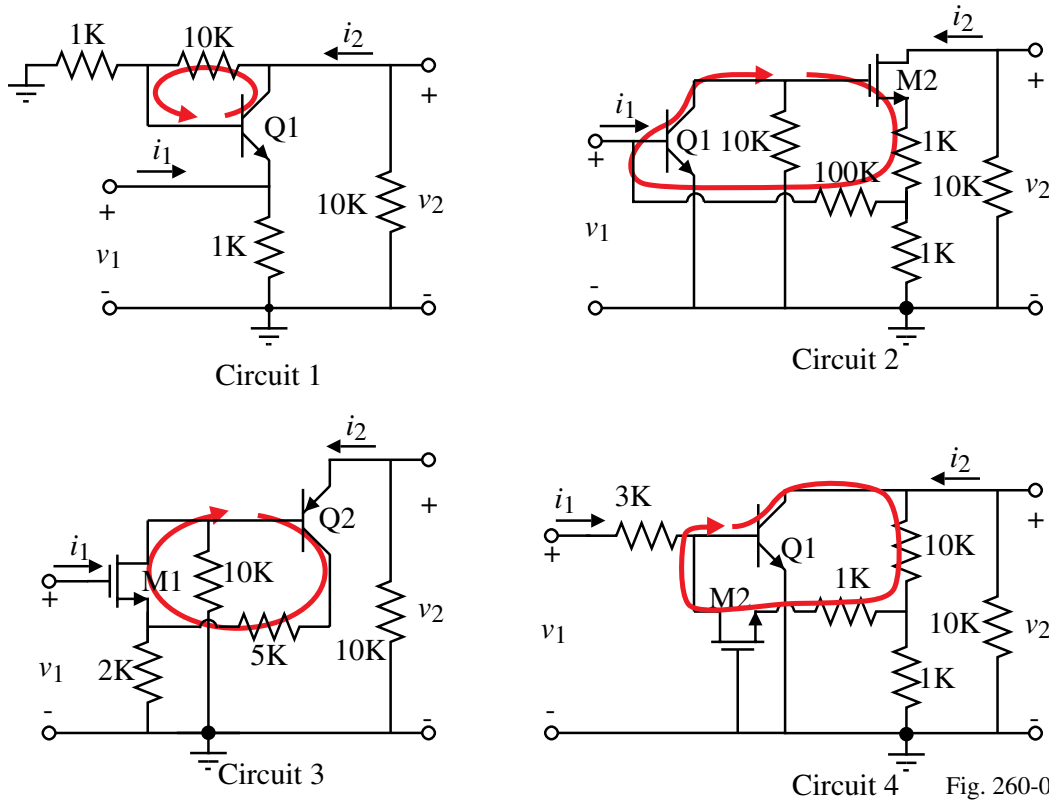


Fig. 260-04

Shunt-Shunt Feedback including Source and Load Resistance

Configuration:

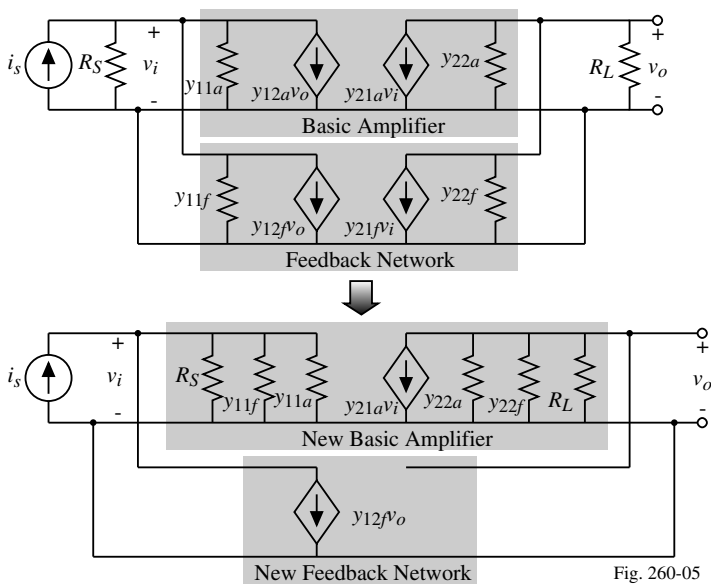


Fig. 260-05

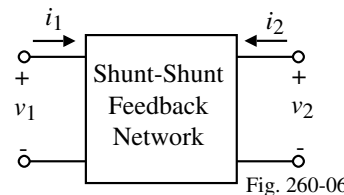


Fig. 260-06

$$i_1 = y_{11}v_1 + y_{12}v_2$$

$$i_2 = y_{21}v_1 + y_{22}v_2$$

where for the new basic amplifier,

$$y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0} = G_S + y_{11a} + y_{11f}$$

$$y_{12} = \frac{i_1}{v_2} \Big|_{v_1=0} = 0$$


$$y_{21} = \frac{i_2}{v_1} \Big|_{v_2=0} = y_{21a}$$

$$y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0} = G_L + y_{22a} + y_{22f}$$

$$\frac{v_o}{i_s} = \frac{v_2}{i_1} = A = \frac{a}{1+af} = \frac{(-y_{21a}/y_{11}y_{22})}{1+(-y_{21a}/y_{11}y_{22})y_{12f}} \Rightarrow a = \frac{-y_{21a}}{y_{11}y_{22}} \quad \text{and} \quad f = y_{12f}$$

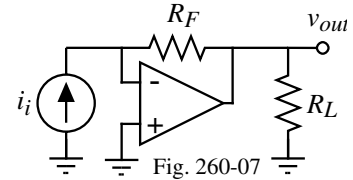
Example 1 – Inverting Op Amp

Find the closed-loop transfer function, A , the closed-loop input resistance, Z_{if} , and the closed-loop output resistance, Z_{of} of the shunt-shunt configuration shown. The op amp has a differential input resistance of z_i , voltage gain of a_v , and output resistance of z_o .



Solution

Equivalent circuit:

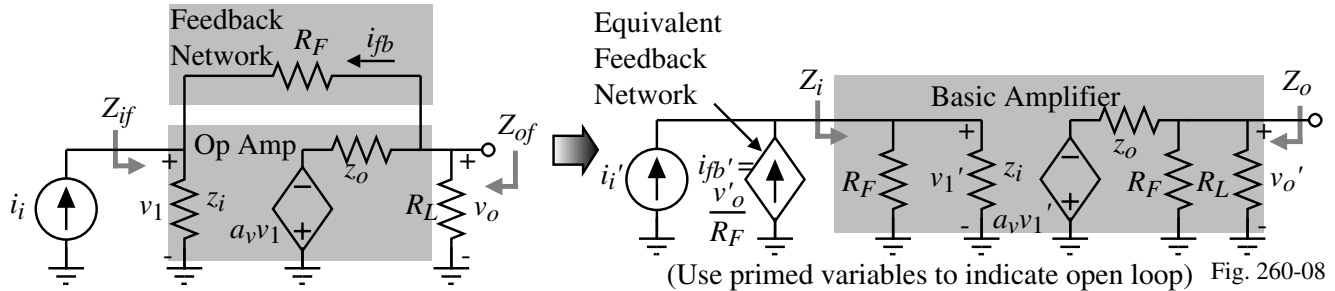

It is easy to show that $f = y_{12f} = \frac{i_1'}{v_2'} \Big|_{v_1'=0} = \frac{-1}{R_F}$

The forward gain, a , is

$$a = \frac{v_o'}{i_i'} = \left(\frac{v_o'}{v_1'} \right) \left(\frac{v_1'}{i_i'} \right) = \left(\frac{-a_v(R_F \parallel R_L)}{z_o + (R_F \parallel R_L)} \right) \left(\frac{z_i R_F}{z_i + R_F} \right) \quad \text{where } i_{fb}' = 0$$

Example 1 – Continued

The loop gain is

$$T = af = \left(\frac{a_v R_F R_L}{z_o R_F + z_o R_L + R_F R_L} \right) \left(\frac{z_i}{z_i + R_F} \right)$$

The closed-loop gain is

$$\frac{v_o}{i_i} = \frac{a}{1+af} = \frac{\left(\frac{-a_v R_F R_L}{z_o R_F + z_o R_L + R_F R_L} \right) \left(\frac{z_i R_F}{z_i + R_F} \right)}{1 + \left(\frac{a_v R_F R_L}{z_o R_F + z_o R_L + R_F R_L} \right) \left(\frac{z_i}{z_i + R_F} \right)} = \frac{(-a_v R_F^2 R_L z_i)}{(z_o R_F + z_o R_L + R_F R_L)(z_i + R_F) + a_v R_F R_L z_i}$$

The closed-loop input impedance is

$$Z_{if} = \frac{Z_i}{1+T} = \frac{\frac{z_i R_F}{z_i + R_F}}{1 + \left(\frac{a_v R_F R_L}{z_o R_F + z_o R_L + R_F R_L} \right) \left(\frac{z_i}{z_i + R_F} \right)} \approx \frac{z_o R_F + z_o R_L + R_F R_L}{a_v R_L}$$

The closed-loop output impedance is

$$Z_{of} = \frac{Z_o}{1+T} = \frac{z_o \parallel R_F \parallel R_L}{1 + \left(\frac{a_v R_F R_L}{z_o R_F + z_o R_L + R_F R_L} \right) \left(\frac{z_i}{z_i + R_F} \right)}$$

If $a_v = 200,000$, $z_i = 2\text{M}\Omega$, and $z_o = 75\Omega$, $R_F = 1\text{M}\Omega$, and $R_L = 10\text{k}\Omega$, then $T = 133,333$, $Z_i = 2 \parallel 1 = 0.667\text{M}\Omega \rightarrow Z_{if} = 5\Omega$, $Z_o \approx 75\Omega \rightarrow Z_{of} = 0.563\text{m}\Omega$ and $A = -999,992\Omega$

Example 2 – Transistor Feedback Amplifier

For the amplifier shown, find v_2/v_1 , v_1/i_1 , and v_2/i_2 . Assume that $g_m = 5\text{mS}$ and $r_{ds} = \infty$ for the MOSFET and $r_{\pi 1} = r_{\pi 3} = 1000\Omega$ and $\beta_{F1} = \beta_{F3} = 100$ for the BJTs.

Solution



1.) Find the feedback topology and polarity of feedback.

The loop consists of base-collector of Q1, gate-drain of M2, and base-collector of Q3. A positive change at the base of Q1 gives a “-“ and the gate of M2, which gives a “+” at the base of Q3, which gives a “-“ at the base of Q1. \therefore feedback is negative.

2.) The mixing circuit is shunt because only the base terminal of Q1 is connected to the input and feedback. Note that $i_{C3} = i_{fb}$ and $i_{B1} = i_e \Rightarrow i_e = i_i - i_{fb}$.

3.) The feedback circuit is shunt because the output transistor (M2) has one of its possible output terminals on ac ground. Also, if $R_L = R_4$ goes to zero, $i_{fb} = 0$.

4.) Draw the closed-loop circuit and small-signal model.

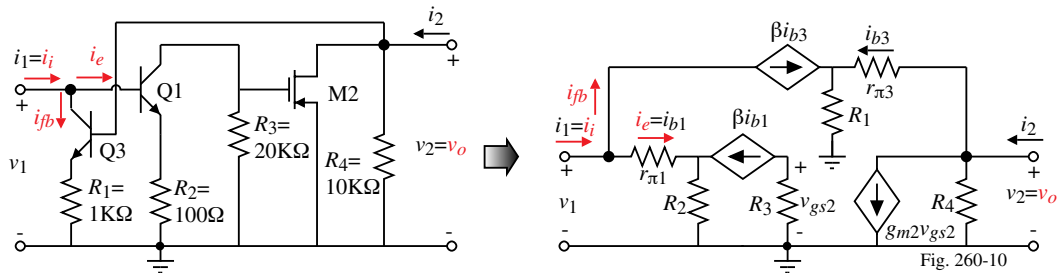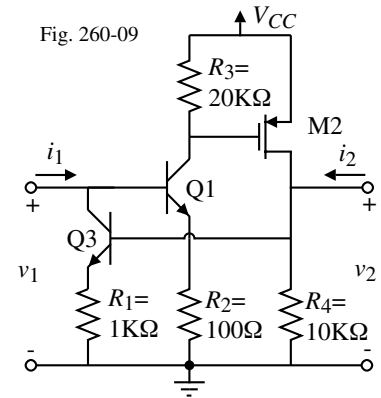


Example 2 – Continued

5.) AC open-loop model is drawn by,

- a.) Looking back into the feedback network (Q3,R1) to the left with $v_1 = 0$.
- b.) Looking back into the feedback network (Q3,R1) to the right with $v_2 = 0$.

The result is,

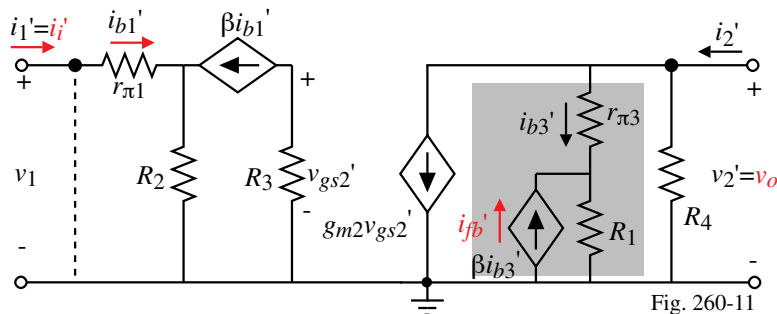

6.) Next, find a and f .

$$a = \frac{v_o'}{i_1'} = \left(\frac{v_o'}{v_{gs2'}} \right) \left(\frac{v_{gs2'}}{i_1'} \right) = -g_{m2} \{ R_4 \parallel [r_{\pi 3} + (1 + \beta_3)R_1] \} (-\beta_3 R_3) = (-45.54)(-2 \times 10^6) = 91.07 \text{M}\Omega$$

$$f = \frac{i_{fb}'}{v_o'}, \quad i_{B1}' = \frac{v_o'}{r_{\pi 3} + (1 + \beta_3)R_1} \rightarrow i_{fb}' = \beta_3 i_{B3}' \rightarrow f = \frac{\beta_3}{r_{\pi 3} + (1 + \beta_3)R_1} = 0.98 \text{mS} (\approx 1/R_1)$$

Example 2 – Continued

7.) Calculate R_i and R_o .

$$R_i = \frac{v_1'}{i_1'} = r_{\pi 1} + (1 + \beta_1)R_2 = 11\text{k}\Omega$$

and

$$R_o = \frac{v_2'}{i_2'} = R_4 \parallel [r_{\pi 3} + (1 + \beta_3)R_1] = 10\text{k}\Omega \parallel 102\text{k}\Omega = 9.107\text{k}\Omega$$

8.) Find v_2/v_1 , v_1/i_1 , and v_2/i_2 .

$$\frac{v_o}{i_1} = \frac{a}{1+T} = \frac{91.07\text{M}\Omega}{1+89.287 \times 10^3} = 1019.2\Omega \quad (\text{Note: } \frac{1}{f} = 1020\Omega)$$

$$R_{if} = \frac{v_1}{i_1} = \frac{R_i}{1+T} = \frac{11\text{k}\Omega}{1+89.287 \times 10^3} = \underline{0.1243\Omega}$$

$$R_{of} = \frac{v_2}{i_2} = \frac{R_o}{1+T} = \frac{9.107\text{k}\Omega}{1+89.287 \times 10^3} = \underline{0.102\Omega}$$

Now,

$$\frac{v_2}{v_1} = \left(\frac{v_2}{i_1} \right) \left(\frac{i_1}{v_1} \right) = \frac{v_2/i_1}{R_{if}} = \frac{1019.2\Omega}{0.1243\Omega} = \underline{8204.5\text{V/V}}$$

SUMMARY

- We have shown how to identify the type of feedback topology
- Illustrate the analysis of shunt-shunt feedback circuits
- Procedure
 - 1.) Identify the type of feedback topology
 - 2.) Draw the schematic for the closed-loop amplifier
 - 3.) Break the feedback loop by replacing the feedback network with the resistance seen looking into each end of the feedback network with the other end shorted.
 - 4.) Draw a schematic of the open-loop amplifier with all variables primed.
 - 5.) Solve for a , f , R_i , and R_o .
 - 6.) Calculate A and R_{if} and R_{of} by the following formulas:

$$A = \frac{a}{1+T}, \quad R_{if} = \frac{R_i}{1+T}, \quad \text{and} \quad R_{of} = \frac{R_o}{1+T}$$
 - 7.) If necessary, use the results of 6.) to find the desired closed-loop transfer function.