
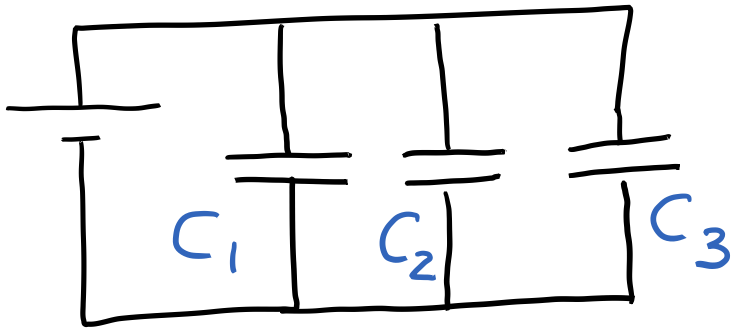


Lecture 10: Capacitor networks

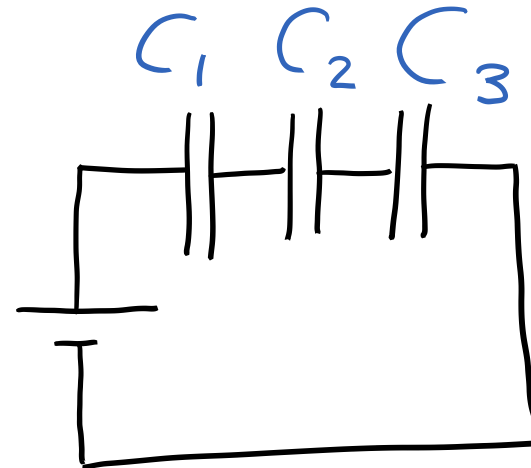


in parallel



in series

Capacitors in parallel

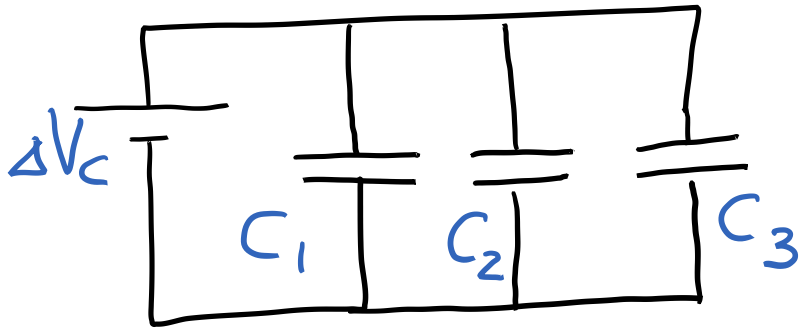

in parallel

ΔV_c same for all capacitors

C_1 stores $Q_1 = C_1 \Delta V$

C_2 stores $Q_2 = C_2 \Delta V$

C_3 stores $Q_3 = C_3 \Delta V$

$$Q_{\text{net}} = (\sum C_i) \Delta V$$



$$C_{\text{eq}} = \sum_i C_i$$

equivalent
capacity

Capacitors in series

$$\Delta V_1 + \Delta V_2 + \Delta V_3 = \Delta V$$
$$Q_1 = Q_2 = Q_3 = Q_{\text{net}}$$
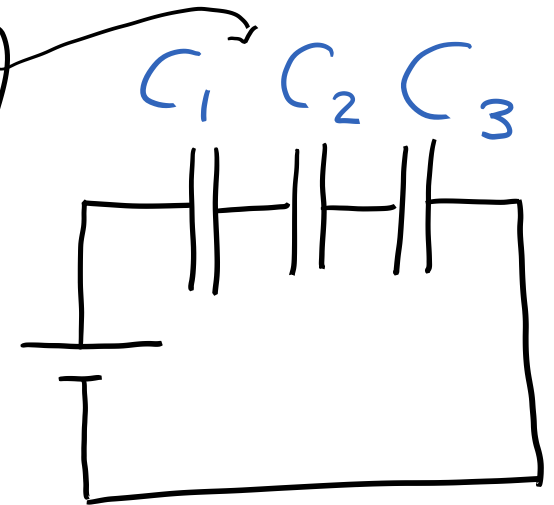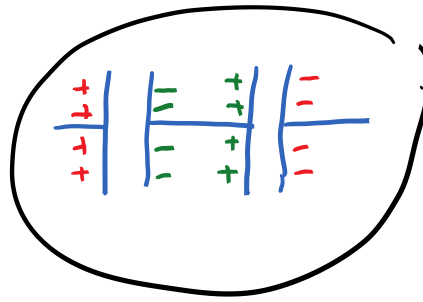
$$\frac{\Delta V_1}{Q_1} + \frac{\Delta V_2}{Q_2} + \frac{\Delta V_3}{Q_3} = \frac{\Delta V}{Q_{\text{net}}}$$
$$\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{C_{\text{eq}}}$$



$$\frac{1}{C_{\text{eq}}} = \sum_i \frac{1}{C_i}$$

$$C_{\text{eq}} = \left(\sum_i \frac{1}{C_i} \right)^{-1}$$

Ex. 23.10

