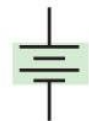


Lecture 15: Kirchhoff's Laws

Drawing Circuit Diagrams



Battery




Wire



Resistor




Bulb

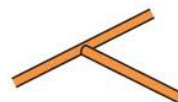

Junction



Capacitor

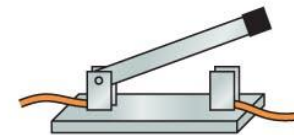

Switch




Kirchhoff's Laws: Junction Law

Lecture 14:

Current is the same at all points in a current-carrying wire.

Current is not “used up”. Charge cannot be created or destroyed.

“What goes in must come out”.

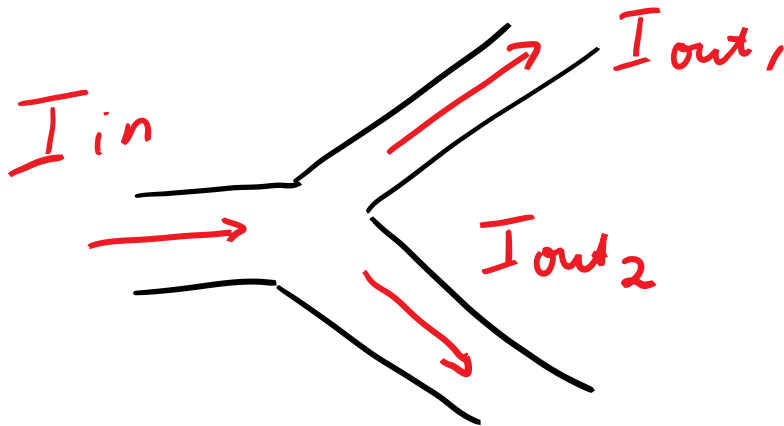


$$\sum I_{in} = \sum I_{out}$$

Current flow through resistor (from lec 14)

Assume “ideal wires” ($R=0$).

In reality: $R_{\text{wire}} \ll R_{\text{circuit element}}$

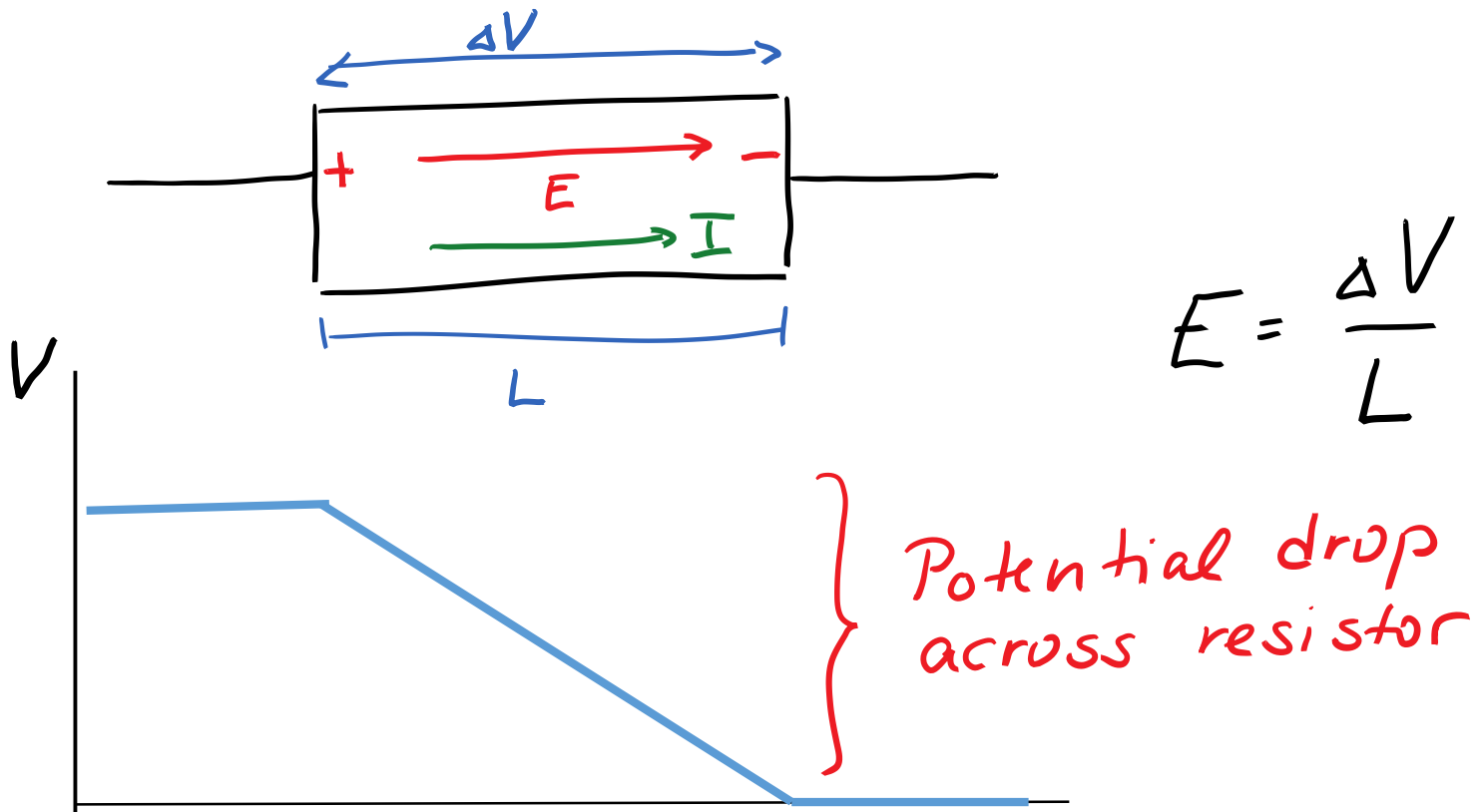Example: flashlight bulb $R=3\Omega$; wire connecting bulb to battery: $R=0.01\Omega$



Kirchhoff's Laws: Loop Law



Potential energy depends on position.

If we come back to the same point, we come back to the same value of potential energy.

For closed loop: $\Delta U_{\text{el}} = 0$

Because $V = U/q$: $\Delta V = 0$

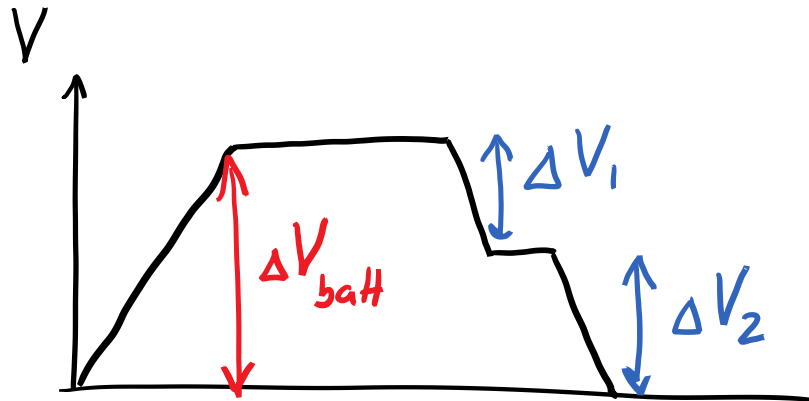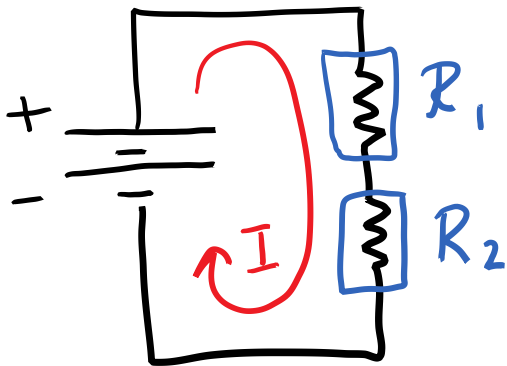
$$\Delta V_{\text{loop}} = \sum_i \Delta V_i = 0$$




Analyzing circuits

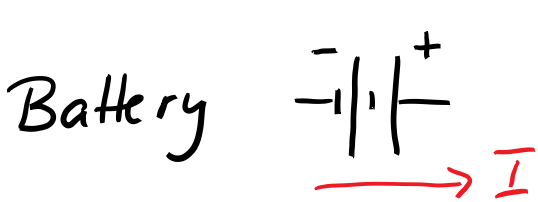1. Draw circuit diagram. Label known and unknown quantities
2. Assign direction for current, based on batteries.
3. Pick starting point, travel around the loop.


$$\Delta V = V_{\text{downstream}} - V_{\text{upstream}}$$



$$\Delta V_{\text{bat}} = +\mathcal{E}$$

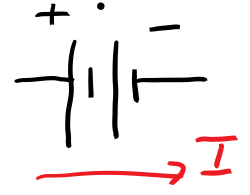

$$\Delta V_{\text{bat}} = -\mathcal{E}$$

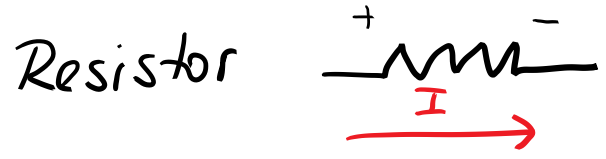


$$\Delta V_R = -IR$$

Potential decreases

4. Use loop law $\sum \Delta V_i = 0$

Example

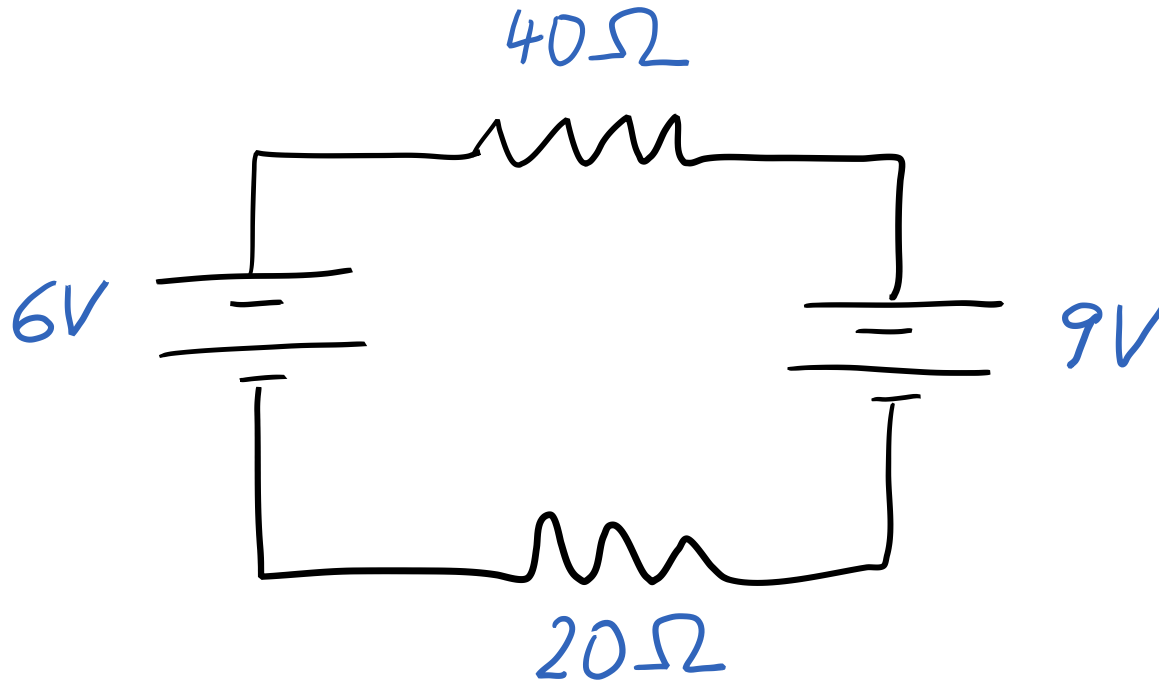

I ?

V for each resistor ?