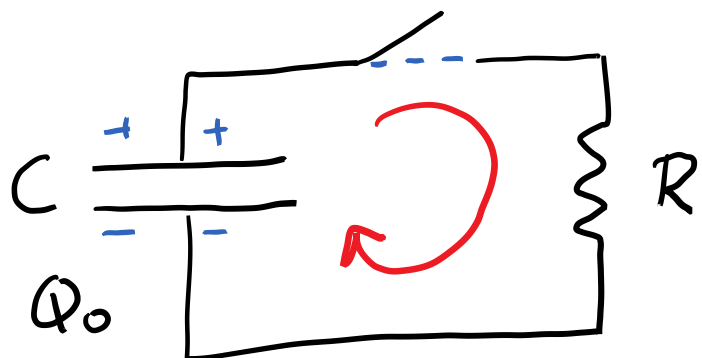


Lecture 19: RC Circuits

- Charging and discharging capacitors through a resistor

Discharging a capacitor



$$\Delta V_C = \frac{Q_0}{C}$$

Loop rule: $\sum \Delta V_i = 0$

$$\Delta V_C + \Delta V_R = 0$$


$$\Delta V_C - IR = 0$$

$$t=0: \Delta V_{C_0} = I_0 R$$


$$I_0 = \frac{\Delta V_{C_0}}{R}$$

As t increases: $I, \Delta V_C$ decrease until capacitor is discharged and $Q = 0$


Discharging a capacitor

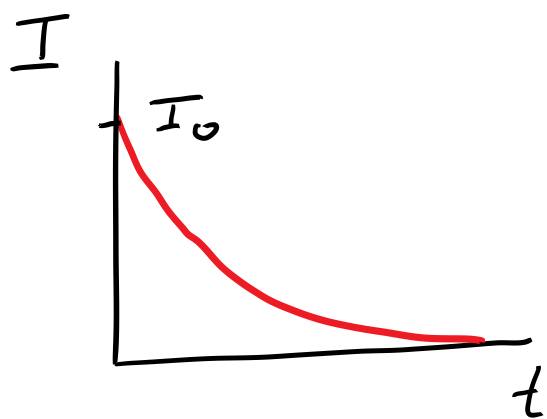

$$I = I_0 e^{-\frac{t}{RC}}$$

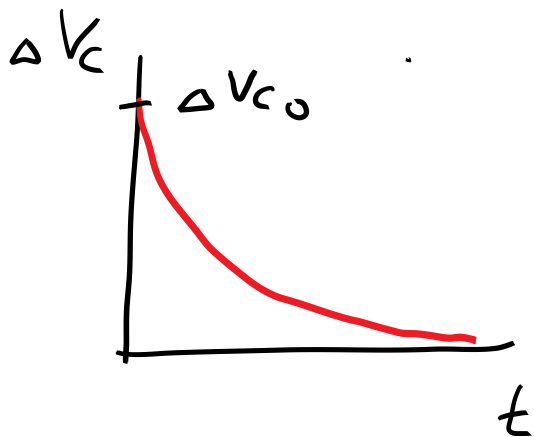
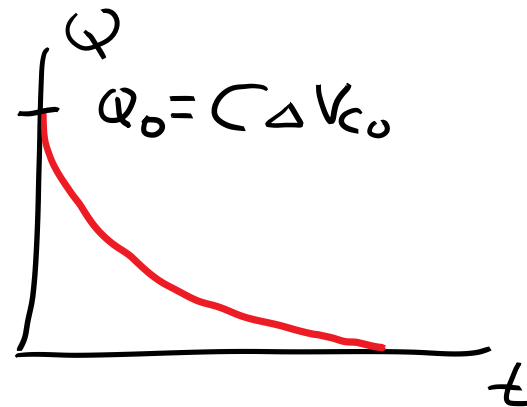
$$\Delta V_c = \Delta V_{c_0} e^{-\frac{t}{RC}}$$



$$Q = Q_0 e^{-\frac{t}{RC}}$$



$\tau = RC$ time constant

Discharging a capacitor:

Thanks to Dr. Pringle for the use of these slides

$$q(t) = Q_0 e^{-\frac{t}{RC}}$$

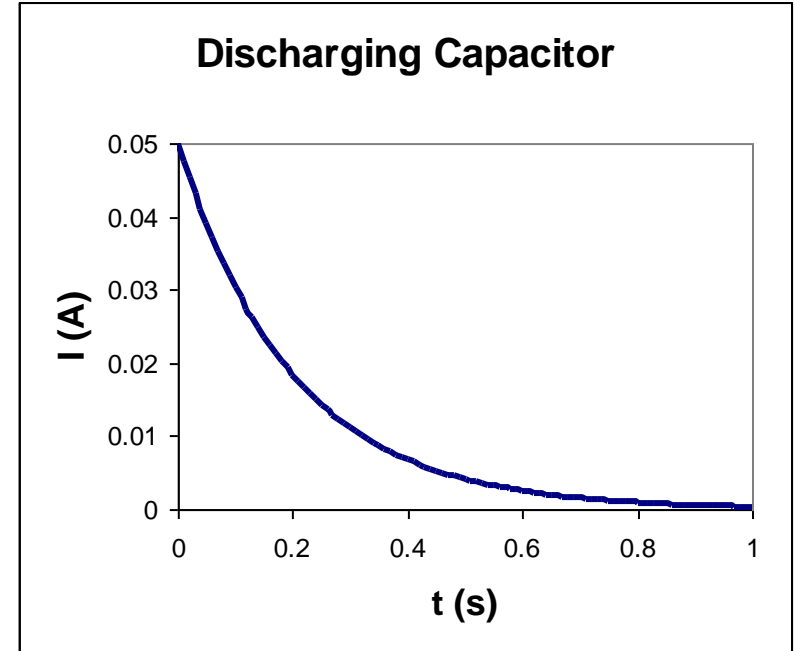
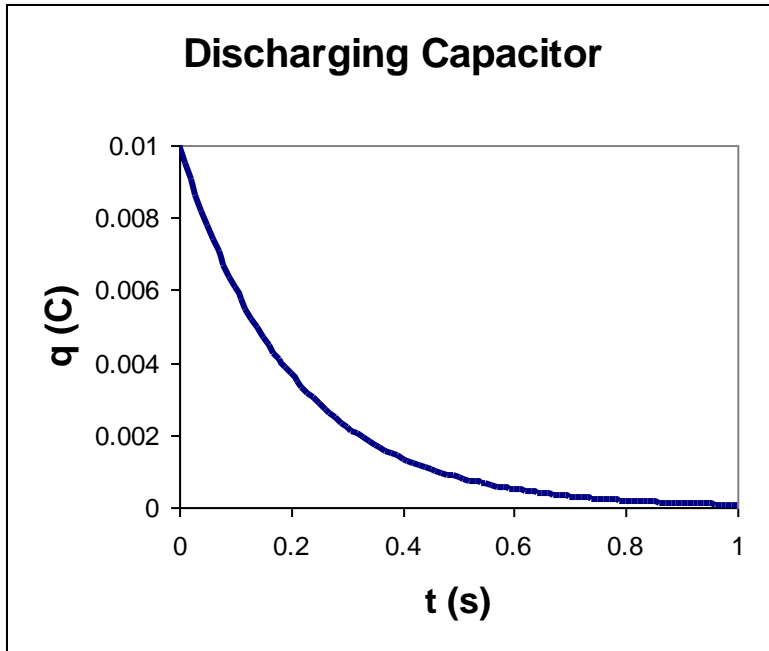
$$I(t) = \frac{\varepsilon}{R} e^{-\frac{t}{RC}}$$



Sample plots with $\varepsilon=10$ V, $R=200$ Ω , and $C=1000$ μF .
 $RC=0.2$ s


In a time $t=RC$, the capacitor discharges to Qe^{-1} or 37% of its capacity...

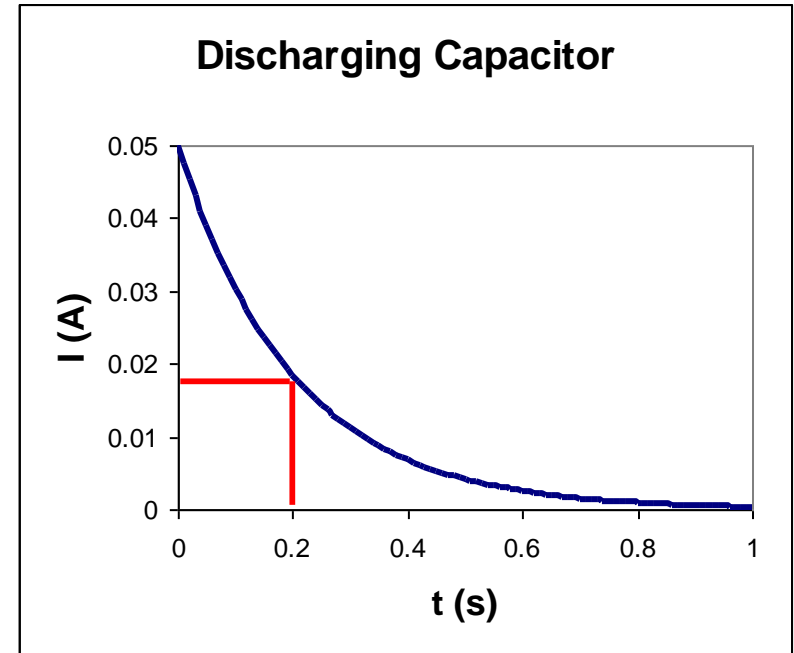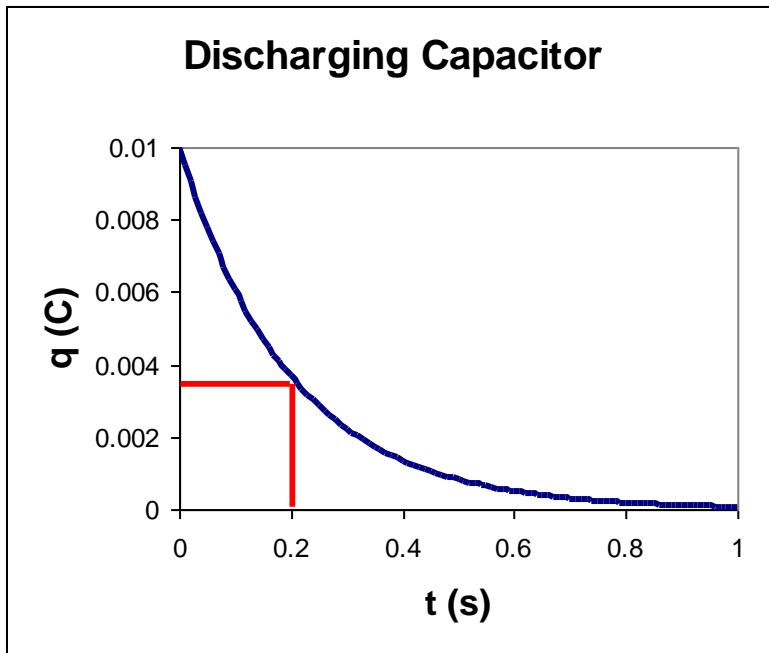...and the current drops to $I_{\max}(e^{-1})$ or 37% of its maximum.



$RC=0.2$ s

Charging a capacitor

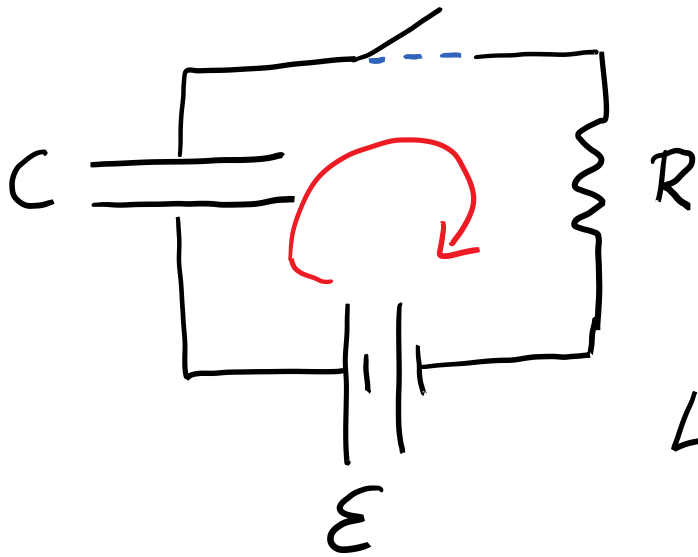

Switch closed at $t = 0$
→ Current flows
→ Capacitor charges




Loop rule: $\sum \Delta V_i = 0$

$$\varepsilon - \frac{Q}{C} - IR = 0$$

$$t = 0: \quad Q = 0 \quad \varepsilon = \underline{I}_0 R \quad \underline{I}_0 = \frac{\varepsilon}{R}$$

$$t \rightarrow \infty: \quad Q \rightarrow Q_f = \varepsilon C \quad \underline{I} \rightarrow 0, \quad \text{"full"}$$

Charging a capacitor

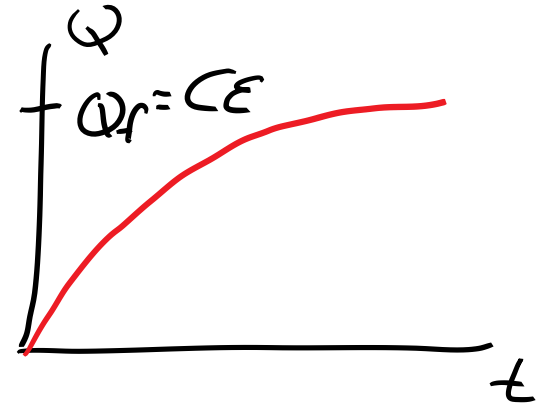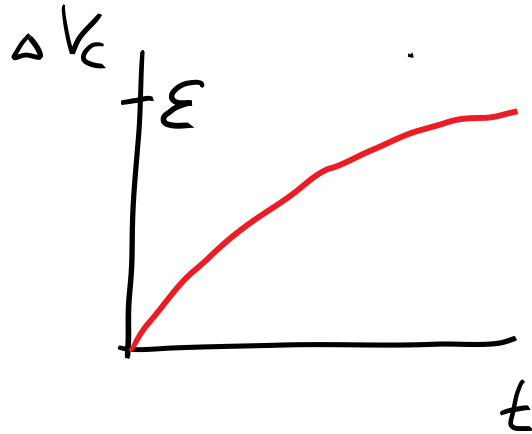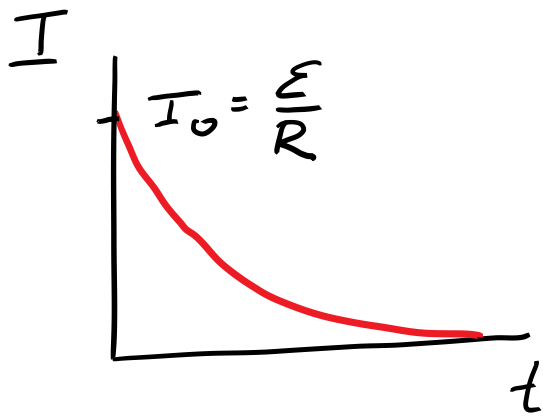

$$I = I_0 e^{-\frac{t}{RC}}$$

$$\Delta V_C = \mathcal{E} (1 - e^{-\frac{t}{RC}})$$

$$Q = Q_f (1 - e^{-\frac{t}{RC}})$$



$\tau = RC$ time constant

Charging a capacitor:

Thanks to Dr. Pringle for the use of these slides

$$q(t) = Q_{\text{final}} \left(1 - e^{-\frac{t}{RC}} \right)$$

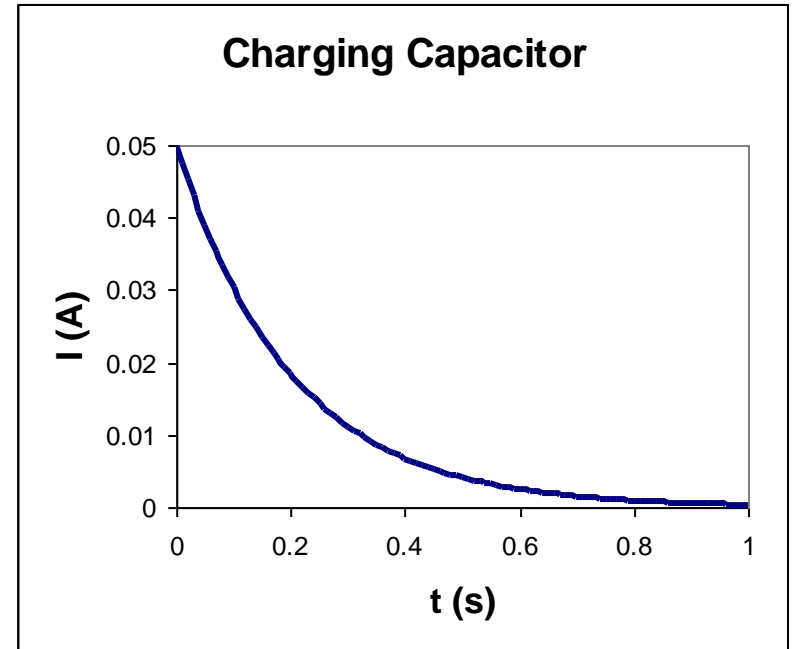
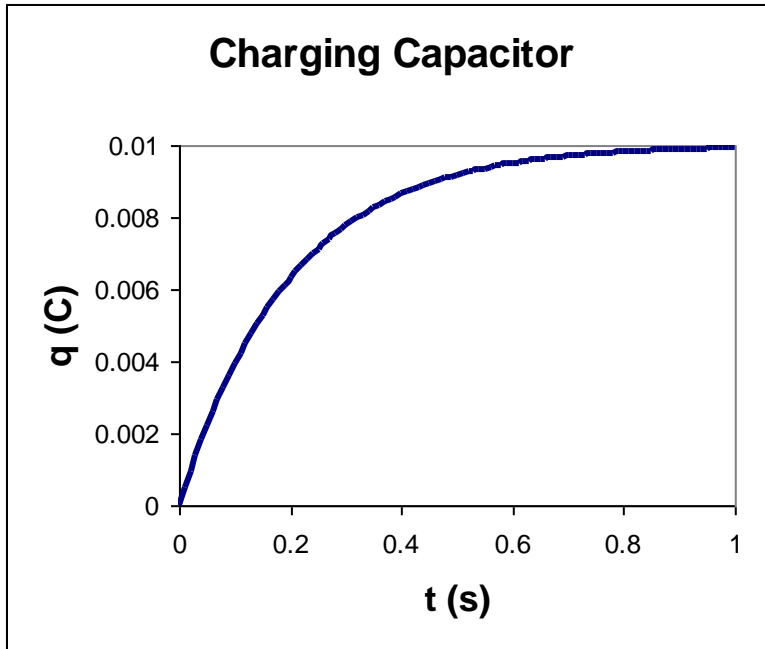
$$I(t) = \frac{\varepsilon}{R} e^{-\frac{t}{RC}}$$



Sample plots with $\varepsilon = 10$ V, $R = 200 \Omega$, and $C = 1000 \mu\text{F}$.
 $RC = 0.2$ s

In a time $t=RC$, the capacitor charges to $Q(1-e^{-1})$ or 63% of its capacity...

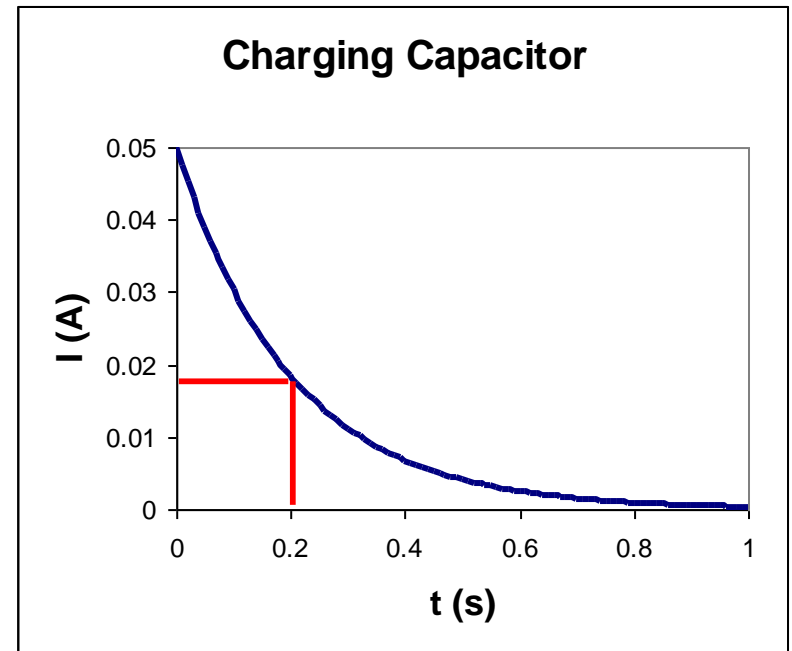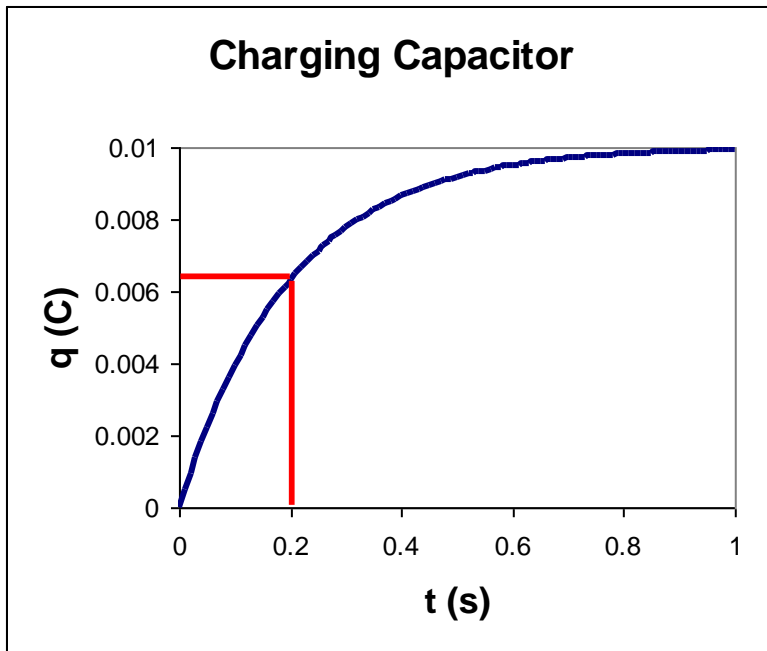...and the current drops to $I_{\max}(e^{-1})$ or 37% of its maximum.



$$RC = 0.2 \text{ s}$$

$\tau = RC$ is called the **time constant** of the RC circuit