

Physics 24 Exam 2

March 18, 2014

Exam Total

200 / 200

Printed Name: _____ **Key** _____

Rec. Sec. Letter: N/A

Five multiple choice questions, 8 points each. Choose the **best** or **most nearly correct** answer.

C 1. You need to store electrical energy with a simple parallel plate capacitor of fixed plate area A_0 and separation d_0 . Which of the following configurations stores the most energy?

- [A] capacitor voltage equals V and dielectric with $\kappa = 3$ between the plates
- [B] capacitor voltage equals $2V$ and dielectric with $\kappa = 1.5$ between the plates
- [C] capacitor voltage equals $3V$ and dielectric with $\kappa = 1$ between the plates
- [D] capacitor voltage equals $2V$ and dielectric with $\kappa = 2$ between the plates

D 2. If the current through an ohmic resistor is doubled, which of the following is true?


- [A] The power dissipated by the resistor doubles and the resistance doubles.
- [B] The power dissipated by the resistor quadruples and the resistance doubles.
- [C] The power dissipated by the resistor doubles and the resistance is unchanged.
- [D] The power dissipated by the resistor quadruples and the resistance is unchanged.

B 3. Your car's intermittent windshield wipers are based on an RC timing circuit. It has a fixed capacitor and a variable resistor, and executes one wiper sweep every τ seconds, where τ is the RC time constant. If you want to decrease the time between wiper sweeps you should

- [A] increase the resistance
- [B] decrease the resistance.

A 4. A proton moves through a region of space that has both a uniform electric field and a uniform magnetic field. The direction of the magnetic field is shown in the diagram. In order for the proton to move through this region with a constant velocity, the direction of the electric field must be

- [A] \downarrow
- [B] \uparrow
- [C] \otimes
- [D] \odot

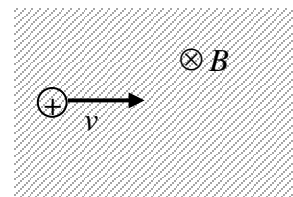


ABCD 5. What would you name the movie that this picture was taken from?

- [A] Attack of the Flying Dogs
- [B] Dawn of the Flying Dogs
- [C] Flight of the Living Dogs
- [D] Flying Dogs Versus Zombies



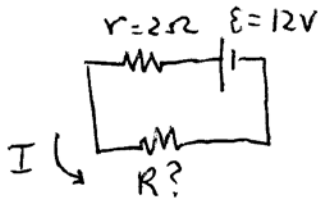6. (10 points total) A battery has an emf of 12 V and an internal resistance of 2 Ω. You connect an external resistor of resistance R across the terminals of the battery and observe that the total power dissipated in the circuit is 18 W. Find R .



$$\mathcal{E} = I(r + R)$$

$$I = \frac{\mathcal{E}}{r + R}$$

$$P_{\text{diss}} = I^2(r + R)$$

$$18 = \frac{\mathcal{E}^2}{(r + R)^2} (r + R)$$

$$18 = \frac{\mathcal{E}^2}{r + R} = \frac{144}{R + 2}$$

$$R + 2 = \frac{144}{18} = 8$$

$$\boxed{R = 6\Omega}$$

There are other correct ways to solve this problem!

7. (30 points total) An air-filled parallel-plate capacitor consists of two circular plates of radius R_0 and plate separation d_0 . It is charged to an initial voltage V_0 .

(a) (10 points) Calculate the energy U_0 stored in the capacitor in terms of R_0 , d_0 , V_0 , and constants.

$$U_0 = \frac{1}{2} C_0 V_0^2 = \frac{1}{2} \frac{\epsilon_0 \pi R_0^2}{d_0} V_0^2 = \boxed{\frac{\epsilon_0 \pi R_0^2 V_0^2}{2d_0}}$$

(b) (20 points) The capacitor is disconnected from the battery. After that, the plates are slowly pulled apart until their distance is $5d_0$. Find the work done by the external force that pulled the plates apart. You may express your answer in terms of R_0 , d_0 , and V_0 , and/or the initial energy U_0 .

$$W_{\text{ext}} = \Delta U = U_f - U_0 \quad C_f = \frac{\epsilon_0 \pi R_0^2}{5d_0} = \frac{C_0}{5}$$

$$U_f = \frac{Q_f^2}{2C_f} = \frac{Q_0^2}{2(C_0/5)} = 5 \frac{Q_0^2}{2C_0} = 5U_0$$

$$W_{\text{ext}} = 5U_0 - U_0$$

$$\boxed{W_{\text{ext}} = 4U_0}$$

There are other ways to solve this.

$$W_{\text{ext}} = 4(C_0 V_0^2) = 2 \frac{\epsilon_0 \pi R_0^2}{d_0} V_0^2$$

is also correct

8. (40 points total) In the circuit shown, a total current of 4A comes out of the battery. The current through resistor R_1 is 2A. The electrical power dissipated by resistor R_1 is 16.0 W. Find R_1 , R_2 , and the emf \mathcal{E} of the battery. Make sure to clearly draw a box around your three answers.

$$P_1 = I_1^2 R_1$$

$$R_1 = \frac{P_1}{I_1^2} = \frac{16}{4}$$

$$\boxed{R_1 = 4 \Omega}$$

$$V_1 = V_2 = V_3 = \mathcal{E} = I_1 R_1 = (2)(4) = 8$$

$$\boxed{\mathcal{E} = 8V}$$


$$\mathcal{E} = I R_{eq} \Rightarrow R_{eq} = \frac{\mathcal{E}}{I} = \frac{8}{4} = 2$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$\frac{1}{R_2} = \frac{1}{R_{eq}} - \frac{1}{R_1} - \frac{1}{R_3} = \frac{1}{2} - \frac{1}{4} - \frac{1}{8} = \frac{4-2-1}{8} = \frac{1}{8}$$

$$\boxed{R_2 = 8 \Omega}$$

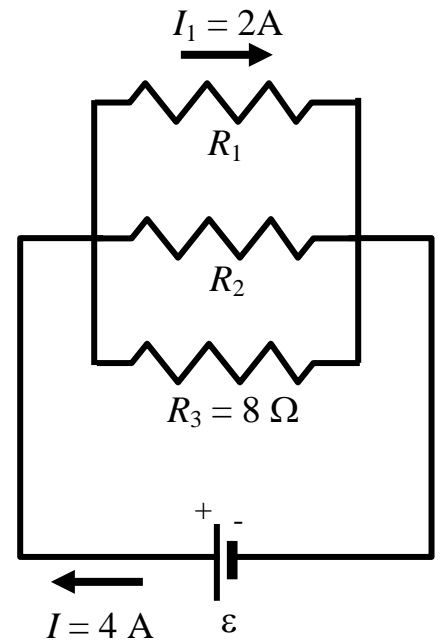As is usually the case for circuit problems, there are other correct ways to solve this.



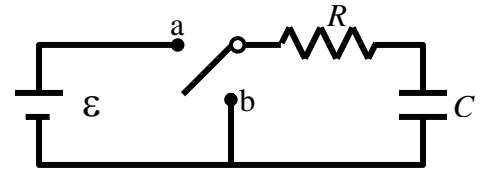9. (40 points total) In the circuit shown with a resistance R , capacitance C , and voltage source ϵ , the capacitor is initially uncharged.



(a) (15 points) The switch is set to position "a" at time $t = 0$. Derive the expression for the current, $I(t)$, through the resistor R , at time t , in terms of R , C , ϵ , and t .

Charging $Q(t) = Q_f(1 - e^{-t/RC})$ where $Q_f = C\epsilon$

$$I(t) = \frac{dQ}{dt} = Q_f(-e^{-t/RC})\left(-\frac{1}{RC}\right) = \frac{Q_f}{RC} e^{-t/RC} = \frac{C\epsilon}{RC} e^{-t/RC}$$

$$I(t) = \frac{\epsilon}{R} e^{-t/RC}$$

(b) (15 points) If $\epsilon = 10V$ what is the voltage across the capacitor when $t = 2RC$?

$$Q(t) = Q_f(1 - e^{-t/RC})$$

$$CV(t) = C\epsilon(1 - e^{-t/RC})$$

$$V(t) = \epsilon(1 - e^{-t/RC})$$

$$V(2RC) = \epsilon(1 - e^{-2RC/RC}) = \epsilon(1 - e^{-2}) = 10(1 - e^{-2})$$

$$V = 8.65V$$

(c) (10 points) After a long time, the capacitor fully charges to a value of $5 \mu C$. Then the switch is set to position "b." What is the charge on the capacitor when the voltage across the capacitor drops to $2V$?

Discharging $Q(t) = Q_0 e^{-t/RC}$

$$CV(t) = C\epsilon e^{-t/RC} \quad Q_0 = C\epsilon \text{ because "fully charged"}$$

$$V(t) = \epsilon e^{-t/RC}$$

$$2 = 10 e^{-t/RC} \Rightarrow e^{-t/RC} = \frac{2}{10} = \frac{1}{5}$$

See note about this problem on page 6.

When $e^{-t/RC} = \frac{1}{5}$

$$Q(t) = Q_0 e^{-t/RC} = 5\left(\frac{1}{5}\right) \left(\frac{1}{5}\right)$$

$$Q(t) = 1 \mu C$$

10. (20 points) A beam of positive ions moves in a clockwise orbit with a 10.0 cm radius inside a uniform 0.500 T magnetic field pointing out of the page, as shown in the figure below. The ions have a mass of 6.64×10^{-27} kg and a speed of 4.82×10^6 m/s.


(a) (15 points) What is the charge on each ion?

$$F_B = |q \vec{v} \times \vec{B}| = qvB = ma = m \frac{v^2}{R}$$

$$qvB = \frac{mv^2}{R}$$

\vec{v} and \vec{B} are perpendicular

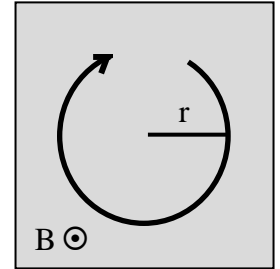We don't need absolute value signs around q because we are told it is positive.



$$q = \frac{mv}{RB} = \frac{(6.64 \times 10^{-27})(4.82 \times 10^6)}{(0.1)(0.5)} = \boxed{6.4 \times 10^{-19} \text{ C}}$$

(b) (5 points) According to your answer for part (a), how many electrons were removed from each neutral atom to produce an ion?

$$N = \frac{q}{|e|} = \frac{6.4 \times 10^{-19}}{1.6 \times 10^{-19}} = \boxed{4 \text{ electrons removed}}$$

11. (20 points) A square loop made of a single turn of current-carrying wire is oriented vertically with its top half in a uniform magnetic field and is found to hover in midair. The loop has a total mass m , side length L , and carries a current I . Find the magnitude B of the magnetic field. Express your answer in terms of m , L , I , and any necessary constants.

$\vec{F}_1 = -\vec{F}_2$ magnetic forces on vertical segments are equal magnitude, opposite direction




$$\sum \vec{F} = m\vec{a}$$

$$F_3 - W = 0$$

$$ILB = W = mg$$

$$\boxed{B = \frac{mg}{IL}}$$

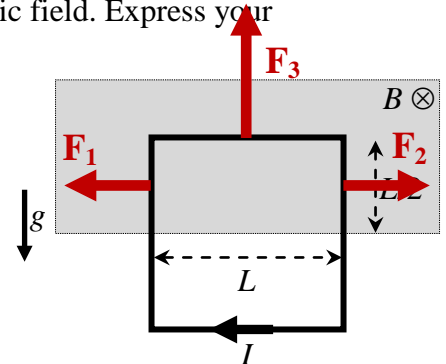

$$|\vec{F}_3| = |I \vec{L} \times \vec{B}| = ILB$$

\vec{L} and \vec{B} are perpendicular

Here is another way to do part c. Very simple, and correct.

(c) (10 points) After a long time, the capacitor fully charges to a value of $5 \mu\text{C}$. Then the switch is set to position "b." What is the charge on the capacitor when the voltage across the capacitor drops to 2V ?

The capacitance doesn't change. Let Q_0 be the full charge ($5 \mu\text{C}$) when the capacitor is fully charged to V_0 (10 volts). Let Q_1 be the charge when the capacitor voltage is $V_1 = 2$ volts. Then

$$C = \frac{Q_0}{V_0} = \frac{Q_1}{V_1}$$

$$\frac{5}{10} = \frac{Q_1}{2}$$

$$Q_1 = 1\mu\text{C}$$