
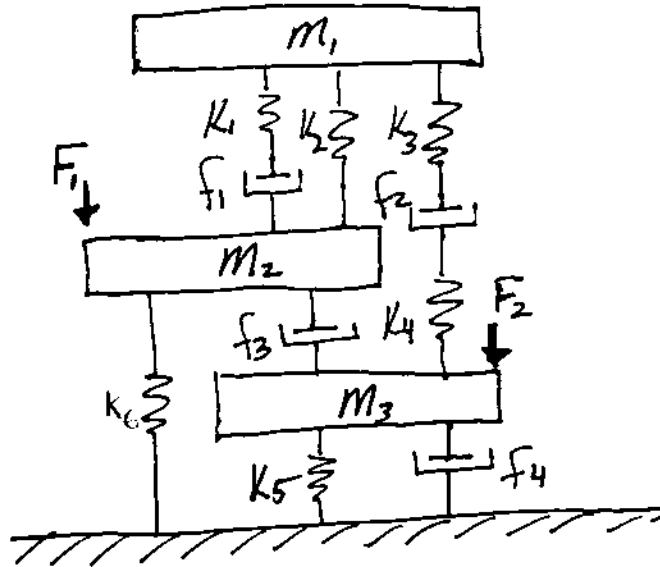


Copyright © 1996 by Levent Acar. All rights reserved. No parts of this document may be reproduced, stored in a retrieval system, or transmitted in any form or by any means without the written permission of the copyright holder(s).

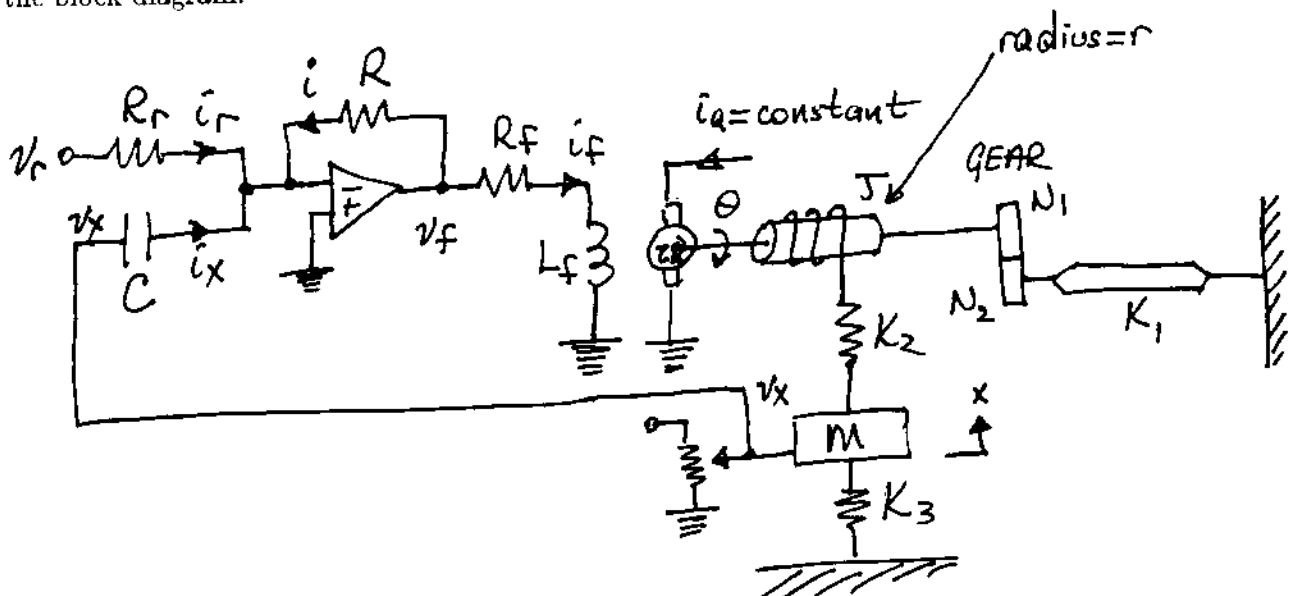
- For the mechanical system shown below, obtain *either* the force-voltage *or* the force-current analog of the system. (25pts)




- In the following system, the location of a mass is controlled by a motor control system. Assuming that the input and the output are v_r and x , respectively, and the voltage from the variable resistor is linearly related to the location of the mass, such that $v_x = k_x x$; obtain a detailed block diagram of the system without reducing or combining the equations, and show the variables v_r , i_r , v_x , i_x , i , v_f , i_f , τ , θ , and x on the block diagram. (30pts)



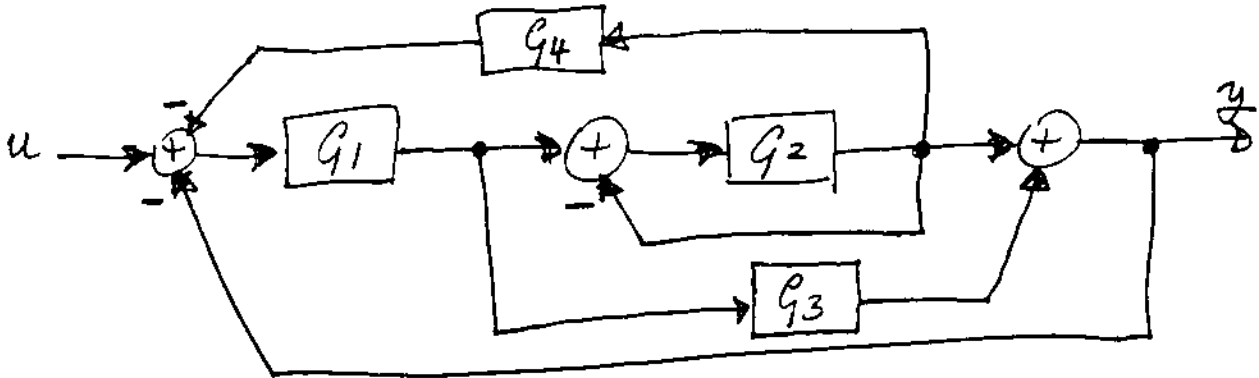
3. For the block diagram given below, determine the transfer function *either* by block diagram reduction, *or* by Mason's formula. Show your work clearly. (25pts)



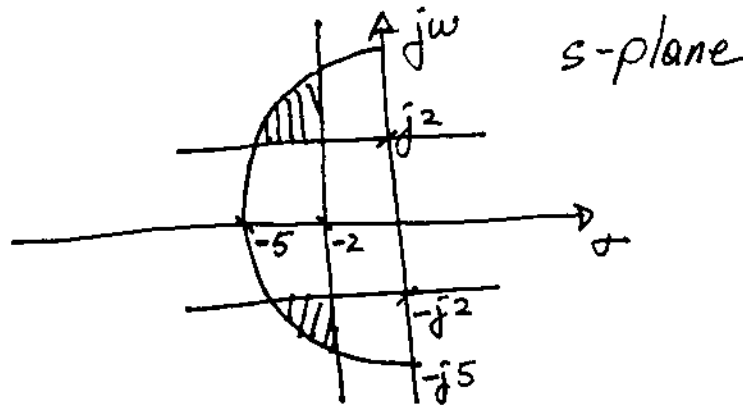4. Obtain the necessary inequalities to describe the poles in the shaded region below in terms of only ζ and ω_n of a second-order system described by $Y(s)/U(s) = \omega_n^2 / (s^2 + 2\zeta\omega_n s + \omega_n^2)$. (20pts)



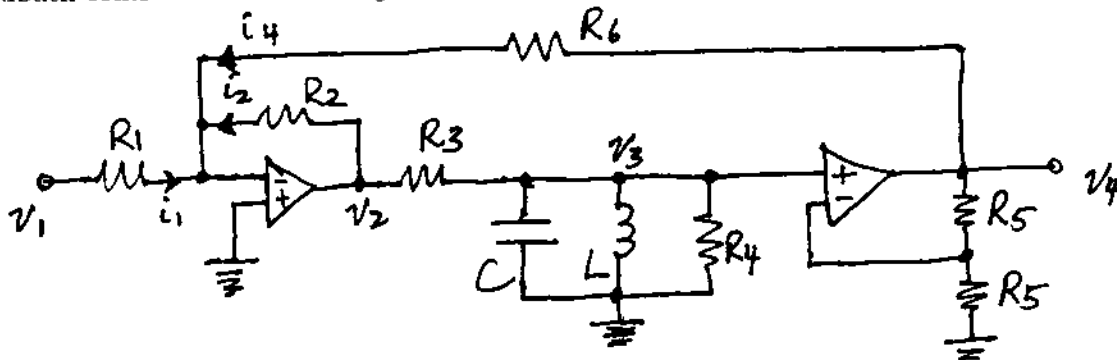
5. A feedback controller is to be designed for the following circuit.




- (a) First, determine its block diagram, such that the variables v_1 , i_1 , i_2 , v_2 , v_3 , and v_4 are clearly shown. Then, obtain its transfer function from the block diagram, where v_1 is the input, and v_4 is the output. (+25pts)
- (b) Assuming that $R_1 = 5\Omega$, $R_3 = 2\Omega$, $R_4 = 4\Omega$, $R_5 = 1\Omega$, $R_6 = 5\Omega$, $L = 4\text{H}$, and $C = 1\text{F}$; design for R_2 , such that the $t_{5\%s} \approx 40/3\text{s}$. (+15pts)

#1


Copyright © 1996
by Levent Acar

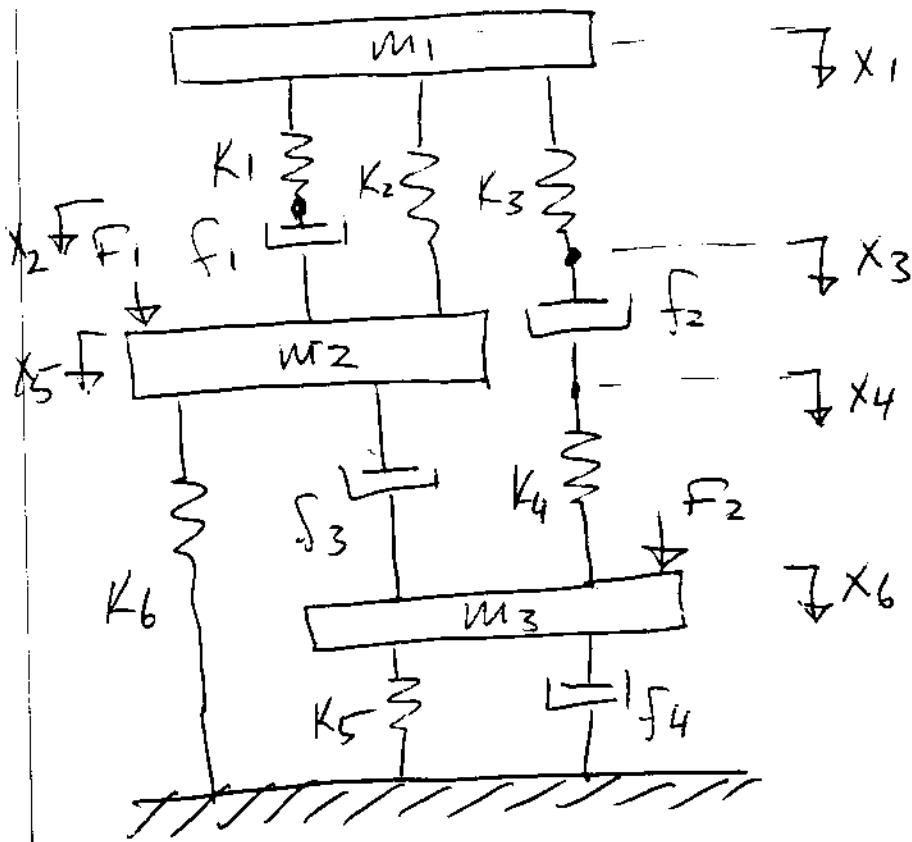

FORCE-VOLTAGE


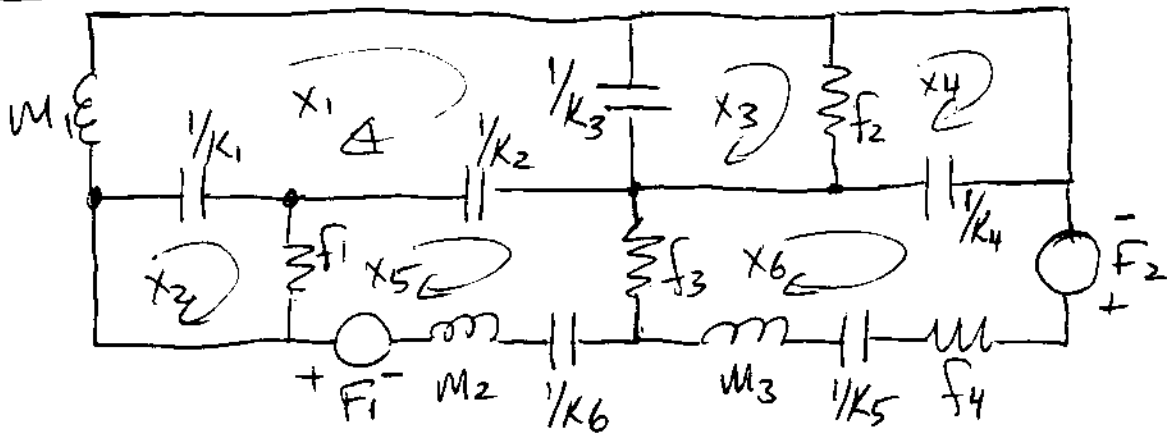


FORCE-CURRENT


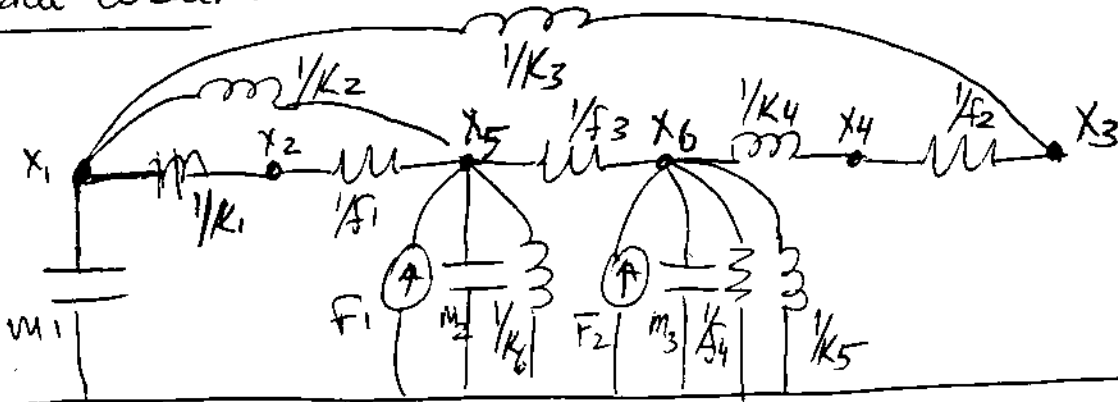


NATIONAL INSTRUMENTS COMPANY
 11000 SHILOH ROAD
 DALLAS, TEXAS 75243
 214-343-7000
 FAX 214-343-7001
 NATIONAL BRAND
 NATIONAL INSTRUMENTS COMPANY


#2

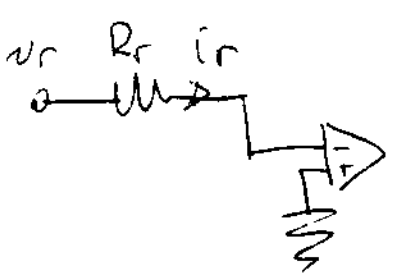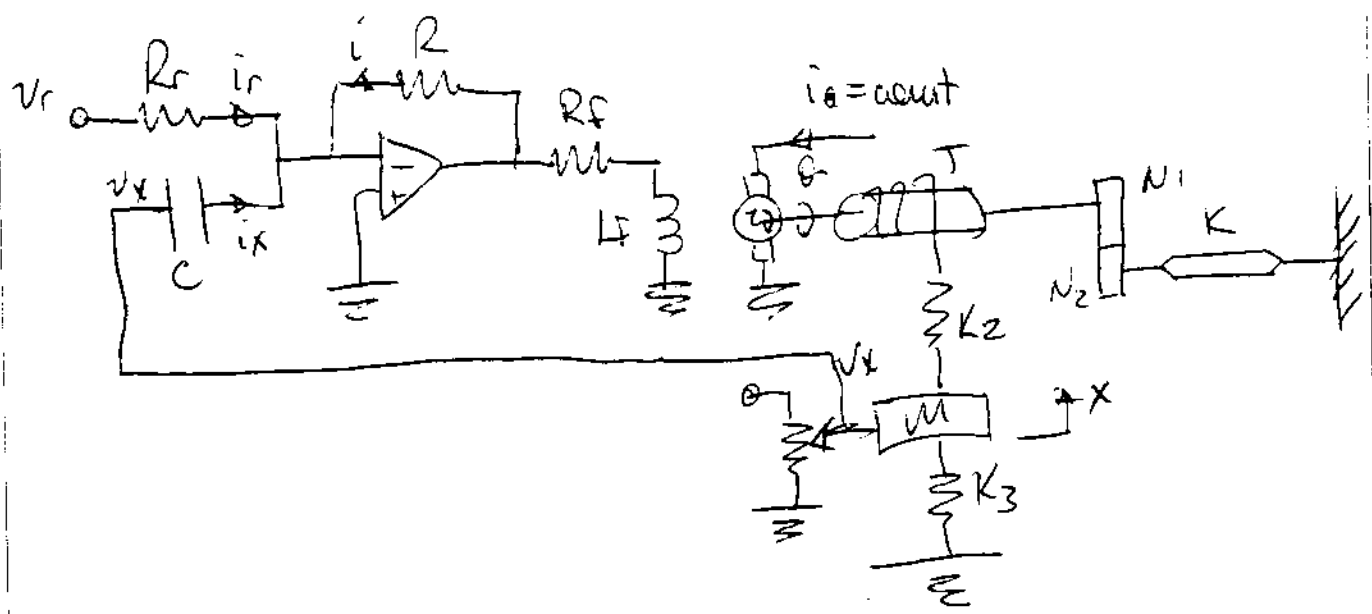

$$i_r = \frac{v_r}{R_r}$$

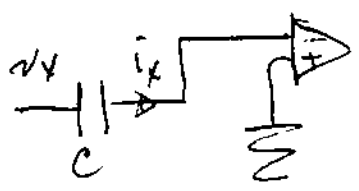
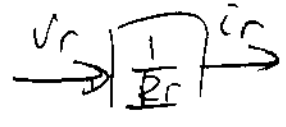


$$i_x = \frac{v_x}{1/sC} = sC v_x$$


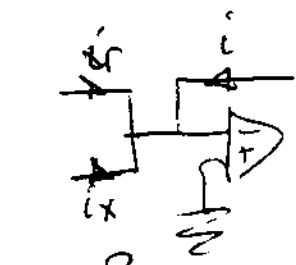


$$i + i_r + i_x = 0$$


$$i = -(i_r + i_x)$$

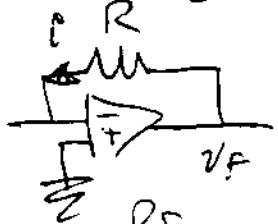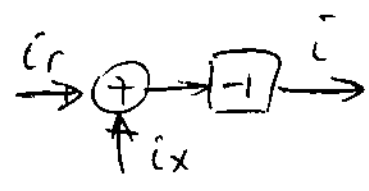

$$v_f = R i$$

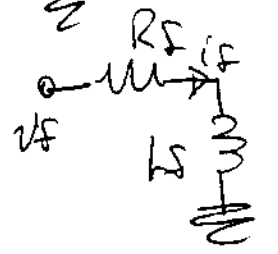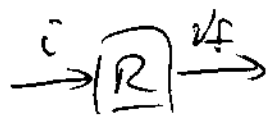


$$i_f = \frac{1}{L_f s + R_f} v_f$$

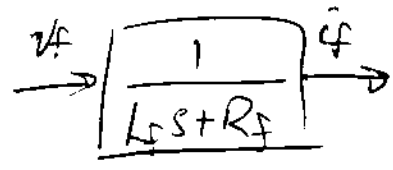


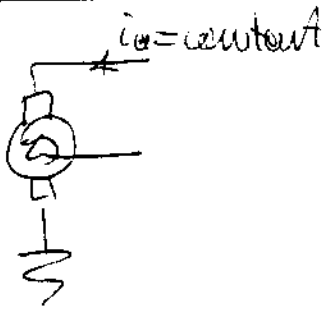10-984
12-983
14-982
16-981
18-980
20-979
22-978
24-977
26-976
28-975
30-974
32-973
34-972
36-971
38-970
40-969
42-968
44-967
46-966
48-965
50-964
52-963
54-962
56-961
58-960
60-959
62-958
64-957
66-956
68-955
70-954
72-953
74-952
76-951
78-950
80-949
82-948
84-947
86-946
88-945
90-944
92-943
94-942
96-941
98-940
100-939
102-938
104-937
106-936
108-935
110-934
112-933
114-932
116-931
118-930
120-929
122-928
124-927
126-926
128-925
130-924
132-923
134-922
136-921
138-920
140-919
142-918
144-917
146-916
148-915
150-914
152-913
154-912
156-911
158-910
160-909
162-908
164-907
166-906
168-905
170-904
172-903
174-902
176-901
178-900
180-899
182-898
184-897
186-896
188-895
190-894
192-893
194-892
196-891
198-890
200-889







$$c = K_f i_f$$

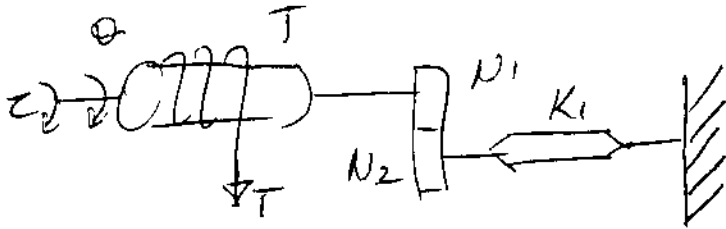


$$J \dot{s} \theta = \tau + rT - \left(\frac{N_1}{N_2}\right)^2 K_1 \theta$$
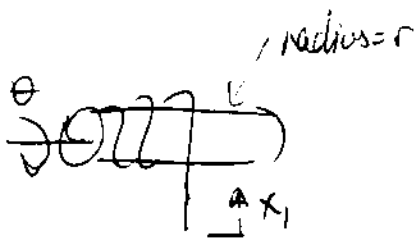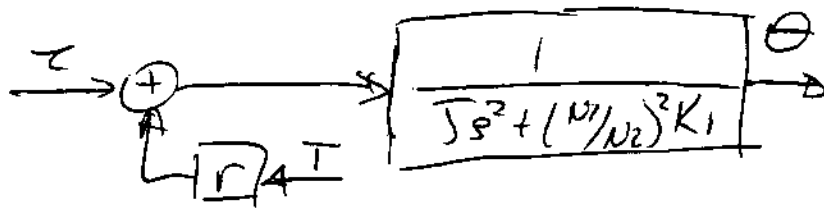
$$\theta = \frac{1}{J s^2 + \left(\frac{N_1}{N_2}\right)^2 K_1} (\tau + rT)$$



$$x_1 = -r\theta$$

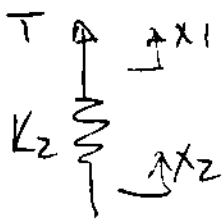


$$0 = T - K_2 (x_1 - x_2)$$

$$T = K_2 (x_1 - x_2)$$



11 787
12 381
13 381
14 381
100 381





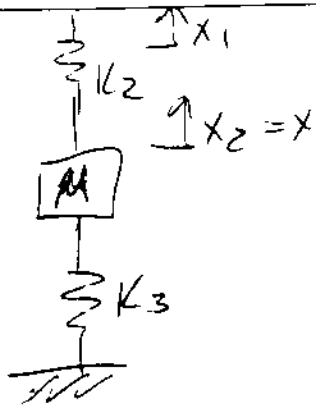


$$Ms^2 X_2 = -K_2(x_2 - x_1) - K_3 X_2$$

$$(Ms^2 + K_2 + K_3) X_2 = K_2 X_1$$

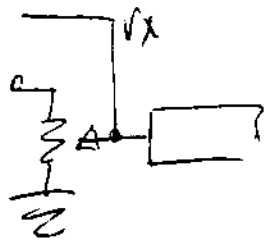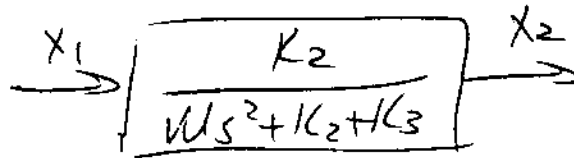
$$X_2 = \frac{K_2}{Ms^2 + K_2 + K_3} X_1$$




$$v_x = K_x X$$

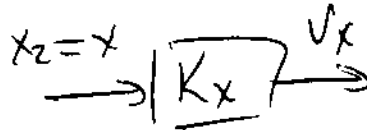




12 381 50 SHEETS (15" x 10") 5 SQUARE
 42 381 100 SHEETS (15" x 10") 5 SQUARE
 42 382 100 SHEETS (15" x 10") 5 SQUARE
 42 383 200 SHEETS (15" x 10") 5 SQUARE
 42 384 200 SHEETS (15" x 10") 5 SQUARE
 42 385 200 SHEETS (15" x 10") 5 SQUARE
 42 386 200 SHEETS (15" x 10") 5 SQUARE
 42 387 200 SHEETS (15" x 10") 5 SQUARE
 42 388 200 SHEETS (15" x 10") 5 SQUARE
 42 389 200 SHEETS (15" x 10") 5 SQUARE
 42 390 200 SHEETS (15" x 10") 5 SQUARE
 42 391 200 SHEETS (15" x 10") 5 SQUARE
 42 392 200 SHEETS (15" x 10") 5 SQUARE
 42 393 200 SHEETS (15" x 10") 5 SQUARE
 42 394 200 SHEETS (15" x 10") 5 SQUARE
 42 395 200 SHEETS (15" x 10") 5 SQUARE
 42 396 200 SHEETS (15" x 10") 5 SQUARE
 42 397 200 SHEETS (15" x 10") 5 SQUARE
 42 398 200 SHEETS (15" x 10") 5 SQUARE
 42 399 200 SHEETS (15" x 10") 5 SQUARE
 42 400 200 SHEETS (15" x 10") 5 SQUARE
 MADE IN U.S.A.

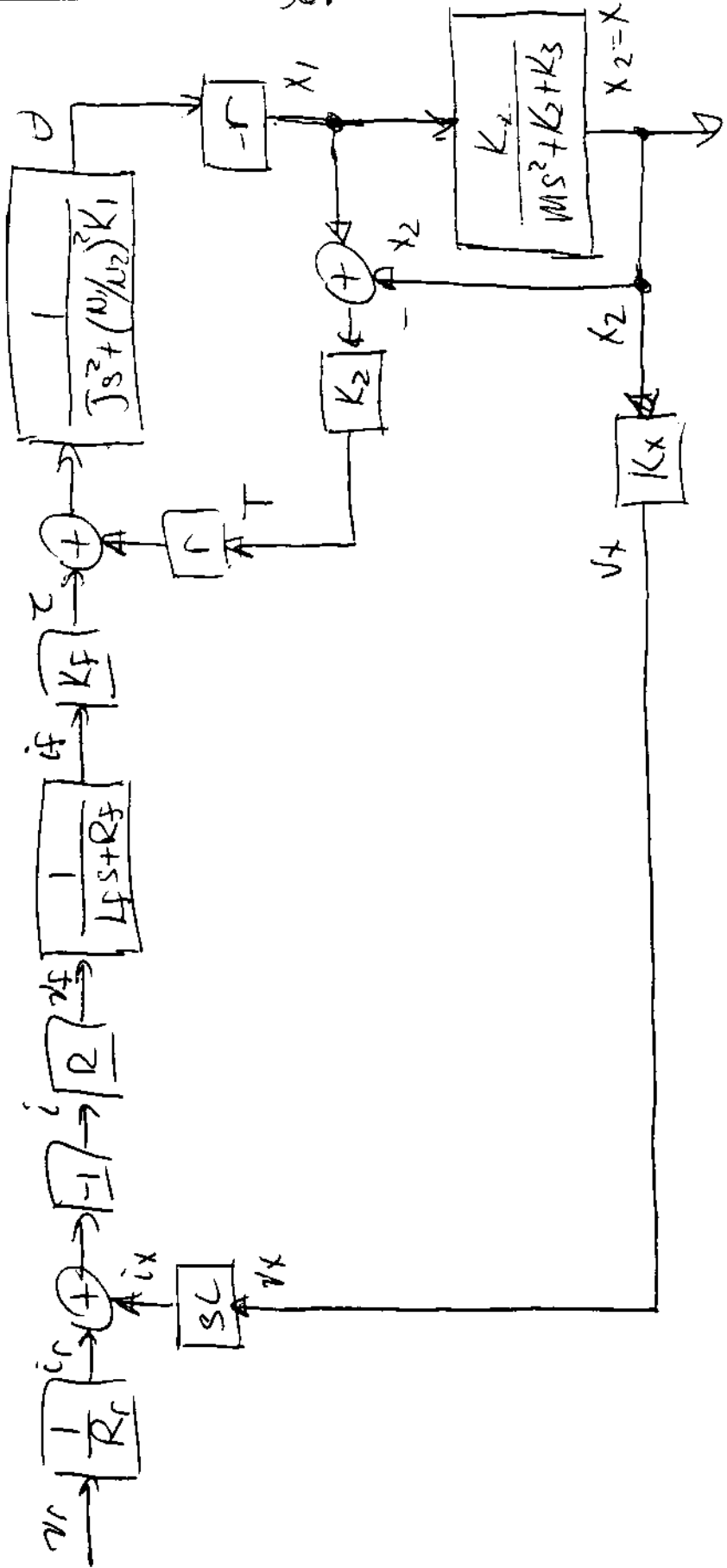

#3

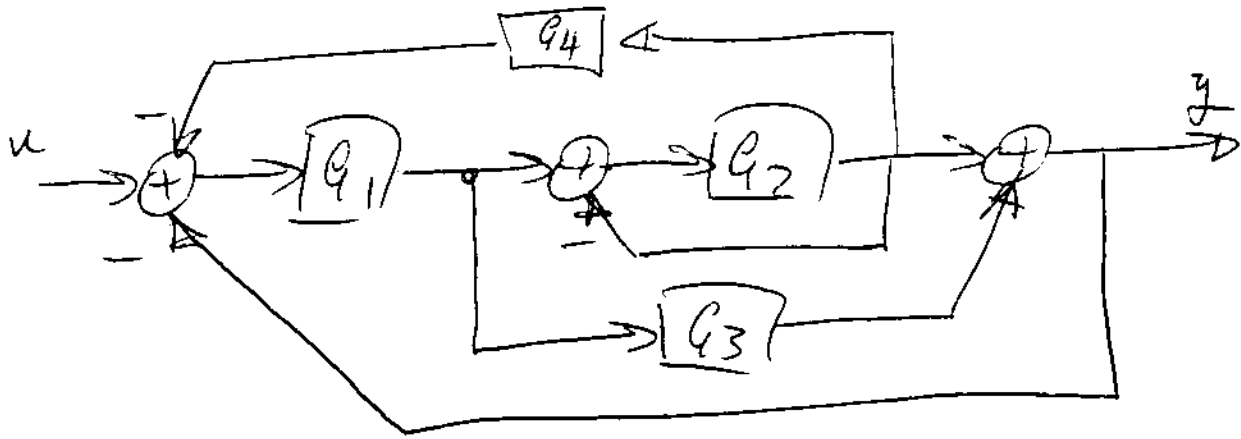

BLOCK DIAGRAM REDUCTION

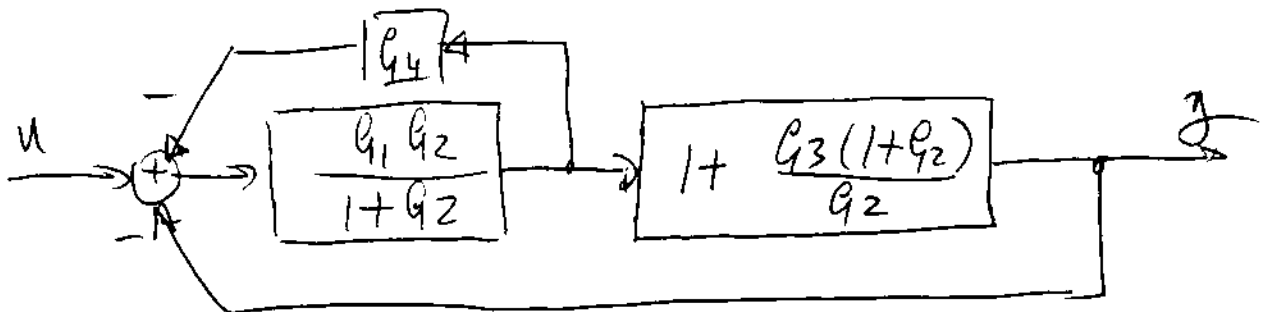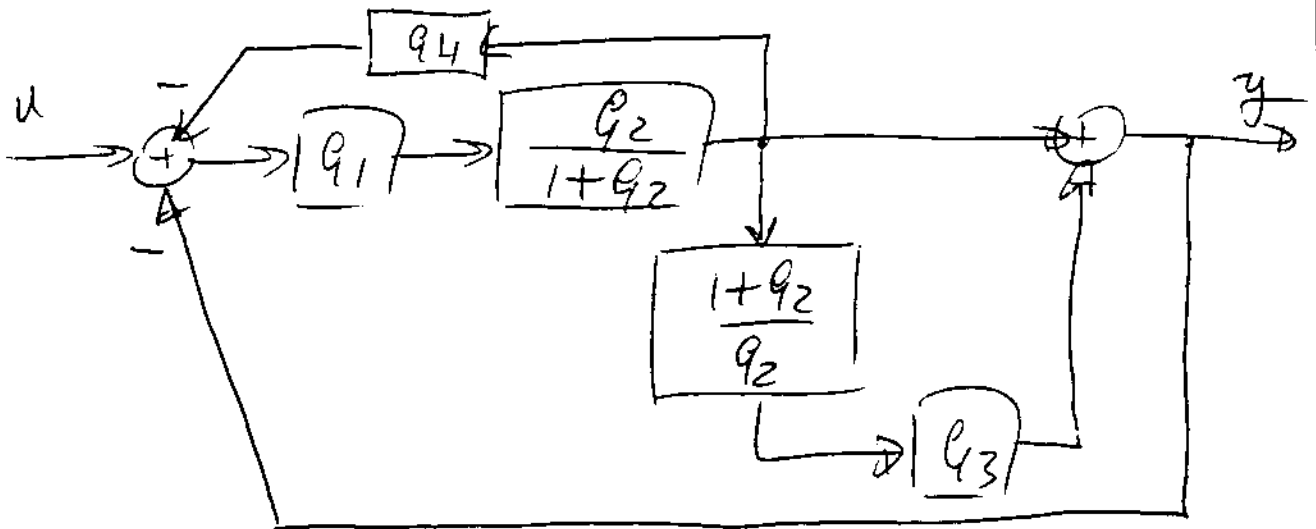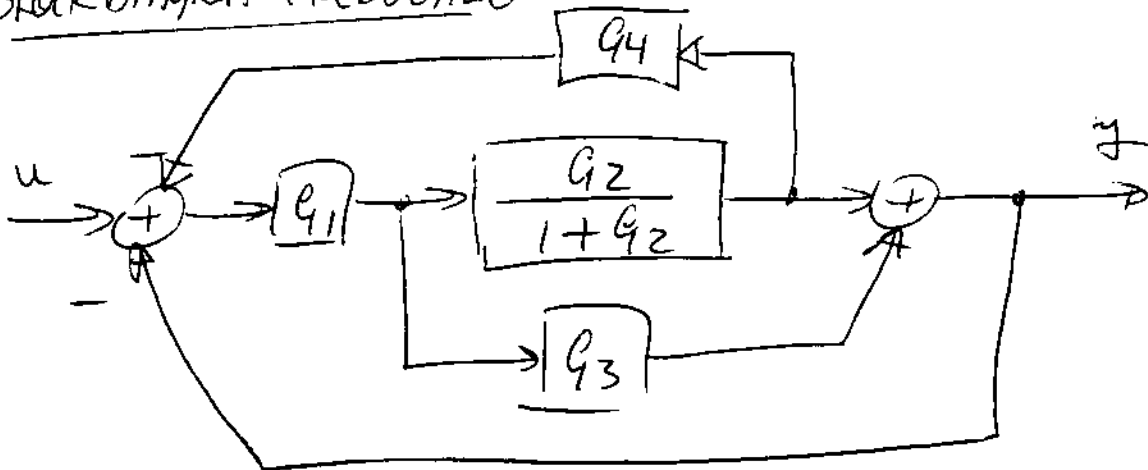

13 SHEETS
12 SHEETS
10 SHEETS
8 SHEETS
6 SHEETS
4 SHEETS
2 SHEETS
1 SHEET



TOUCHING
LOOPS

	l_1	l_2	l_3	l_4
l_1		T	T	N
l_2			T	T
l_3				T
l_4				

Only non-touching pair is l_1 & l_4

LOOPS OF

FORWARD PATHS

	l_1	l_2	l_3	l_4
F_1	0	0	0	0
F_2	N	0	0	0

$$\begin{aligned} \text{So } \Delta &= 1 - (l_1 + l_2 + l_3 + l_4) + l_1 l_4 \\ &= 1 + g_2 + g_1 g_2 g_4 + g_1 g_2 + g_1 g_3 \\ &\quad + g_2 g_1 g_3 \end{aligned}$$

$$\text{and } \Delta_1 = \Delta \Big|_{l_1=l_2=l_3=l_4=0} = 1$$



$$\Delta_2 = \Delta \Big|_{l_2=l_3=l_4=0} = 1 - l_1 = 1 + g_2$$

$$\Rightarrow \frac{y}{u} = \frac{g_1 g_2 + g_1 g_3 (1 + g_2)}{1 + g_2 + g_1 g_2 g_4 + g_1 g_2 + g_1 g_3 + g_1 g_2 g_3}$$



42 281
42 282
42 283
42 284
42 285
42 286
42 287
42 288
42 289
42 290
42 291
42 292
42 293
42 294
42 295
42 296
42 297
42 298
42 299
42 300
42 301
42 302
42 303
42 304
42 305
42 306
42 307
42 308
42 309
42 310
42 311
42 312
42 313
42 314
42 315
42 316
42 317
42 318
42 319
42 320



#5

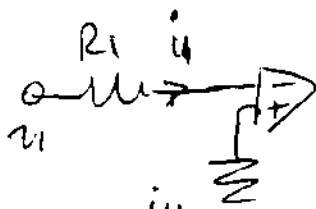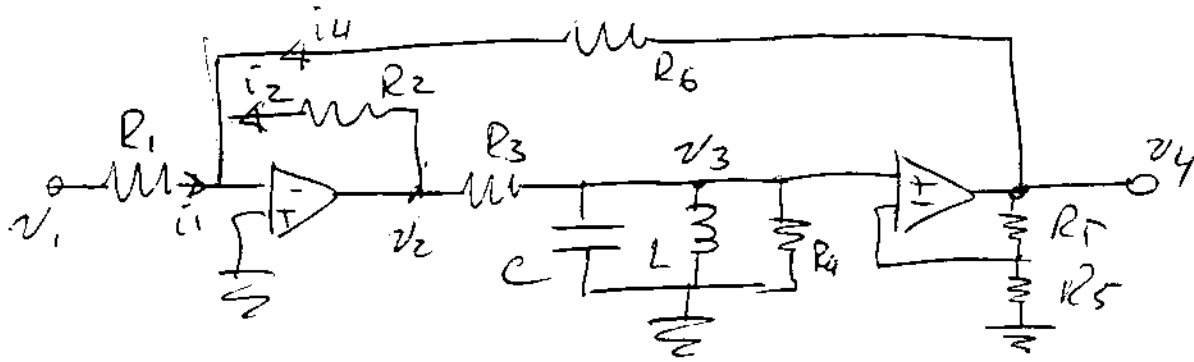


$$i_1 = \frac{1}{R_1} v_1$$

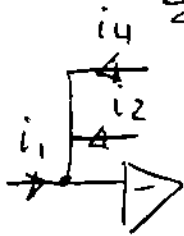
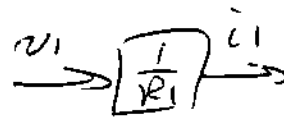


$$i_1 + i_2 + i_4 = 0$$

$$i_2 = -(i_1 + i_4)$$

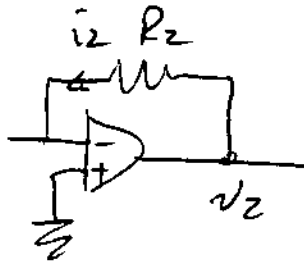


$$v_2 = R_2 i_2$$

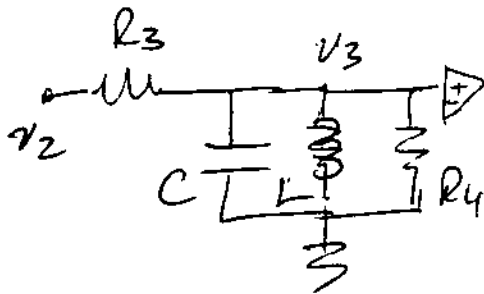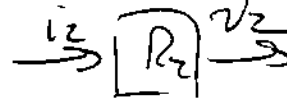


$$\frac{v_3}{1} = \frac{v_2}{R_3 + \frac{1}{sC + \frac{1}{sL} + R_4}}$$

$$v_3 = \frac{1}{R_3 C s + R_3/L s + R_3 R_4 + 1} v_2$$


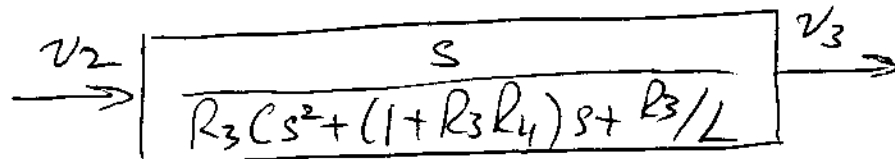
$$v_3 = \frac{s}{R_3 C s^2 + (1 + R_3 R_4) s + R_3/L} v_2$$





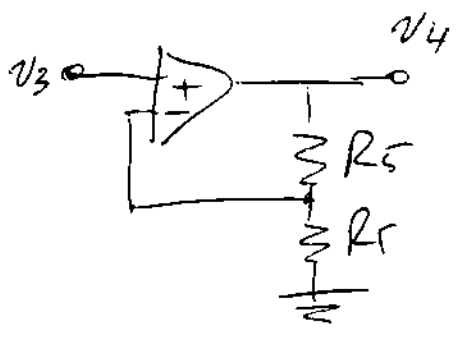


$$\frac{v_4}{2R_5} = \frac{v_3}{R_1}$$

$$v_4 = 2v_3$$

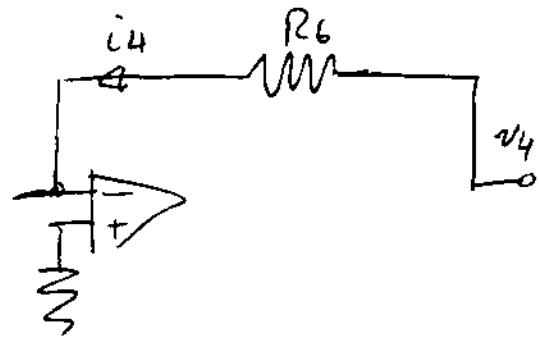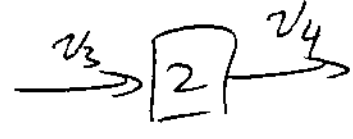

$$i_4 = \frac{1}{R_6} v_4$$

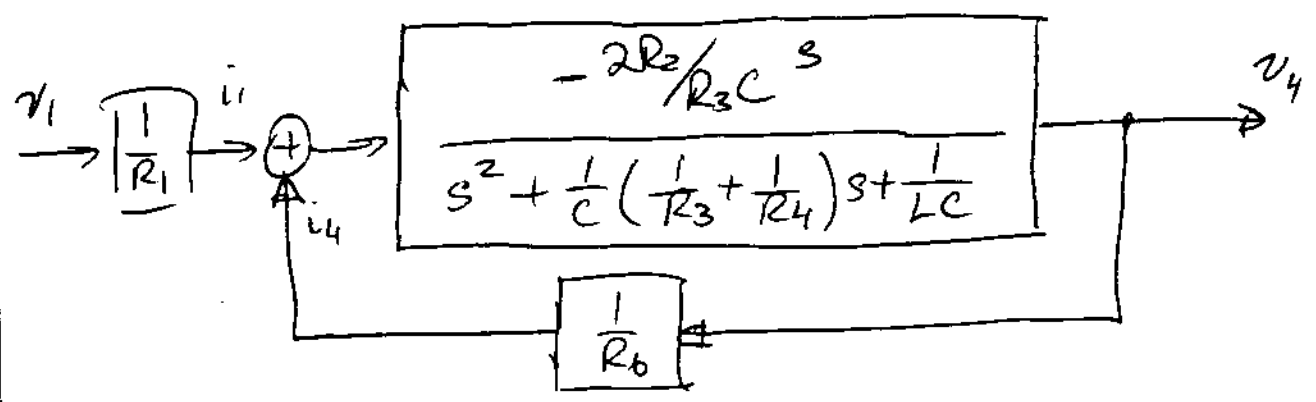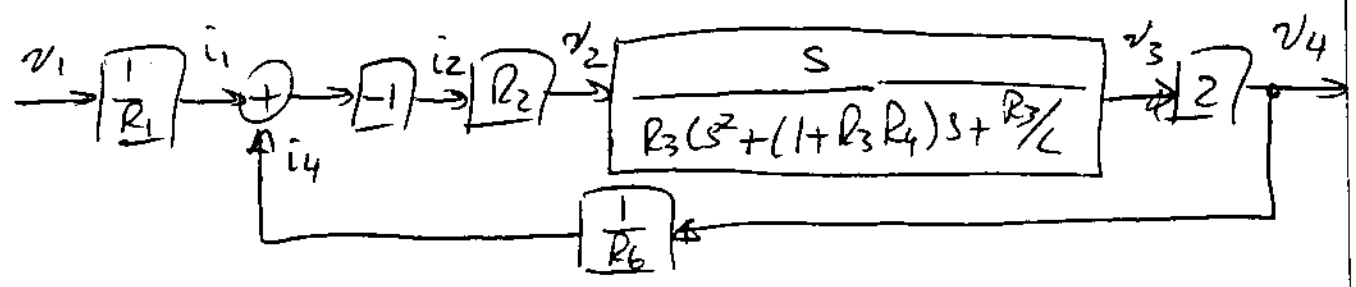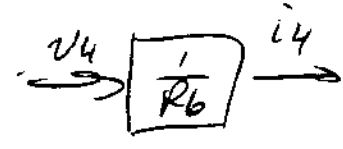

NATIONAL INSTRUMENTS COMPANY
 4200 WEST WILSON AVENUE
 DENVER, COLORADO 80231
 303 750 0000
 FAX 303 750 0000
 WWW.NI.COM
 © 1996 NATIONAL INSTRUMENTS COMPANY
 ALL RIGHTS RESERVED
 PRINTED IN THE USA
 NI-10000-01-0000-0000

$$\frac{v_4}{v_1} = \frac{1}{R_1} \frac{-2R_2/R_3 C s}{s^2 + \frac{1}{C} \left(\frac{1}{R_3} + \frac{1}{R_4} \right) s + \frac{1}{LC} - \left(-\frac{2R_2}{R_3 C} s \cdot \frac{1}{R_6} \right)}$$

Closed-loop poles $s^2 + \frac{1}{C} \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{2R_2}{R_3 R_6} \right) s + \frac{1}{LC} = 0$

$$t_{5\%s} \approx \frac{40}{3} \Rightarrow \frac{3}{\zeta \omega_n} = \frac{40}{3}$$

$$\zeta \omega_n = \frac{9}{40}$$

From the closed-loop pole eqn.

$$s^2 + 2\zeta \omega_n s + \omega_n^2 = 0$$

$$2\zeta \omega_n = \frac{1}{C} \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{2R_2}{R_3 R_6} \right)$$

$$\text{or } \frac{1}{C} \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{2R_2}{R_3 R_6} \right) = 2 \cdot \frac{9}{40}$$

$$C = 1 \text{ F}, R_3 = 2 \Omega, R_4 = 4 \Omega, \text{ and } R_6 = 5 \Omega$$

$$\frac{1}{1} \left(\frac{1}{2} + \frac{1}{4} + \frac{2R_2}{2 \cdot 5} \right) = \frac{9}{20}$$

$$\frac{R_2}{5} = \frac{9}{20} - \frac{3}{4} = -\frac{6}{20}$$

$$\Rightarrow R_2 = -\frac{3}{2} \Omega \quad \text{Ops, this was supposed to be positive.}$$